



DR. GYURCSEK ISTVÁN

Basic Laws of Electrical Circuits

Sources and additional materials (recommended)

- ❑ *Dr. Gyurcsek – Dr. Elmer: Theories in Electric Circuits, GlobeEdit, 2016, ISBN:978-3-330-71341-3*
- ❑ *Ch. Alexander, M. Sadiku: Fundamentals of Electric Circuits, 6th Ed., McGraw Hill NY 2016, ISBN: 978-0078028229*
- ❑ *Simonyi K.: Villamosságtan. AK Budapest 1983, ISBN:9630534134*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságtan 1. MK Budapest 2002, TK szám: 49203/I*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságtan 2. TK Budapest 2002, ISBN:9631026043*
- ❑ *Zombory L.: Elektromágneses terek. MK Budapest 2006, (www.electro.uni-miskolc.hu)*




- Network topology, KCL, KVL**
- Characteristics of Circuit Elements
- Passive Equivalent Transformations


Nodes, Branches, Loops



Fundamental theorem of network topology:

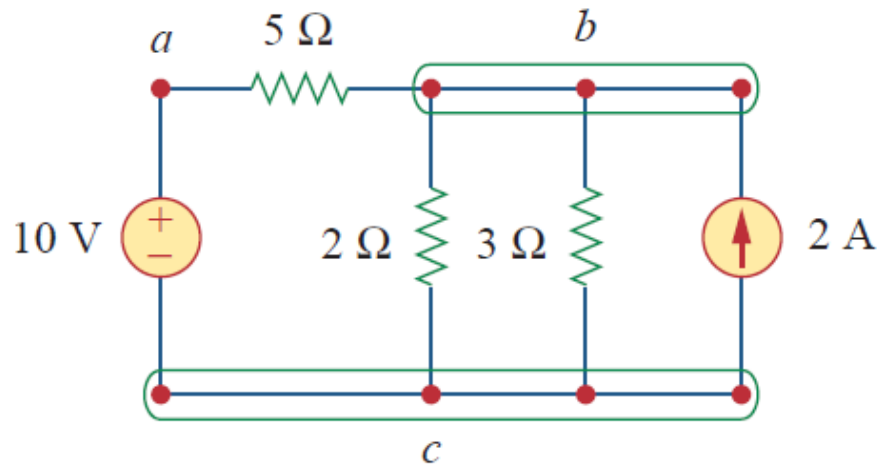


$$b = l + n - 1$$

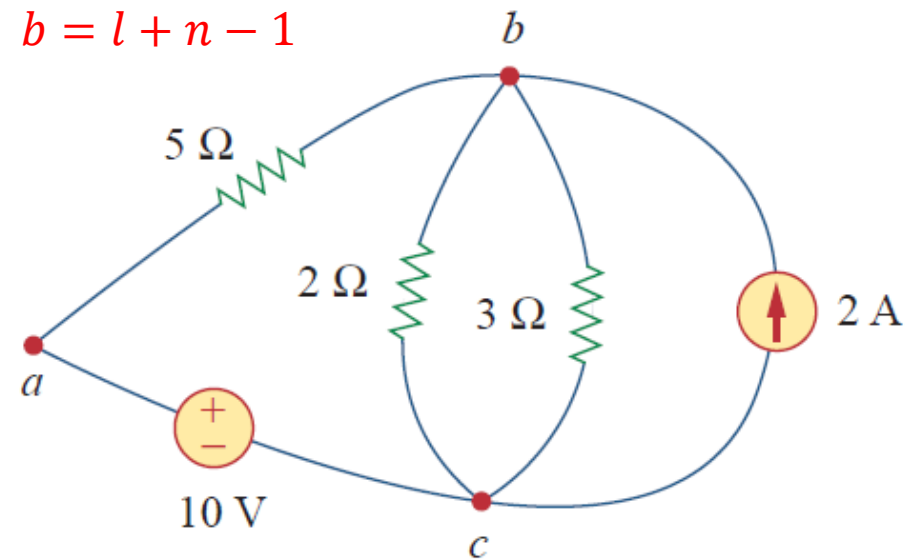

Recall:

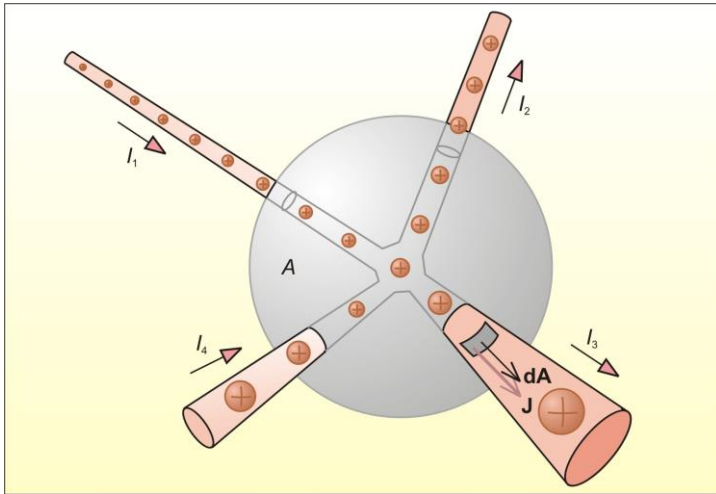Eq. of Continuity - Work Over a Closed Path



$$W = \oint_l \mathbf{F} d\mathbf{l} = \oint_l q \mathbf{E} d\mathbf{l} = 0$$

(E – conservative, curl-free vector field)

$$W = q V = q \oint_l \mathbf{E} d\mathbf{l} = 0$$

Equation of continuity

$$\oint_A \mathbf{J} d\mathbf{A} = 0 \quad \dots (\leftarrow \text{div } \mathbf{J} = 0)$$

$$\oint_l \mathbf{E} d\mathbf{l} = 0$$

$\mathbf{J} \rightarrow$ curly, divergence-less (source-less)

$$\oint_A \mathbf{J} d\mathbf{A} = \sum_{i=1}^n I_i = 0$$

$$\sum_{i=1}^n v_i = 0$$


KCL, KVL



Algebraic sum of currents entering a node (or a closed boundary) is zero. (*Sum of the currents entering a node is equal to the sum of the currents leaving the node.*)

$$\sum_{n=1}^N i_n = 0 \quad \sum i_{\text{entering}} - \sum i_{\text{leaving}} = 0$$


$$I_1 - I_2 + I_3 + I_4 - I_5 = 0$$

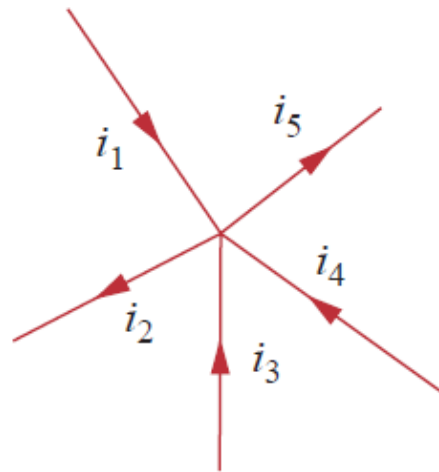

Algebraic sum of all voltages around a closed path (or loop) is zero. (*Sum of voltage drops = sum of voltage rises.*)

$$\sum_{m=1}^M v_m = 0 \quad \sum v_{\text{drops}} - \sum v_{\text{rises}} = 0$$

$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

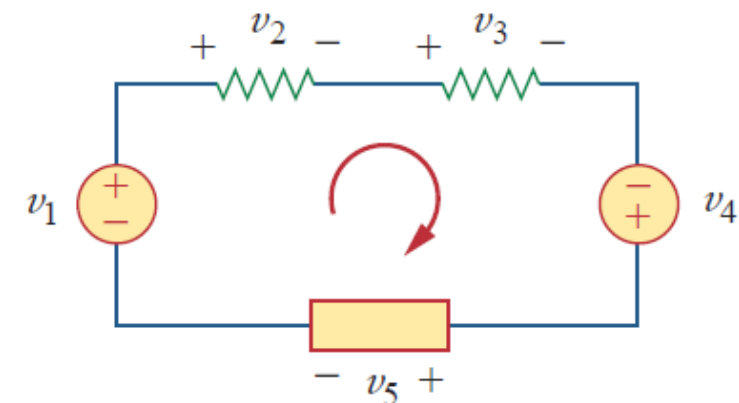




- Network topology, KCL, KVL
- **Characteristics of Circuit Elements**
- Passive Equivalent Transformations


Ohm's Law



Ohm's Law

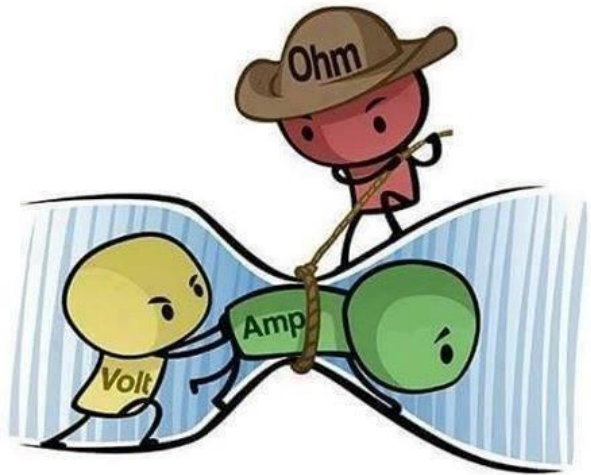

$$R = \rho \cdot \frac{l}{A}$$




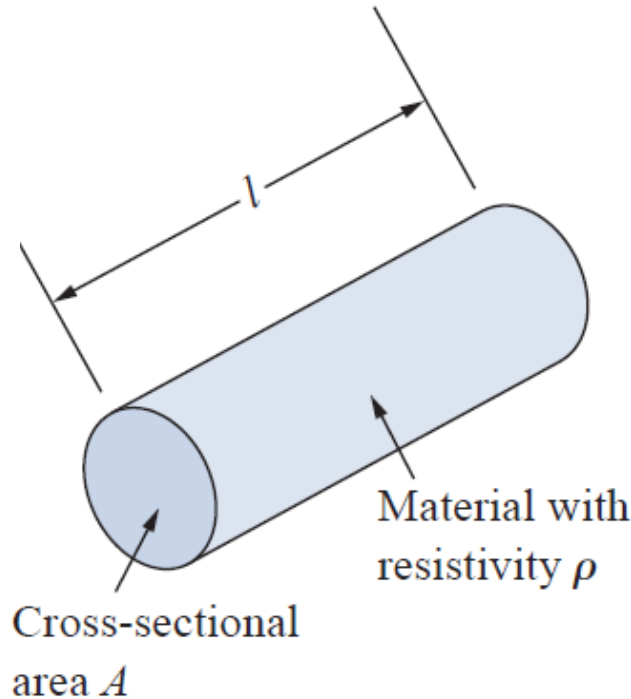


$$J = \frac{1}{\rho} \cdot E \rightarrow i = \frac{1}{R} \cdot v$$

$$J = \sigma \cdot E \rightarrow i = G \cdot v$$

Material	Spec. Resistivity ($\Omega \text{ m}$)	Usage
Silver	$1.64 \cdot 10^{-8}$	Conductor
Copper	$1.72 \cdot 10^{-8}$	Conductor
Gold	$2.45 \cdot 10^{-8}$	Conductor
Aluminum	$2.80 \cdot 10^{-8}$	Conductor
Carbon	$4 \cdot 10^{-5}$	Semiconductor
Germanium	$47 \cdot 10^{-2}$	Semiconductor
Silicon	$6.4 \cdot 10^{-2}$	Semiconductor
Paper	10^{10}	Insulator
Mica	$5 \cdot 10^{11}$	Insulator
Glass	10^{12}	Insulator
Teflon	$3 \cdot 10^{12}$	Insulator

Sort of Resistors

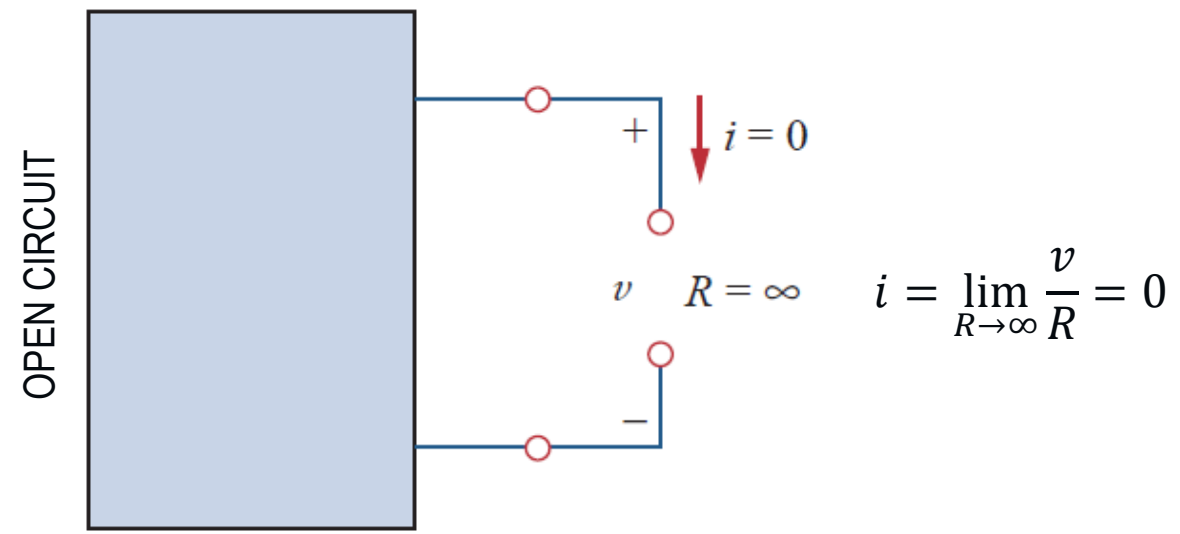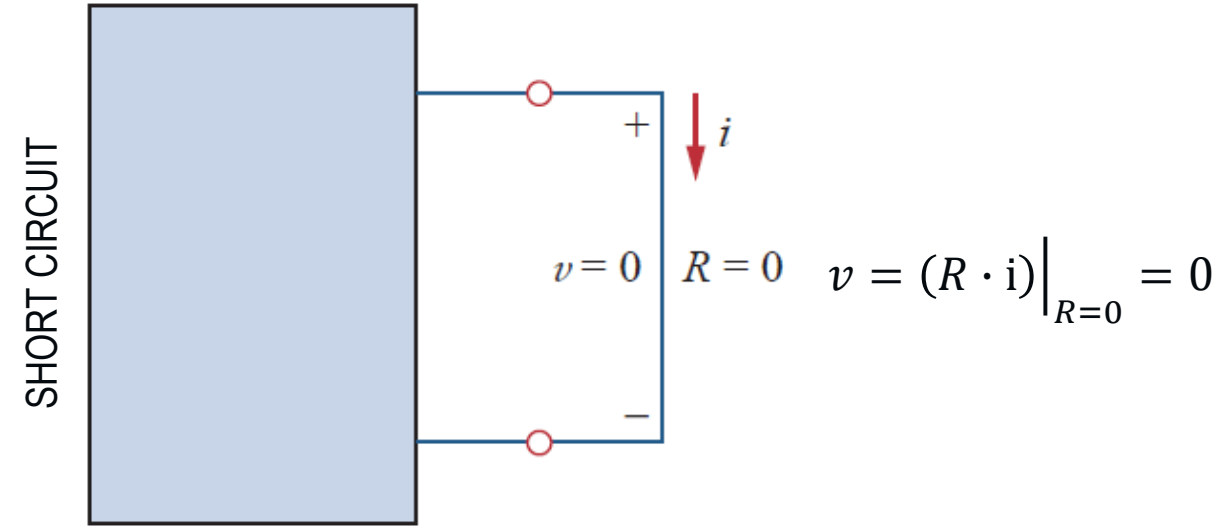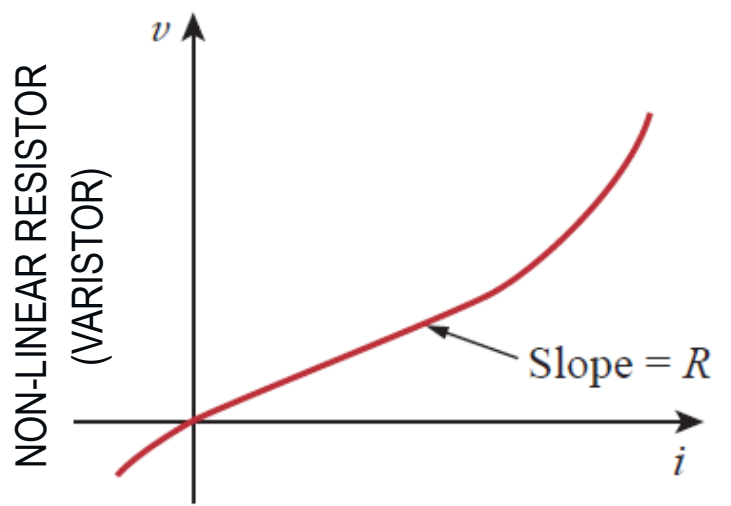
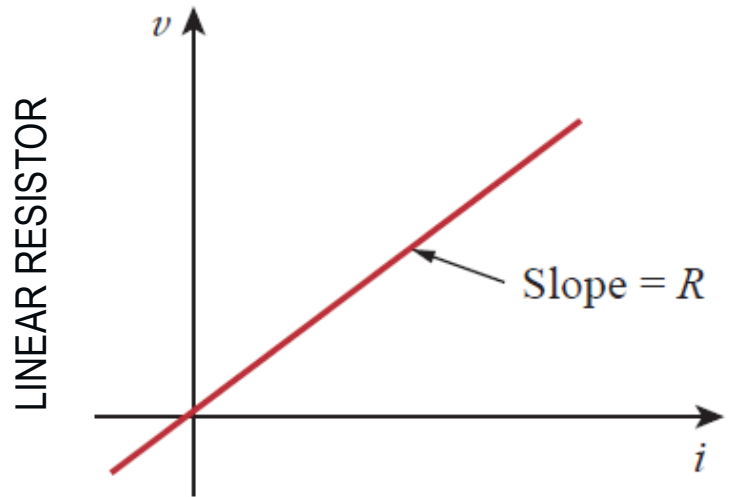


DC Behavior of L and C




$$v(t) = L \frac{di(t)}{dt}$$
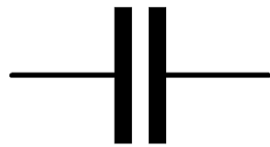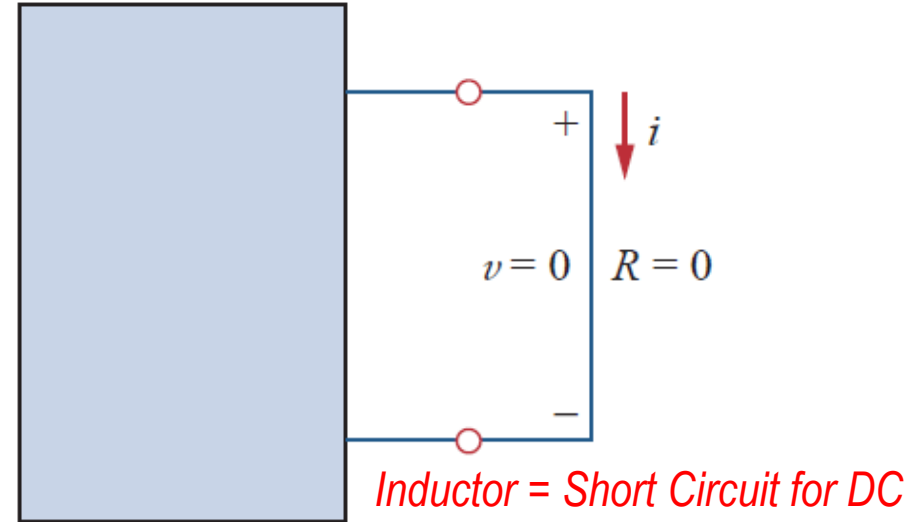
$$i(t) = \text{constant} \rightarrow v(t) = 0$$



$$i(t) = C \frac{dv(t)}{dt}$$

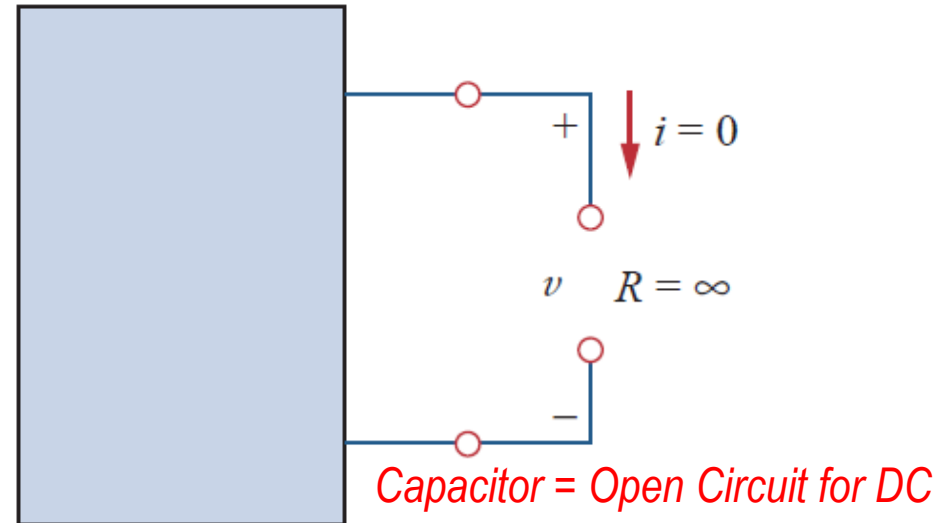
$$v(t) = \text{constant} \rightarrow i(t) = 0$$







- ❑ Network topology, KCL, KVL
- ❑ Characteristics of Circuit Elements
- ❑ **Passive Equivalent Transformations**


Equivalent Transform

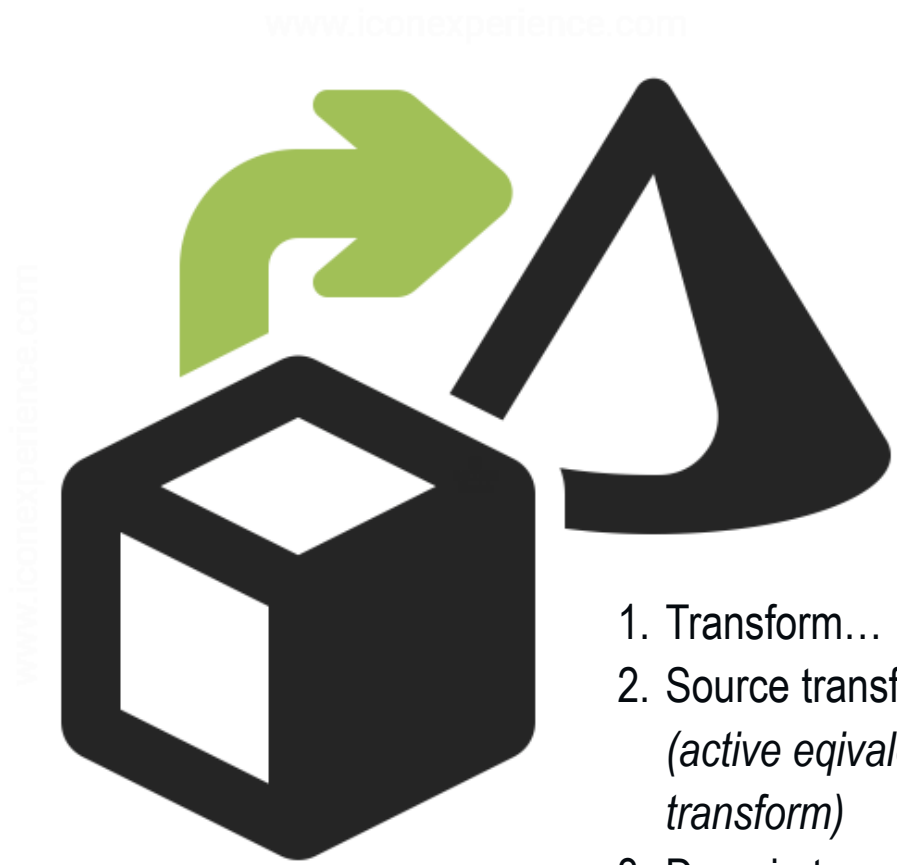

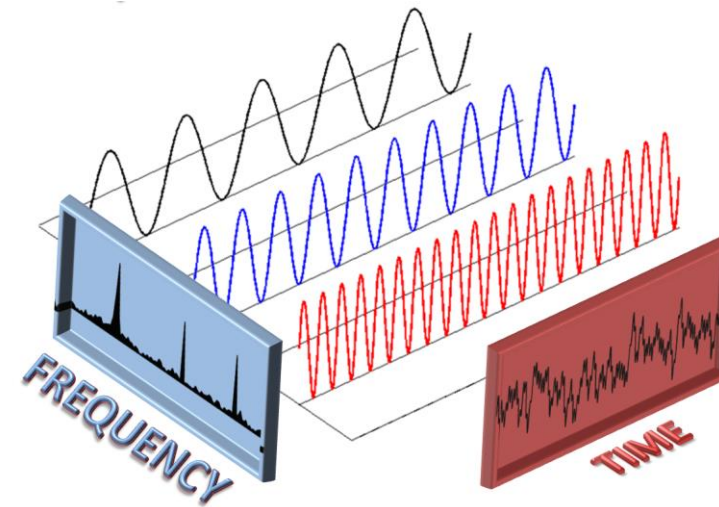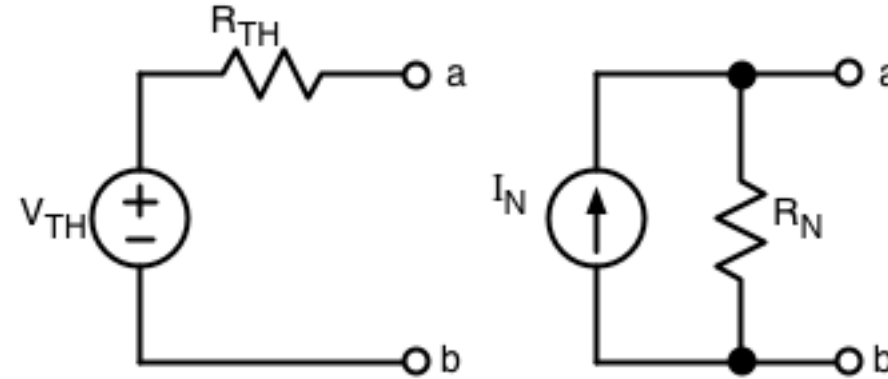1. Transform...
2. Source transform
(active equivalent transform)
3. Domain transform



Series Resistors, Voltage Division

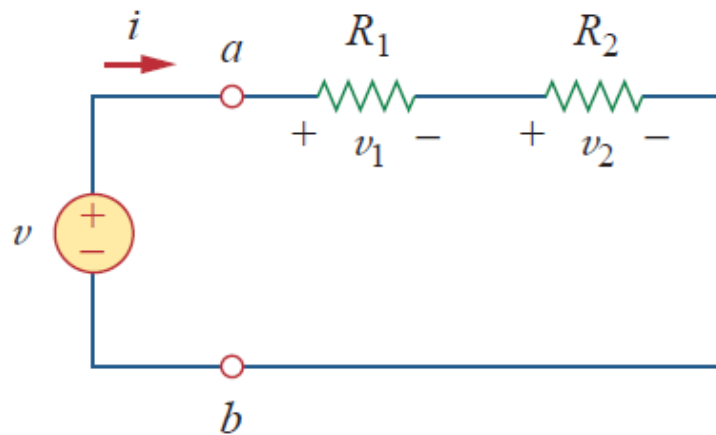


$$v_1 = i \cdot R_1, \quad v_2 = i \cdot R_2$$

$$v = v_1 + v_2 = i \cdot R_1 + i \cdot R_2 = i \cdot (R_1 + R_2)$$

$$v = i \cdot R_{eq}$$

$$R_{eq} = R_1 + R_2$$

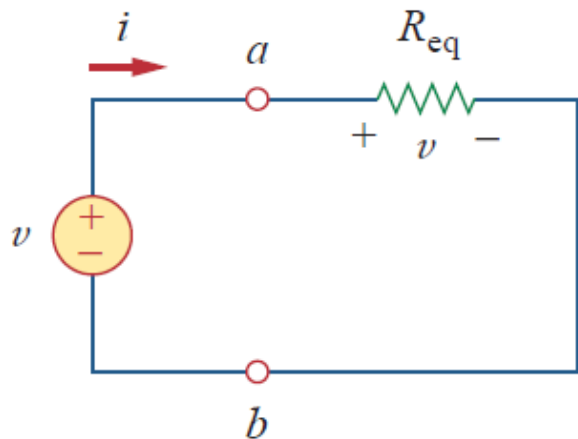

$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n$$

$$R_{eq} = R \cdot N$$

Voltage division


$$\frac{v_n}{v} = \frac{i \cdot R_n}{i \cdot R_{eq}}$$

$$v_n = v \frac{R_n}{R_1 + R_2 + \dots + R_N}$$

$$v_1 = v \frac{R_1}{R_1 + R_2}, \quad v_2 = v \frac{R_2}{R_1 + R_2}$$

$$v_{SC} = v \frac{0}{R_1 + 0} = 0, \quad v_{OC} = v \frac{\infty}{R_1 + \infty} = v$$

Parallel Resistors, Current Division

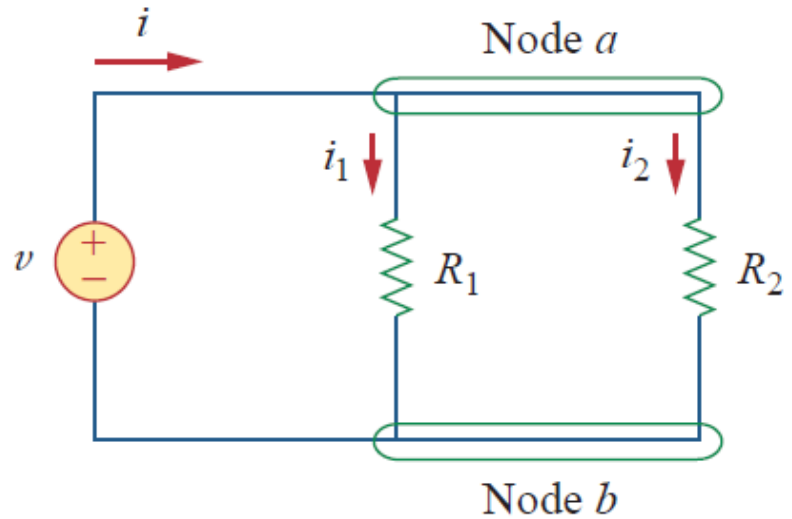


$$i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}$$

$$i = i_1 + i_2 = \frac{v}{R_1} + \frac{v}{R_2} = v \cdot \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$i = v \cdot \frac{1}{R_{eq}}$$

Current division
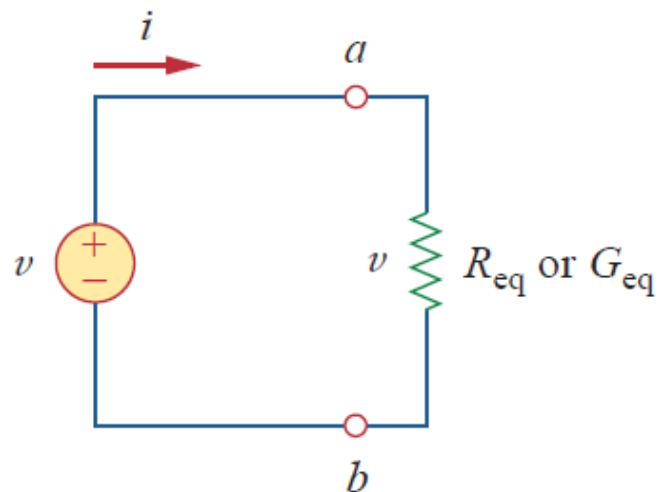
$$\frac{i_n}{i} = \frac{v \cdot G_n}{v \cdot G_{eq}}$$



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \rightarrow R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$i_n = i \cdot \frac{G_n}{G_1 + G_2 + \dots + G_N}$$


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \rightarrow G_{eq} = \sum_{n=1}^N G_n$$

$$i_1 = i \frac{R_2}{R_1 + R_2}$$


$$R_{eq} = \frac{R}{N}$$

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

Current Division in OC and SC

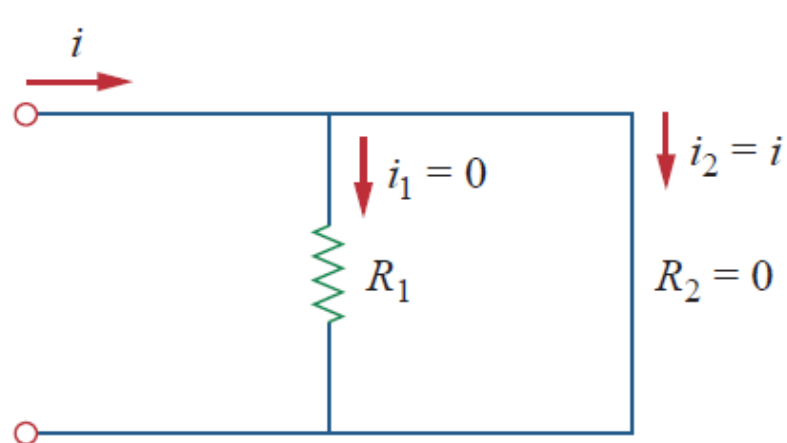

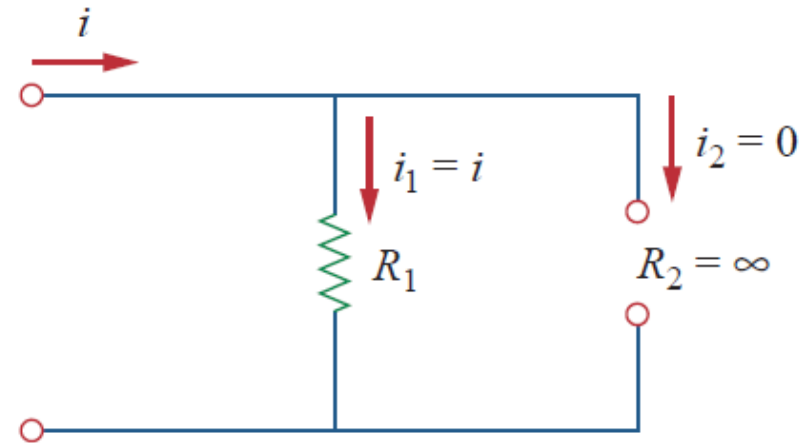
$$i_{SC} = i \frac{R_1}{R_1 + 0} = i \rightarrow i_1 = 0$$





$$i_{OC} = i \frac{R_1}{R_1 + \infty} = 0 \rightarrow i_1 = i$$

Wye-Delta Transformations

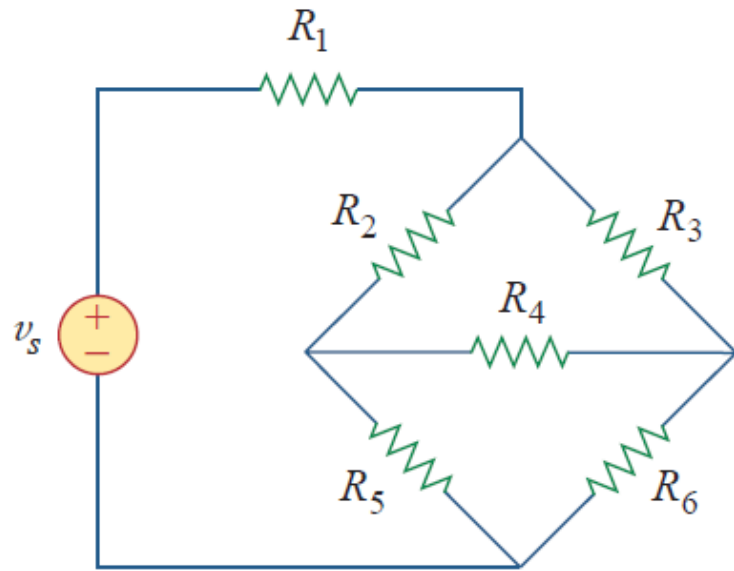


The problem - neither serial nor parallel elements

Solution - equivalent circuits

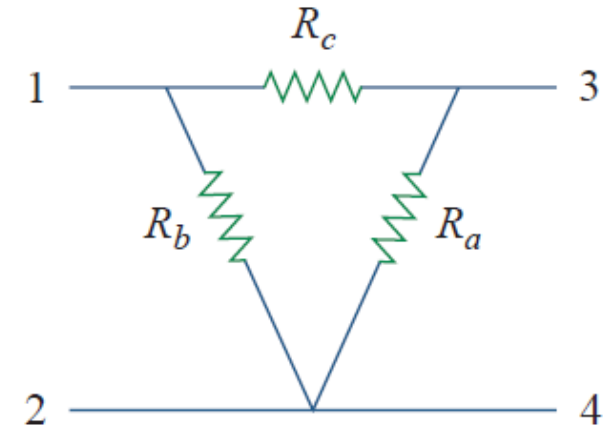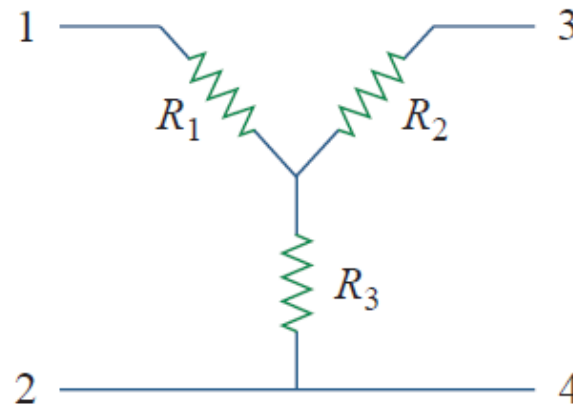

Delta to Wye Conversion

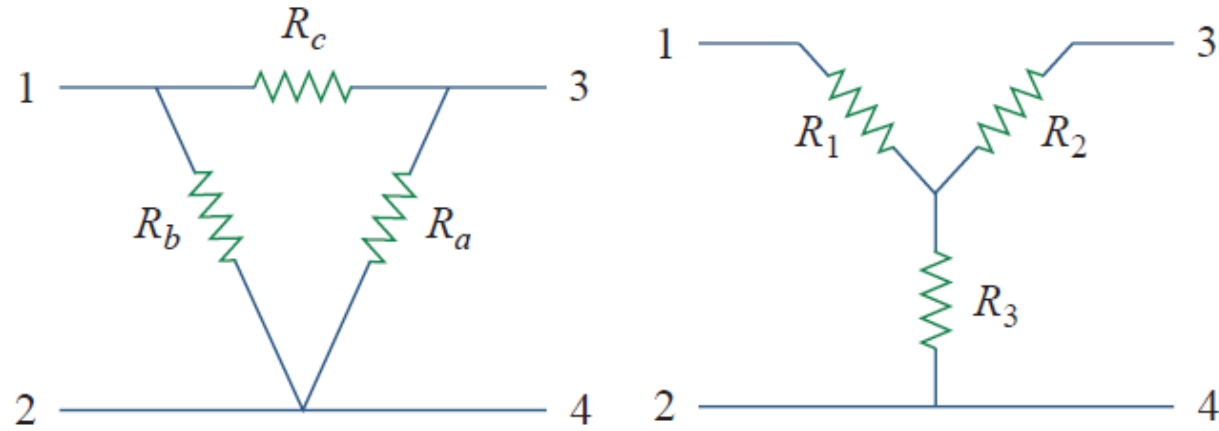

Each resistor in the wye network is the product of the resistors in the two adjacent delta branches, divided by the sum of the three delta resistors.

$$R_{12}(\Delta) = R_b \times (R_a + R_c)$$


$$R_{12}(Y) = R_1 + R_3$$

$$R_{12} = R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c}$$

$$R_{13} = R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c}$$

$$R_{34} = R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c}$$

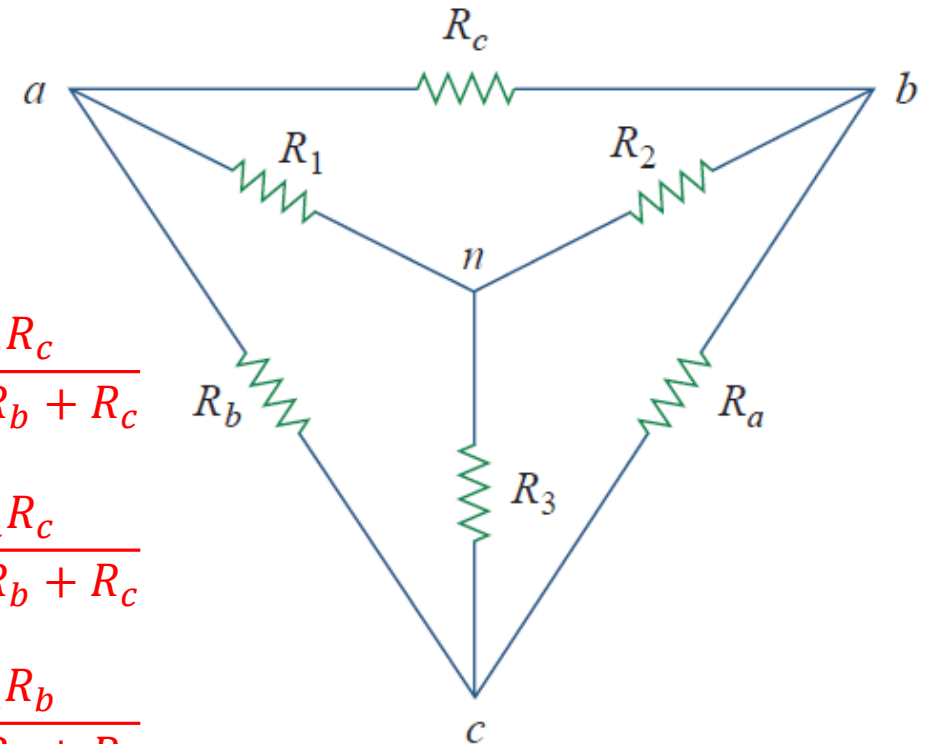
$$\left. \begin{array}{l} \\ \\ \end{array} \right\} \rightarrow \dots \rightarrow \left\{ \begin{array}{l} R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \\ R_2 = \frac{R_a R_c}{R_a + R_b + R_c} \\ R_3 = \frac{R_a R_b}{R_a + R_b + R_c} \end{array} \right.$$



Wye to Delta Conversion

$$\left. \begin{aligned} R_1 &= \frac{R_b R_c}{R_a + R_b + R_c} \\ R_2 &= \frac{R_a R_c}{R_a + R_b + R_c} \\ R_3 &= \frac{R_a R_b}{R_a + R_b + R_c} \end{aligned} \right\} \rightarrow \dots \rightarrow \left\{ \begin{aligned} R_a &= \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1} \\ R_b &= \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2} \\ R_c &= \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3} \end{aligned} \right.$$

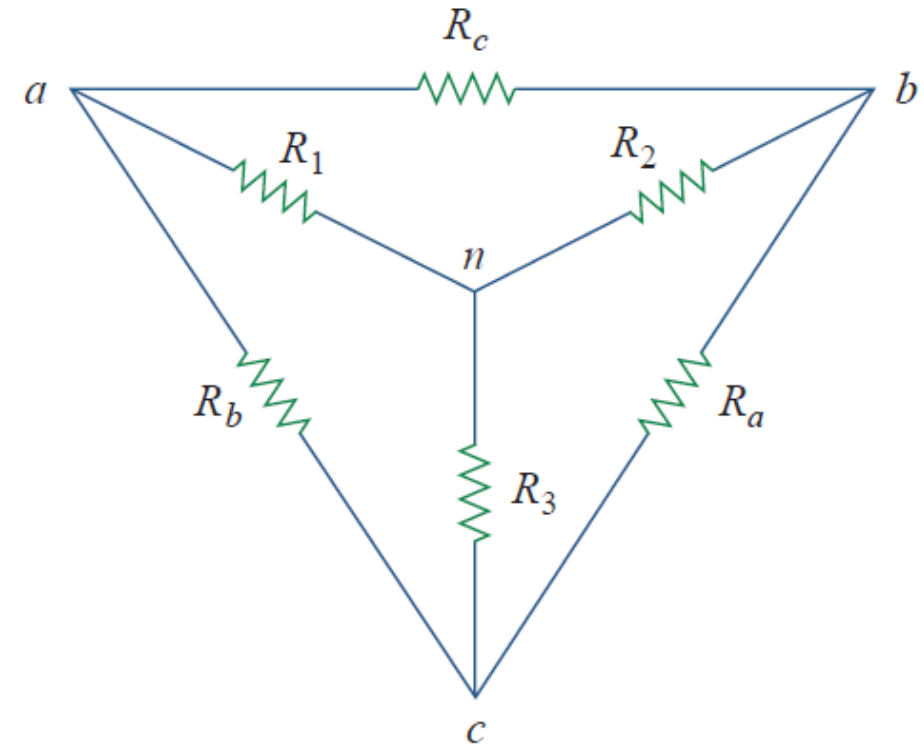Each resistor in the delta network is the sum of all possible product of Y resistors taken two at a time, divided by the opposite Y resistor.



OR ... Each conductor in the delta network is the product of the conductors in the two adjacent wye branches, divided by the sum of the three wye conductors.

$$\begin{aligned} G_a &= \frac{G_2 G_3}{G_1 + G_2 + G_3} \\ G_b &= \frac{G_1 G_3}{G_1 + G_2 + G_3} \\ G_c &= \frac{G_1 G_2}{G_1 + G_2 + G_3} \end{aligned}$$

Balanced network \rightarrow

$$R_Y = \frac{R_\Delta}{3}, \quad R_\Delta = 3 \cdot R_Y$$

Questions

