



DR. GYURCSEK ISTVÁN

Classic Electrical Measurements 4

Potentiometers and Comparators

Sources and additional materials (recommended)

- ❑ *S. Tumanski: Principles of electrical measurement, CRC Press 2006. ISBN 0-7503-1038-3*
- ❑ *Máté J.: Méréstechnika 1. PTE PMMIK, ERF-P-DD2001-HU-B-01*
- ❑ *<http://gyurcsekportal.hu/mik.html>*




- Principle of Compensation**
- DC Compensators
- AC Compensators
- Practical Examples


Electric Compensation Principle

- ❑ Neutralization of two voltages (currents, magnetic fluxes, etc.)
- ❑ Balance conditions


$$E_X = E_W$$

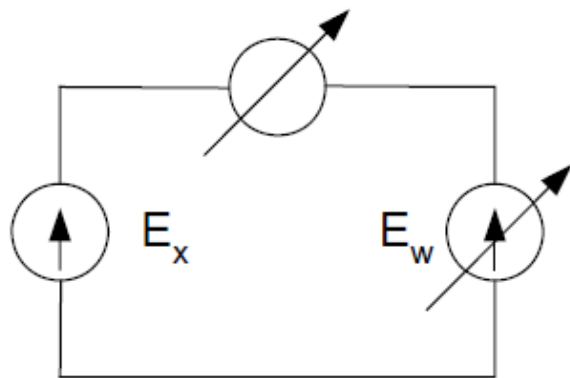

$$I_X = I_W$$

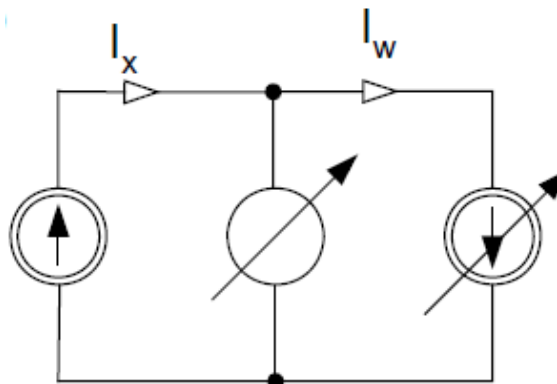


$$\Phi_X = \Phi_W$$

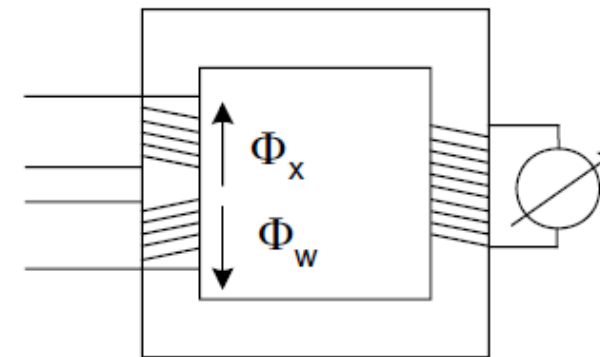

Compensation 2

Potentiometers (manual balancing)

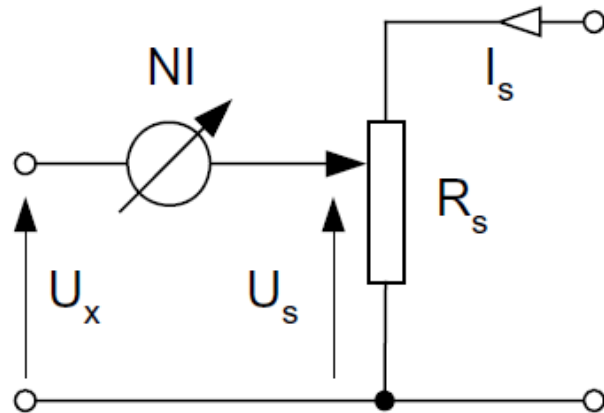- Compensation of two voltages
- For years - most accurate DEV for determ. U (directly) and I, R (indirectly)
- Nowadays - substituted by DVM (compensation principle used internal)




$$U_X = U_S = a \cdot R_S \cdot I_S$$

$$a = (0 \dots 1)$$

- Accurate measurement!
- Truly non-invasive way
- No energy from the tested source
- Infinite input impedance

Electronic feedback (automatic balancing)


$$U_X = U_S = I_{out} \cdot R_S$$

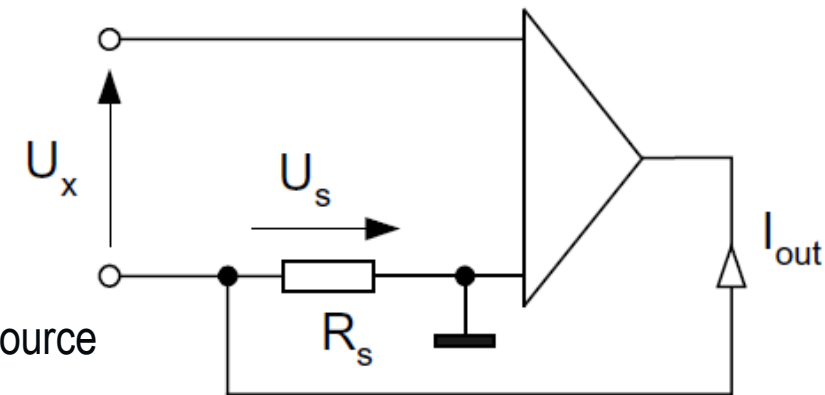




- Principle of Compensation
- DC Compensators**
- AC Compensators
- Practical Examples

Principle of operation

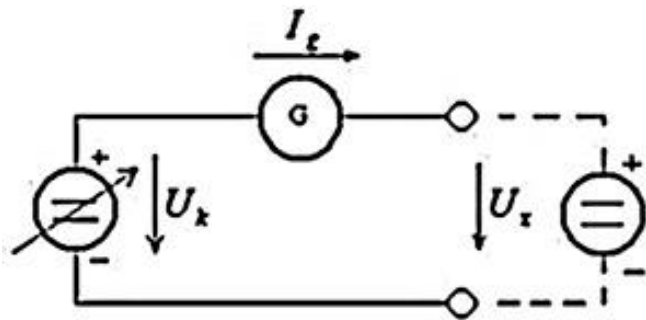

$$U_x = U_k \rightarrow I_g = 0$$


Adjustable auxiliar PWR

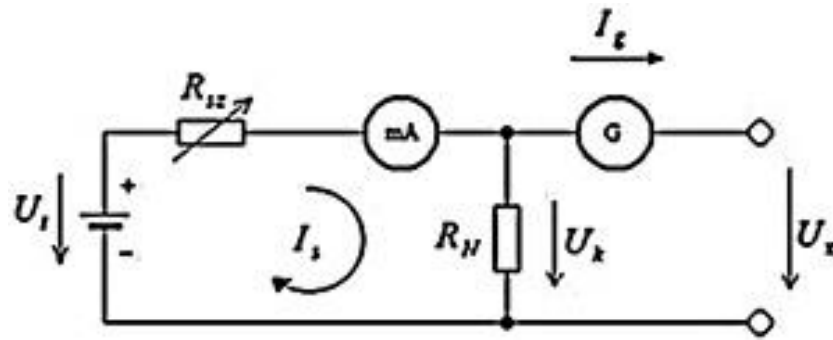

$$U_x = U_k = I_s R_N$$


DC Compensators 2

Constant auxiliar PWR

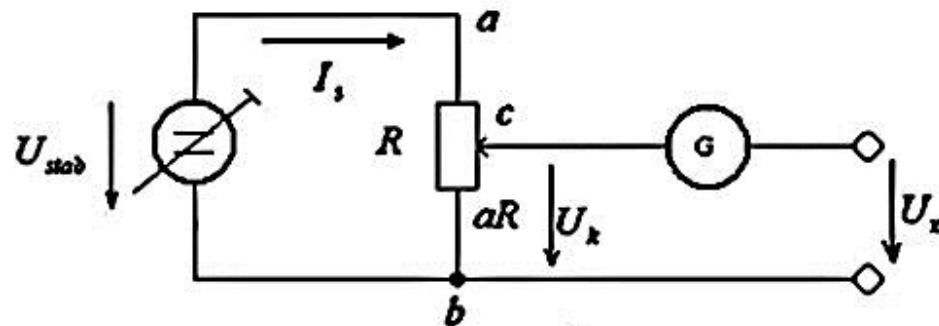

$$I_s = \frac{U_{stab}}{R} = konst.$$

Constant auxiliar PWR (modified)

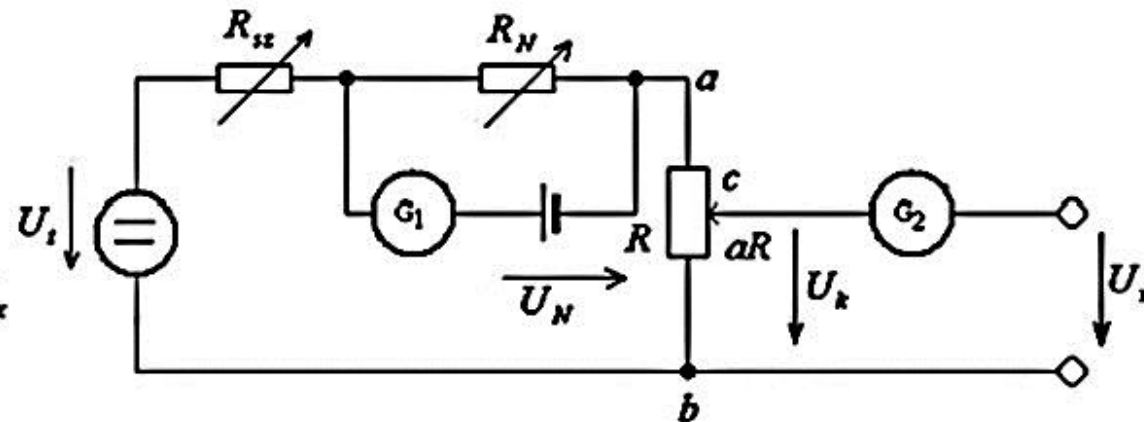

- Comp.1 - balance G_1 (U_N – Weston norm. source)

$$R_N = \frac{U_N}{I_s} = \frac{1,01865V}{1mA} = 1018,65\Omega$$

- Comp.2 - balance G_2


$$U_x = U_k, U_k = I_s aR = \frac{U_N}{R_N} aR \rightarrow U_x = \frac{U_N}{R_N} aR$$





- Principle of Compensation
- DC Compensators
- AC Compensators**
- Practical Examples

AC Compensators 1

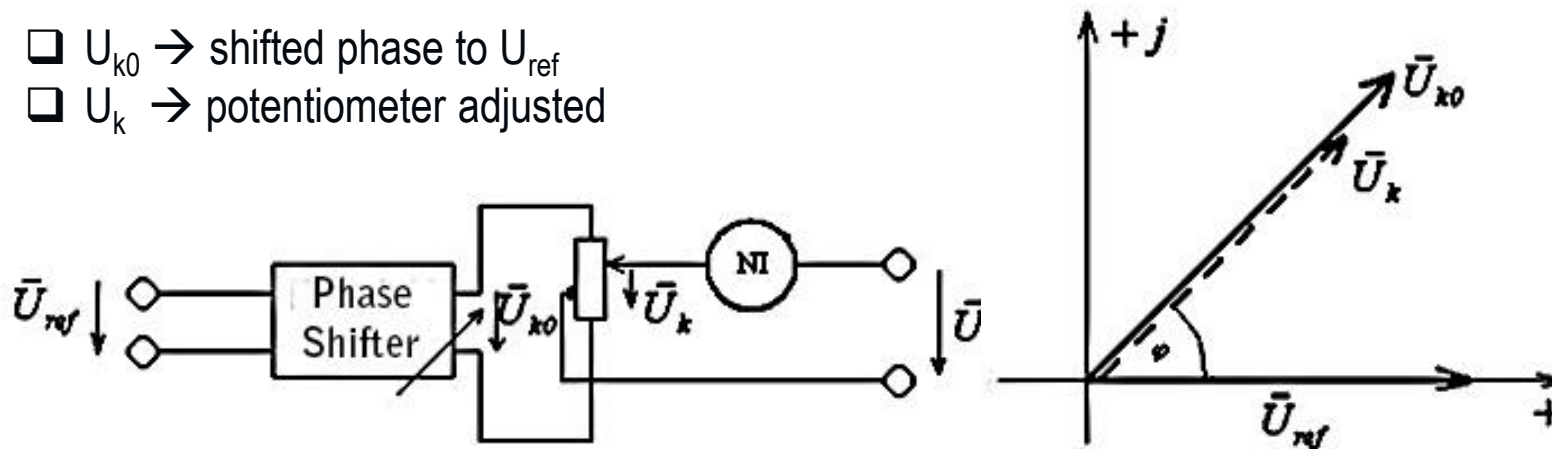- Two params → magnitude, phase (*and frequency!*)
 - *Magnitude condition*
 - *Phase condition*
- General periodic signal → balance only for base harmonic (selective NI necessary)
- U_{k0} → shifted phase to U_{ref}
- U_k → potentiometer adjusted



AC Compensators 2

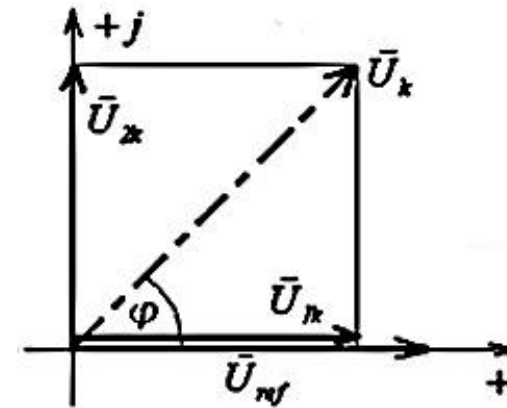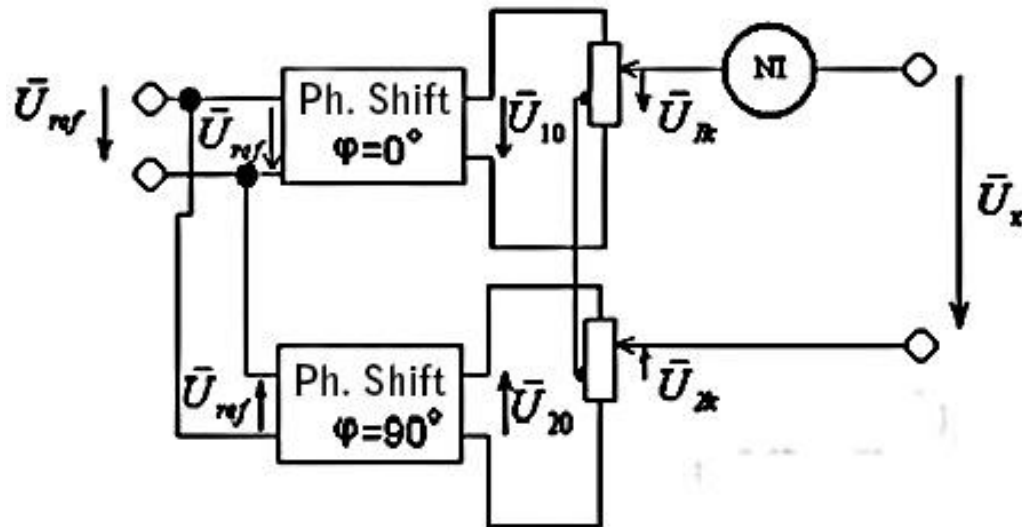

$$\bar{U}_x = \bar{U}_k = \bar{U}_{1k} + \bar{U}_{2k}$$

$$\bar{U}_{10} = \bar{U}_{ref}, \bar{U}_{20} = \bar{U}_{ref} \cdot e^{j90^\circ}$$

$$U_x = \sqrt{U_{1k}^2 + U_{2k}^2}, \varphi = \tan^{-1} \left(\frac{U_{2k}}{U_{1k}} \right)$$



- Principle of Compensation
- DC Compensators
- AC Compensators
- Practical Examples**


Compensation Example 1 – Voltage to Current Transducer

Requirement $I_{out} = f(E_X)$

Solution $E_X = I_{out} \cdot R_S$

Advantages

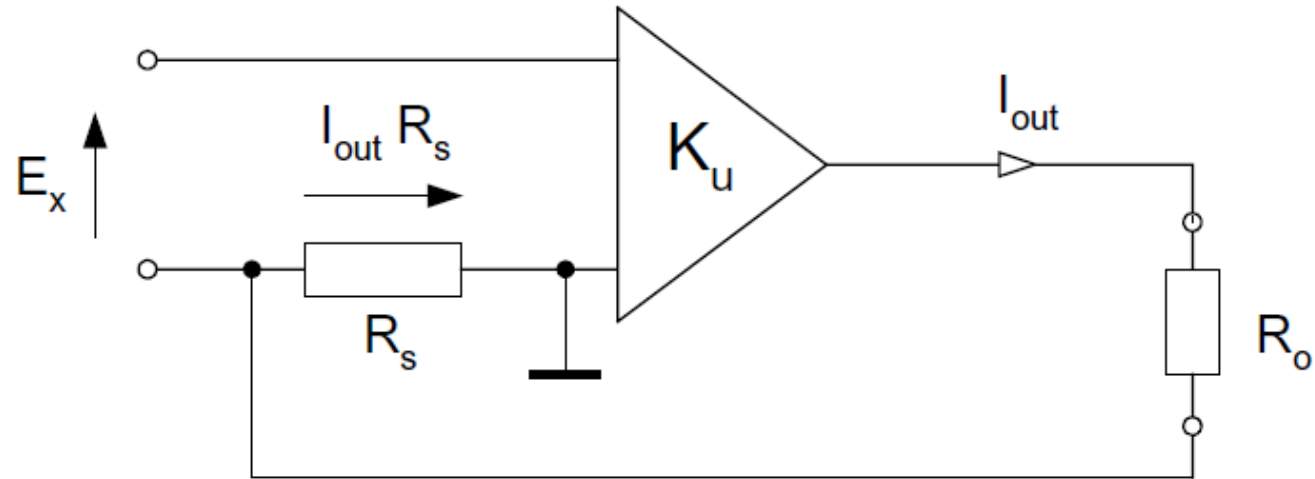- Very large input resistance
- Excellent accuracy
(depends only on standard R_S)



Compensation Example 2 – Direct Current Comparator (DCC)


Hall quantum resistance device (NIST1458 2003 - *National Institute of Standards and Technology*)

- Nobel Prize 1985
- Reconstruction of resistance standard
- Most precise method
- Excellent accuracy (no error in count of turns)
- Transformer's precondition
 - high permeability ring cores
 - with perfect symmetry
 - shielding, etc.

Auto balace $n_S I_S = n_P I_P$

Man. balance $R_S I_S = R_X I_P$


$$R_X = R_S \frac{n_P}{n_S}$$

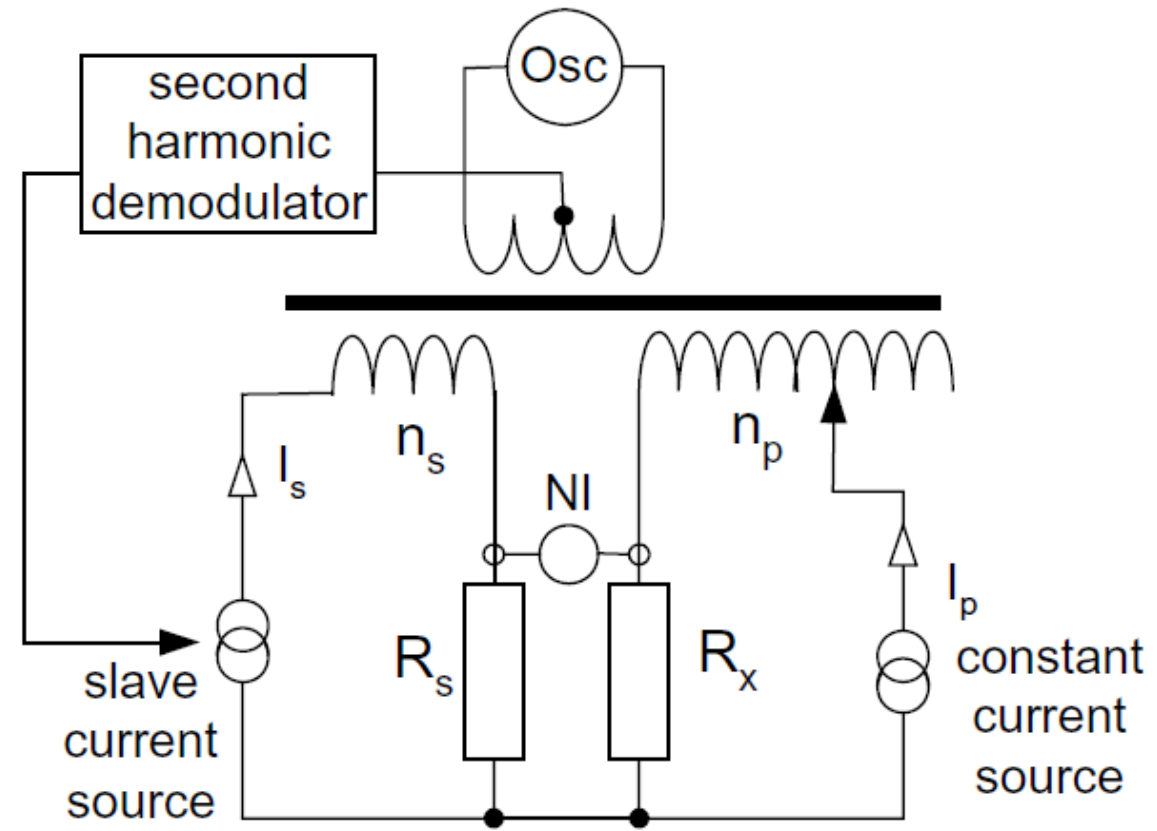

Compensation Example 3 – DC Current Comparator (DCC)

Car lighting system tester

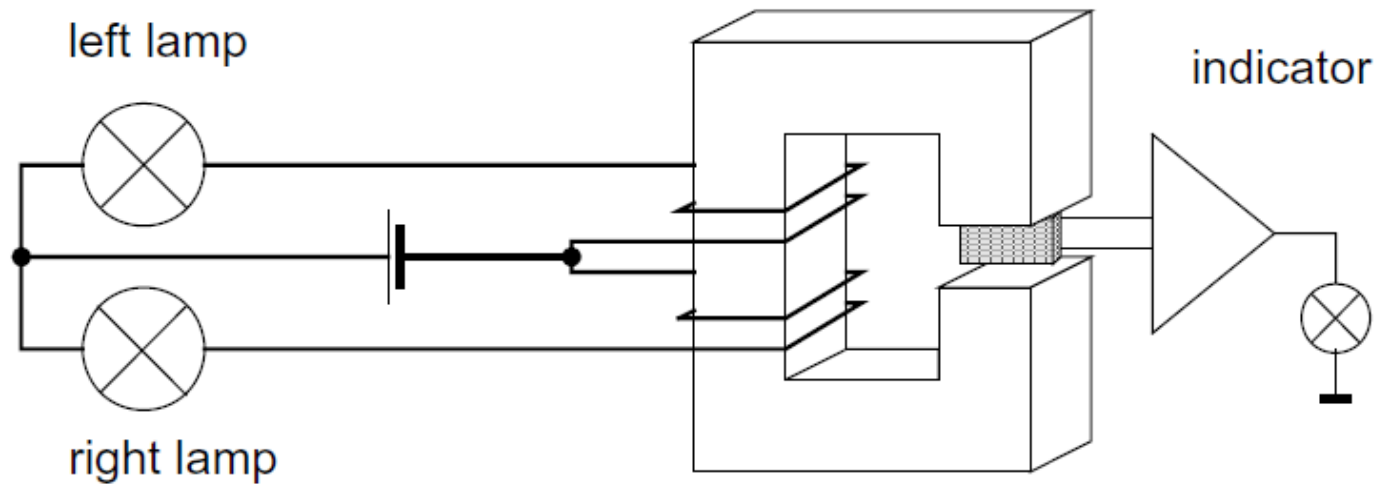- ❑ Both bulbs work \rightarrow same currents \rightarrow magnetic flux = 0
- ❑ Bulb damage \rightarrow unbalanced flux, \rightarrow magnetic field sensor



Compensation Example 4 – AC Current Comparator (ACC)


Testing current transformer (*áramváltó*)

- ❑ I_1 and I_2 are compared
(as voltage drops on the standard R_{w1} and R_{w2} .)
- ❑ Balancing in two steps
 - Magnitude condition (R_1)
 - Phase condition (C)
- ❑ Balance $\rightarrow I_0' = I_0'' \rightarrow (NI=0)$

Test result

❑ Transformation ratio
$$K_I = \frac{I_1}{I_2} = \frac{R_{w2} R_1}{R_{w1} R_2}$$

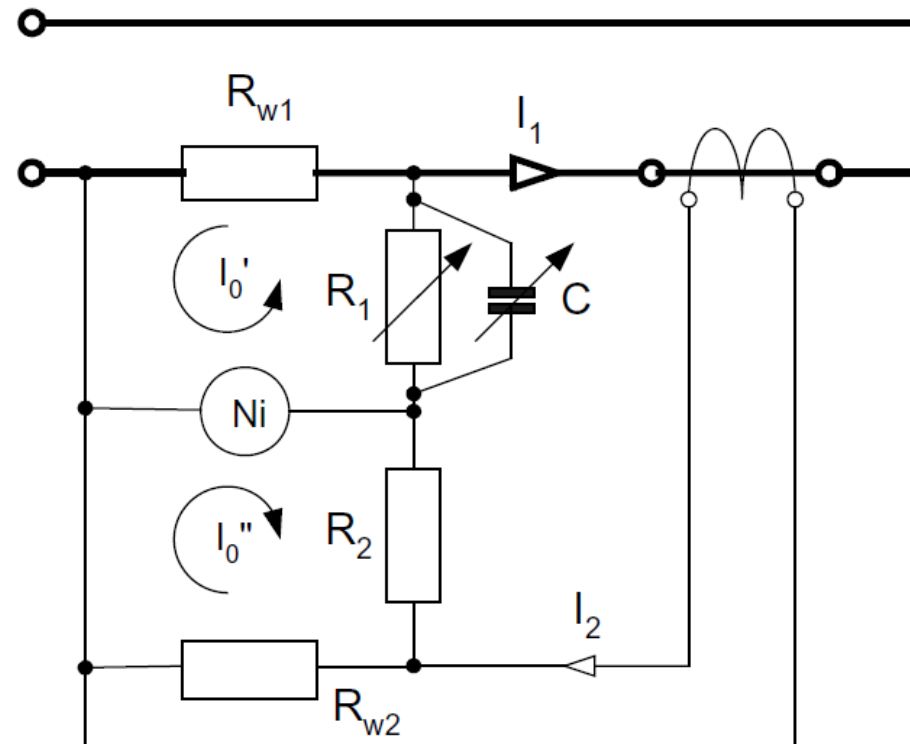❑ Angle error
$$\tan \gamma \cong \omega R_1 C$$



Compensation Example 4 – Light Comparator

- ❑ Light through two absorption cells
 - Cell.1 - standard liquid
 - Cell.2 . measured liquid
- ❑ Two photodetectors (*or one alternately*)
- ❑ Difference bw. lights → controls the movement of the wedge
(→ absorption properties of tested liquid (i.e. concentration)

