



DR. GYURCSEK ISTVÁN

Classic Electrical Measurements 4

Potentiometers and Comparators

Sources and additional materials (recommended)

- ❑ *S. Tumanski: Principles of electrical measurement, CRC Press 2006. ISBN 0-7503-1038-3*
- ❑ *Máté J.: Méréstechnika 1. PTE PMMIK, ERFP-DD2001-HU-B-01*
- ❑ *<http://gyurcsekportal.hu/mik.html>*



Principle of Compensation

- DC Compensators
- AC Compensators
- Practical Examples


Compensation 1




Electric Compensation Principle

- ❑ Neutralization of two voltages (currents, magnetic fluxes, etc.)
- ❑ Balance conditions


$$E_X = E_W$$

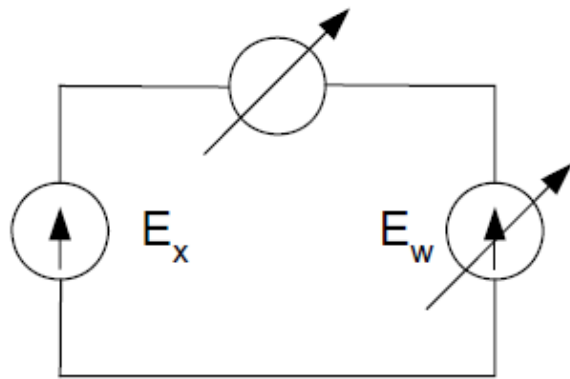


$$I_X = I_W$$

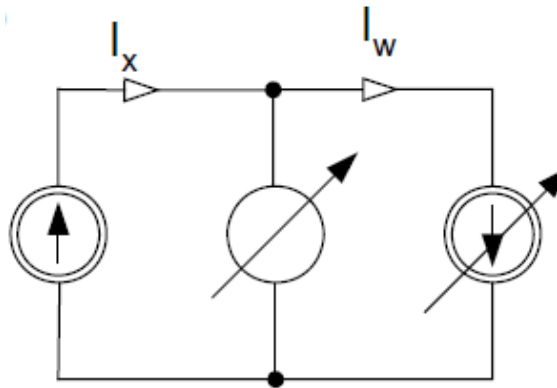

$$\Phi_X = \Phi_W$$

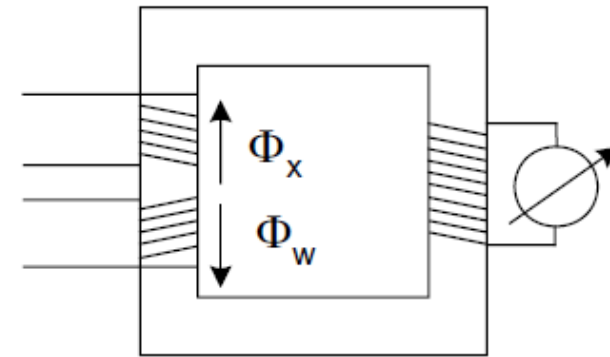


Compensation 2

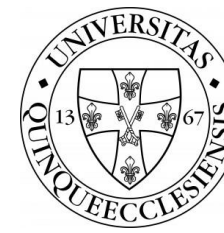

Potentiometers (manual balancing)

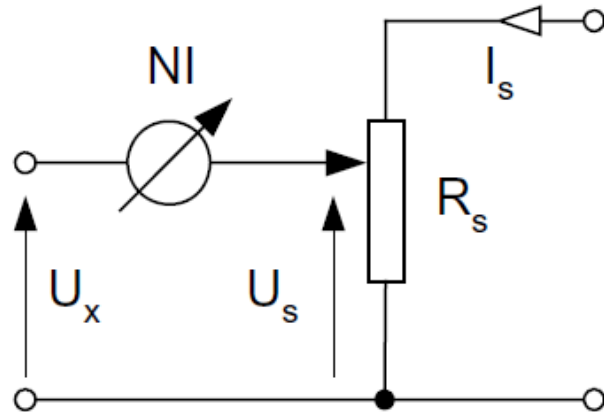- ❑ Compensation of two voltages
- ❑ For years - most accurate DEV for determ. U (directly) and I, R (indirectly)
- ❑ Nowadays - substituted by DVM (compensation principle used internal)




$$U_X = U_S = a \cdot R_S \cdot I_S$$

$$a = (0 \dots 1)$$

- ❑ Accurate measurement!
- ❑ Truly non-invasive way
- ❑ No energy from the tested source
- ❑ Infinite input impedance

Electronic feedback (automatic balancing)

$$U_X = U_S = I_{out} \cdot R_S$$

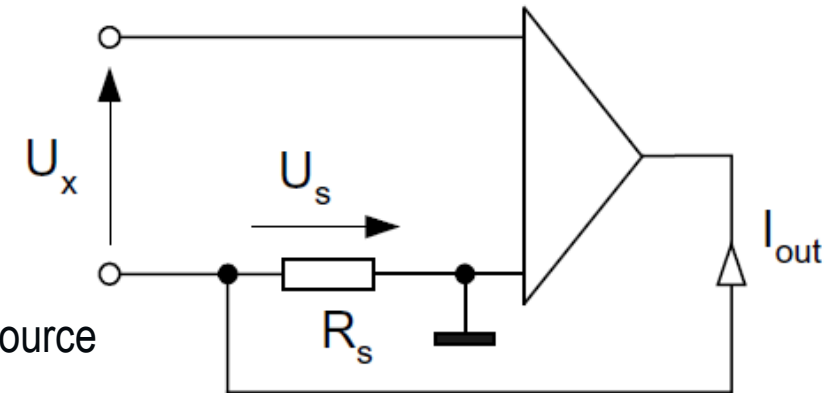




- Principle of Compensation
- DC Compensators**
- AC Compensators
- Practical Examples

DC Compensators 1




Principle of operation

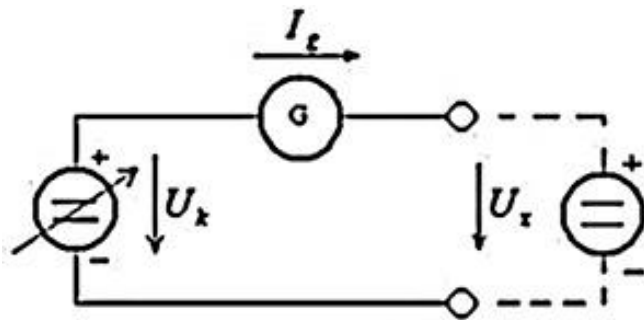

$$U_x = U_k \rightarrow I_g = 0$$

Adjustable auxiliar PWR

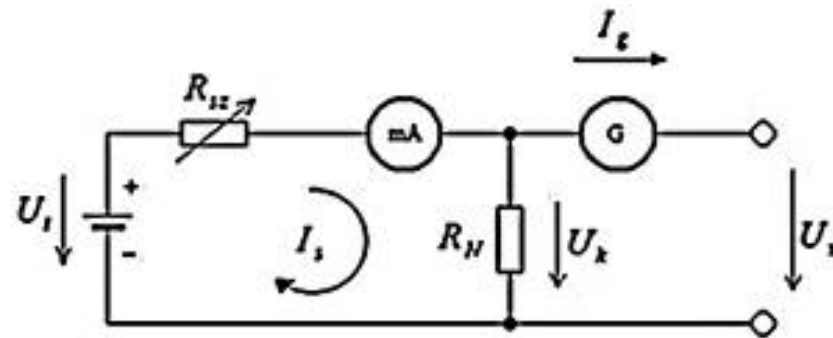


$$U_x = U_k = I_s R_N$$

DC Compensators 2




Constant auxiliar PWR

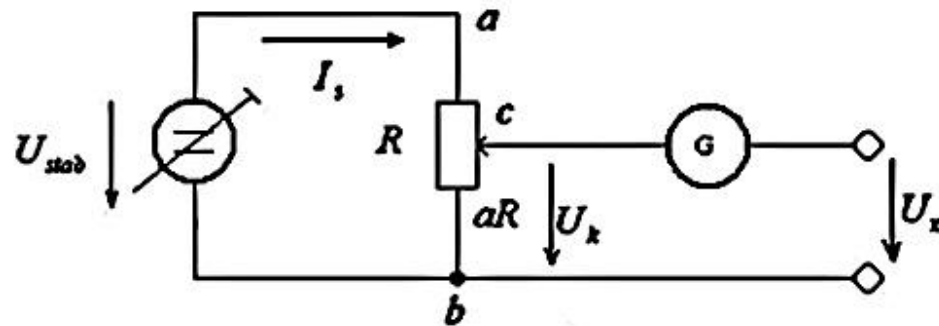

$$I_s = \frac{U_{stab}}{R} = konst.$$

Constant auxiliar PWR (modified)

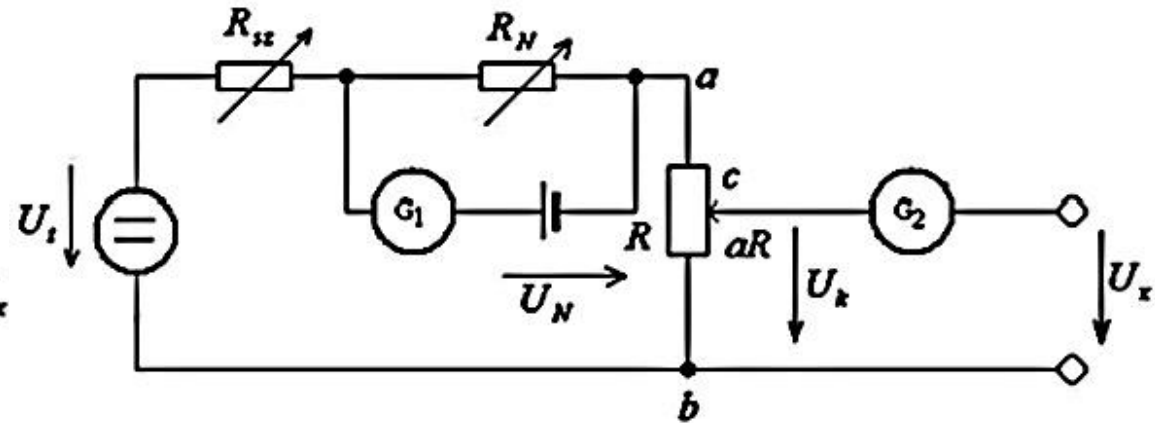

- Comp.1 - balance G_1 (U_N - Weston norm. source)

$$R_N = \frac{U_N}{I_s} = \frac{1,01865V}{1mA} = 1018,65\Omega$$


- Comp.2 - balance G_2

$$U_x = U_k, U_k = I_s aR = \frac{U_N}{R_N} aR \rightarrow U_x = \frac{U_N}{R_N} aR$$




- Principle of Compensation
- DC Compensators
- AC Compensators**
- Practical Examples

AC Compensators 1


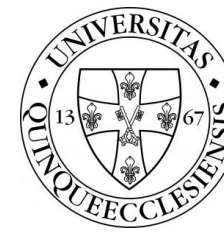


- Two params \rightarrow magnitude, phase (*and frequency!*)
 - *Magnitude condition*
 - *Phase condition*
- General periodic signal \rightarrow balance only for base harmonic (selective NI necessary)

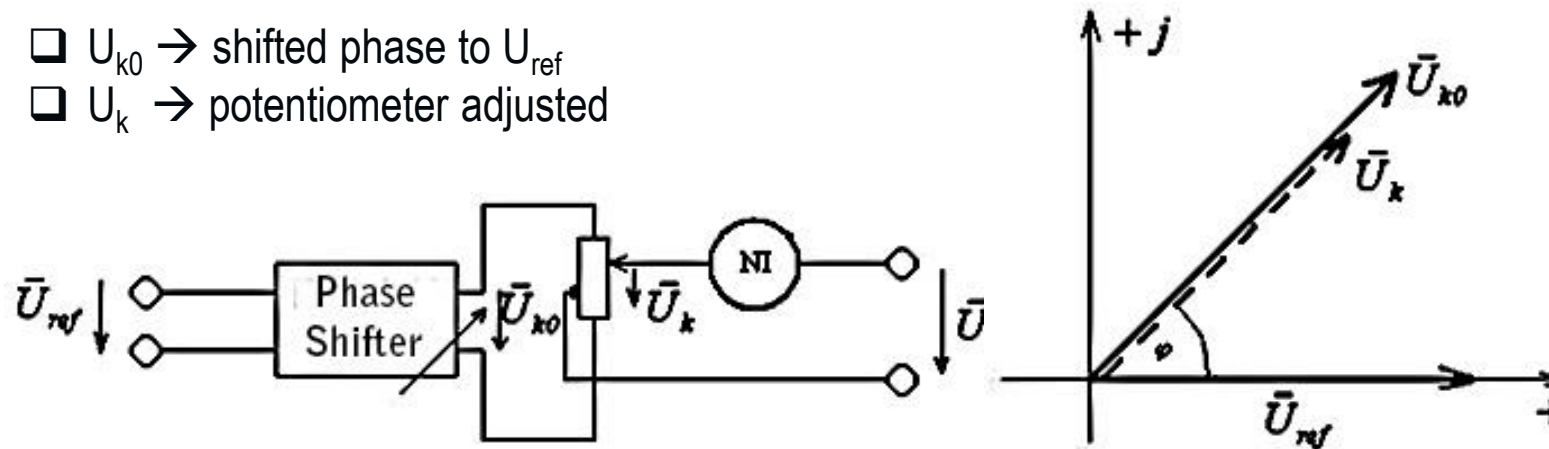- U_{k0} \rightarrow shifted phase to U_{ref}
- U_k \rightarrow potentiometer adjusted



AC Compensators 2

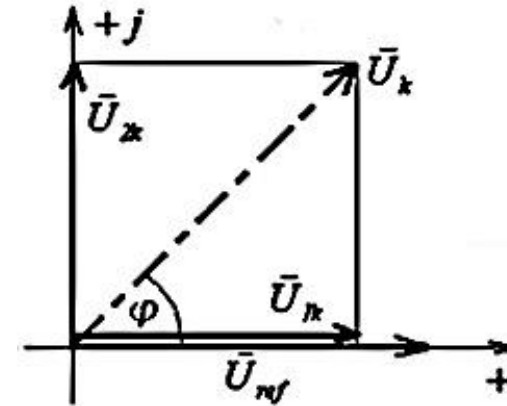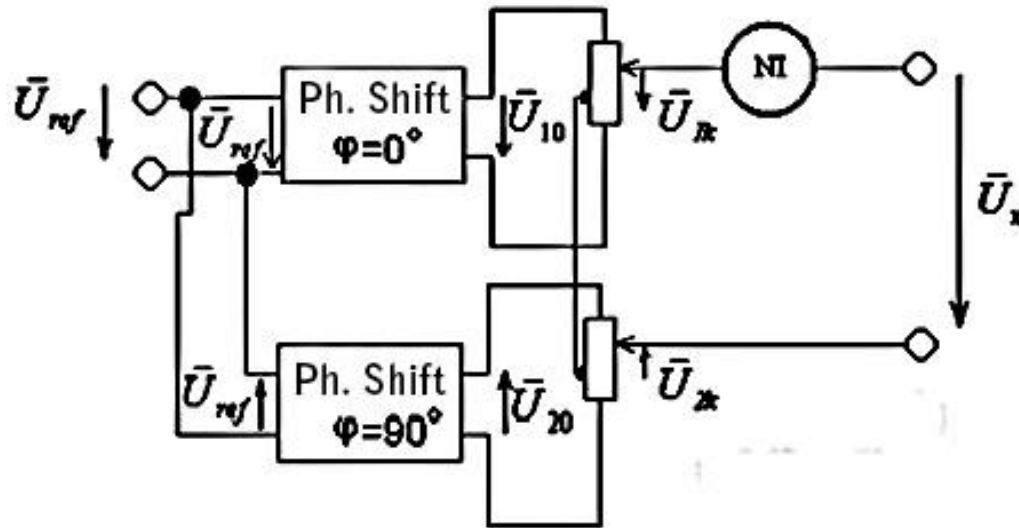

$$\overline{U}_x = \overline{U}_k = \overline{U}_{1k} + \overline{U}_{2k}$$

$$\overline{U}_{10} = \overline{U}_{ref}, \overline{U}_{20} = \overline{U}_{ref} \cdot e^{j90^\circ}$$

$$U_x = \sqrt{U_{1k}^2 + U_{2k}^2}, \varphi = \tan^{-1} \left(\frac{U_{2k}}{U_{1k}} \right)$$



- Principle of Compensation
- DC Compensators
- AC Compensators
- Practical Examples**

Example 1 - VI Transducer




Requirement $I_{out} = f(E_X)$


Solution $E_X = I_{out} \cdot R_S$

Advantages

- Very large input resistance
- Excellent accuracy
(depends only on standard R_S)

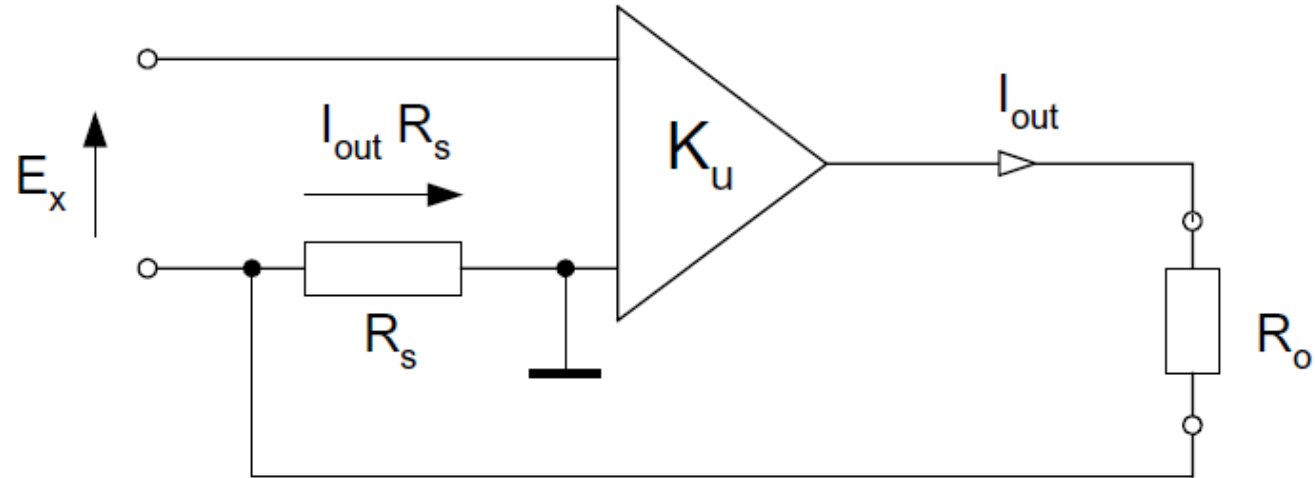

Example 2 – DCC

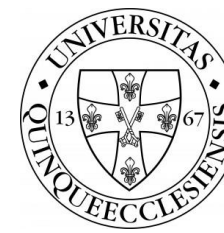

DCC = Direct Current Comparator


Hall quantum resistance device (NIST1458 2003 - *National Institute of Standards and Technology*)

- Nobel Prize 1985
- Reconstruction of resistance standard
- Most precise method
- Excellent accuracy (no error in count of turns)
- Transformer's precondition
 - high permeability ring cores
 - with perfect symmetry
 - shielding, etc.

Auto balace $n_S I_S = n_P I_P$

Man. balance $R_S I_S = R_X I_P$

$$R_X = R_S \frac{n_P}{n_S}$$

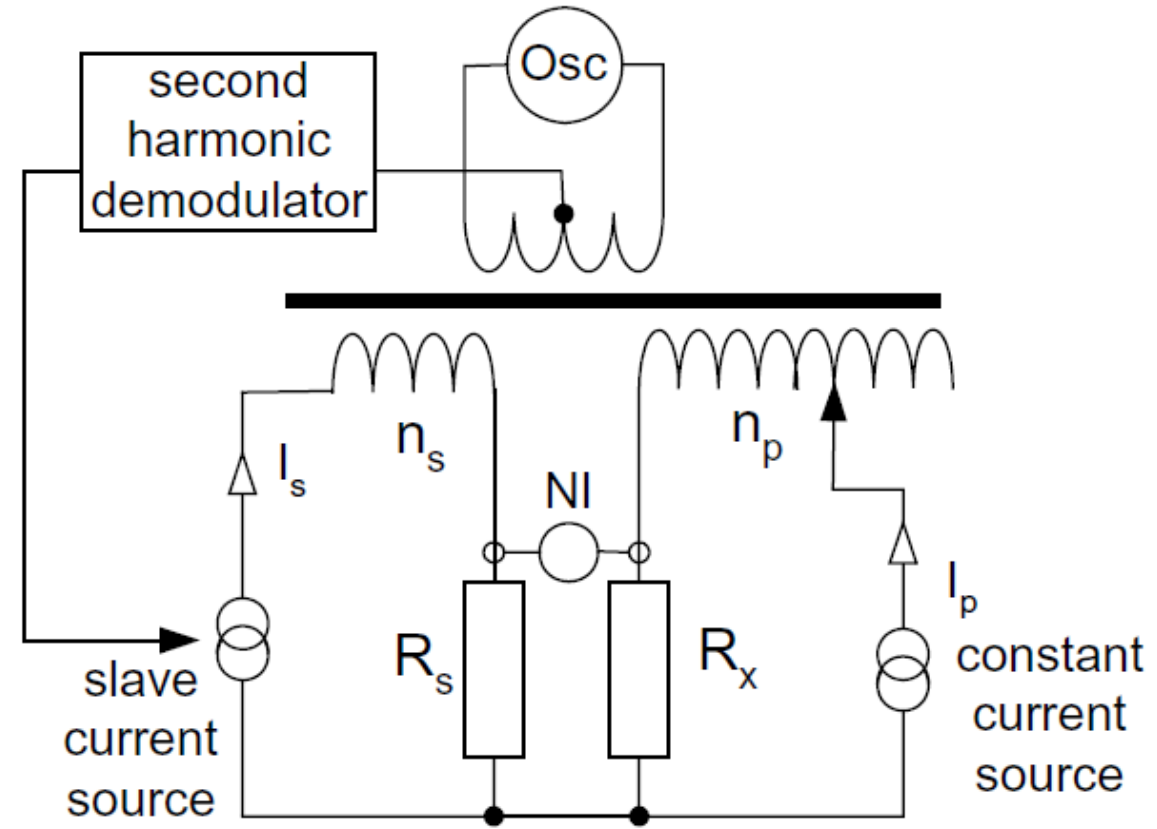


Example 3 – DCC in Car



Car lighting system tester

- ❑ Both bulbs work \rightarrow same currents \rightarrow magnetic flux = 0
- ❑ Bulb damage \rightarrow unbalanced flux, \rightarrow magnetic field sensor

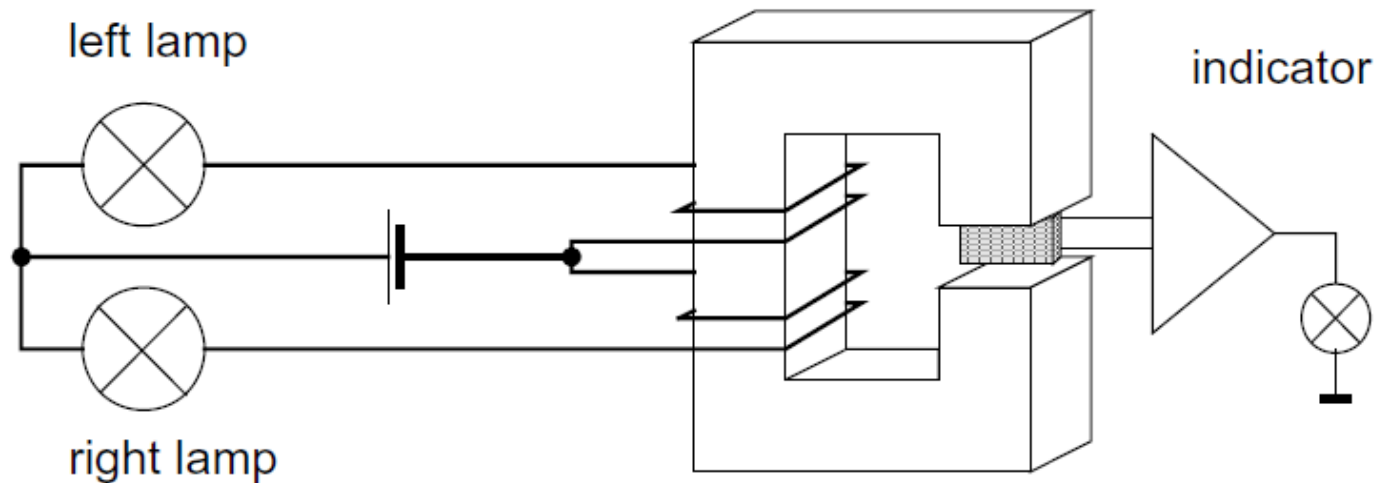

Example 4 - ACC



ACC = AC Current Comparator


Testing current transformer (*áramváltó*)

- ❑ I_1 and I_2 are compared
(as voltage drops on the standard R_{w1} and R_{w2} .)
- ❑ Balancing in two steps
 - Magnitude condition (R_1)
 - Phase condition (C)
- ❑ Balance $\rightarrow I_0' = I_0'' \rightarrow (NI=0)$

Test result

- ❑ Transformation ratio $K_I = \frac{I_1}{I_2} = \frac{R_{w2}R_1}{R_{w1}R_2}$



- ❑ Angle error $\tan \gamma \cong \omega R_1 C$

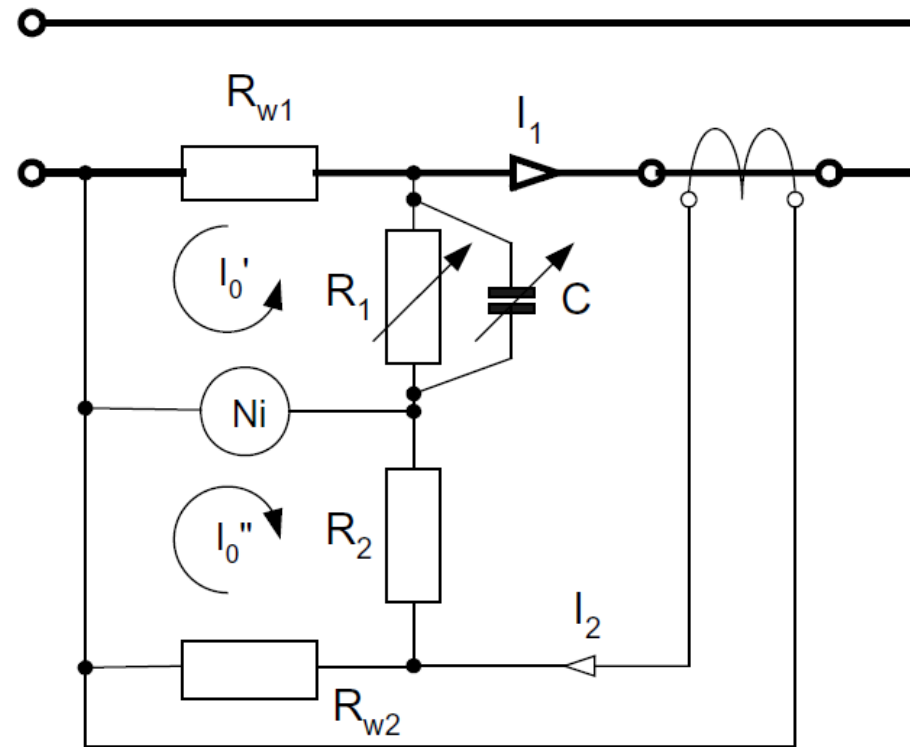

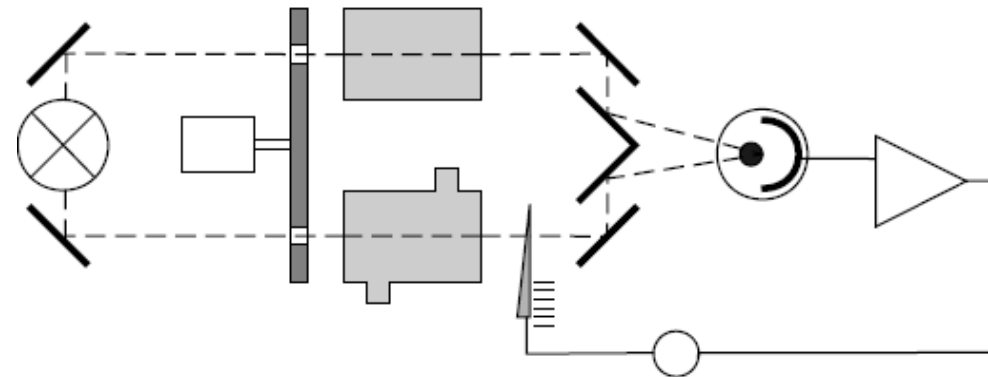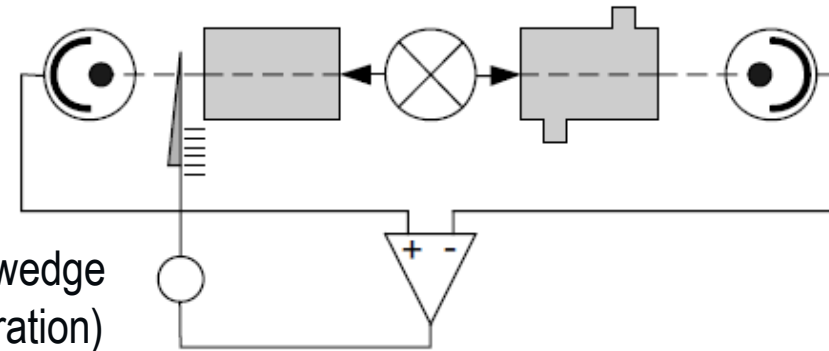Example 4 - Light Comparator



- ❑ Light through two absorption cells
 - Cell.1 - standard liquid
 - Cell.2 . measured liquid
- ❑ Two photodetectors (*or one alternately*)
- ❑ Difference bw. lights → controls the movement of the wedge
(→ absorption properties of tested liquid (i.e. concentration)



Questions

