



DR. GYURCSEK ISTVÁN

# Sinusoids and Phasors

## *Sources and additional materials (recommended)*

- ❑ *Dr. Gyurcsek – Dr. Elmer: Theories in Electric Circuits, GlobeEdit, 2016, ISBN:978-3-330-71341-3*
- ❑ *Ch. Alexander, M. Sadiku: Fundamentals of Electric Circuits, 6th Ed., McGraw Hill NY 2016, ISBN: 978-0078028229*
- ❑ *Simonyi K.: Villamosságtan. AK Budapest 1983, ISBN:9630534134*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságtan 1. MK Budapest 2002, TK szám: 49203/I*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságtan 2. TK Budapest 2002, ISBN:9631026043*
- ❑ *Zombory L.: Elektromágneses terek. MK Budapest 2006, ([www.electro.uni-miskolc.hu](http://www.electro.uni-miskolc.hu))*



- Sinusoids and Phasors**
- Circuit Elements in the Phasor Domain
- Kirchhoff's Laws in the Phasor Domain
- Application Example – Phase Shifters

# Sinusoids 1



(Homework: overview the math. functions)

Periodic function  $v(t) = v(t + nT)$

□  $\rightarrow$  all  $t$ ,  $\rightarrow$  all integers  $n$

$$v(t) = V_m \sin \omega t = V_m \sin\{\omega(t + nT)\}$$



□ Amplitude  $\rightarrow V_m$  (V)

□ Argument  $\rightarrow \omega t$  (rad)

□ Angular frequency  $\rightarrow \omega$  (rad/s)

$$\omega T = 2\pi \quad f = \frac{1}{T} \rightarrow \omega = 2\pi f$$
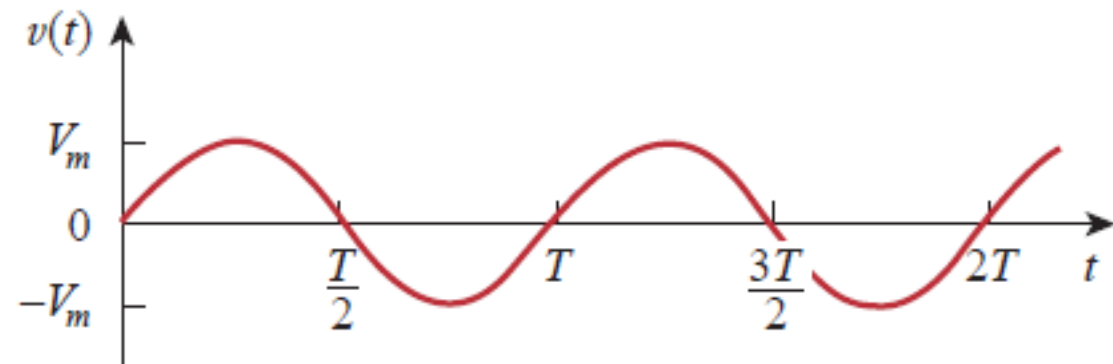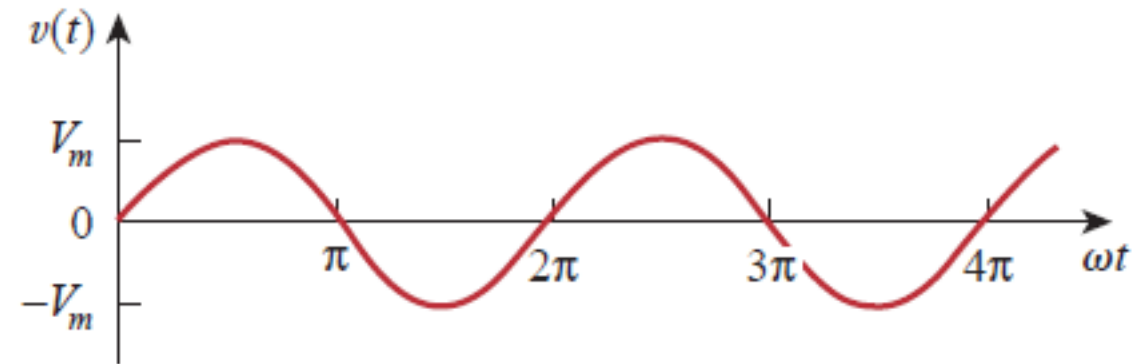
$$\left( \text{wave propagation} \rightarrow \lambda = c \cdot T = \frac{c}{f} \right)$$



## Sinusoids 2

### General expression for sinusoid

$$v(t) = V_m \sin(\omega t + \phi)$$

Argument  $\rightarrow \omega t + \phi$

$v_2$  leads  $v_1$  by  $\phi$

Same (sin or cos) forms  $\rightarrow$  in calculations

$$\sin(\alpha \pm \beta) = \sin \alpha \cos \beta \pm \cos \alpha \sin \beta$$


$$\cos(\alpha \pm \beta) = \cos \alpha \cos \beta \mp \sin \alpha \sin \beta$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

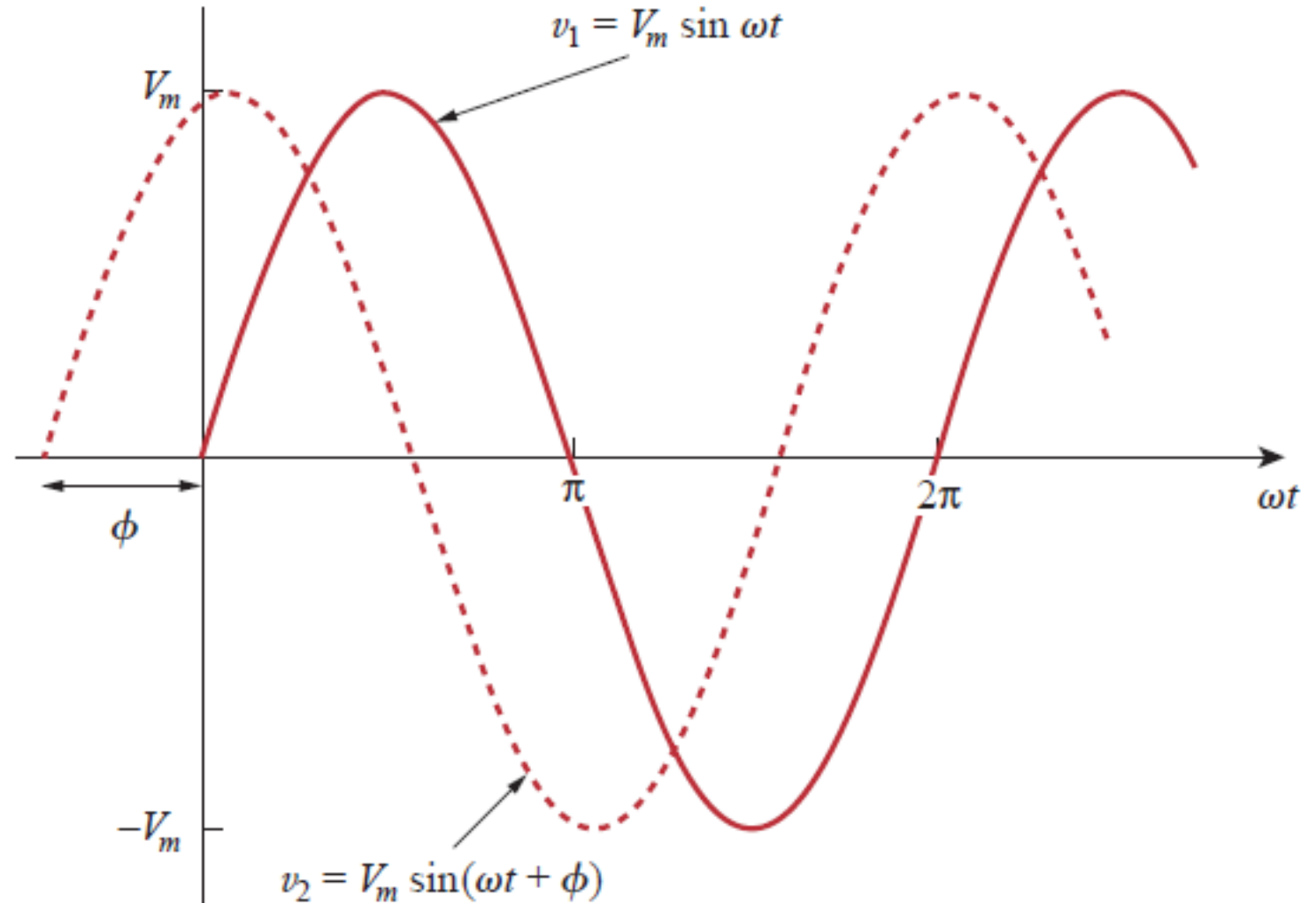
$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$


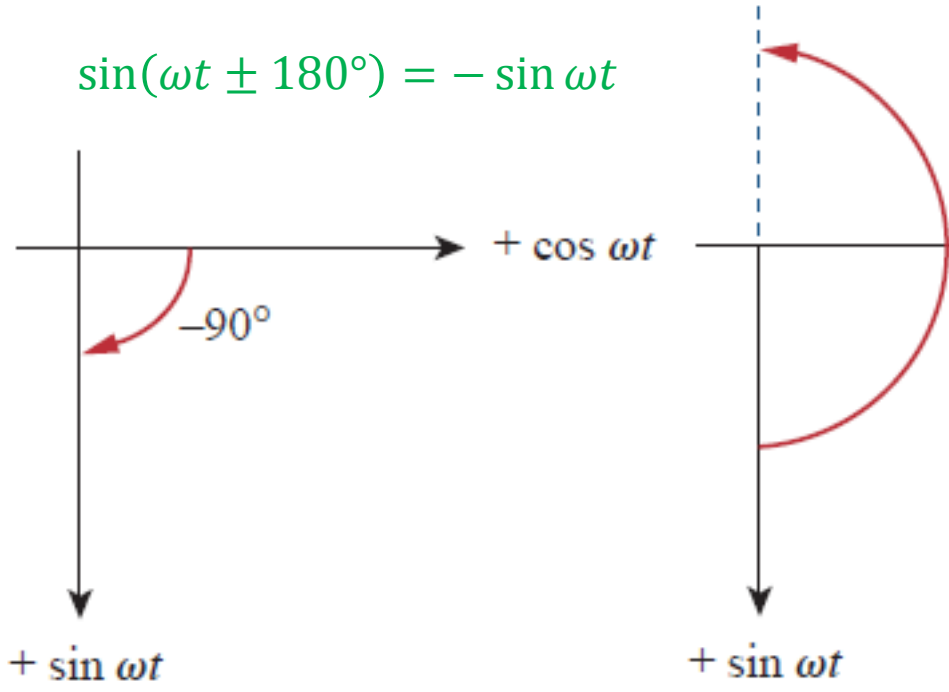
# Sinusoids 3 – Graphical Representation


$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$



$$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \Theta)$$
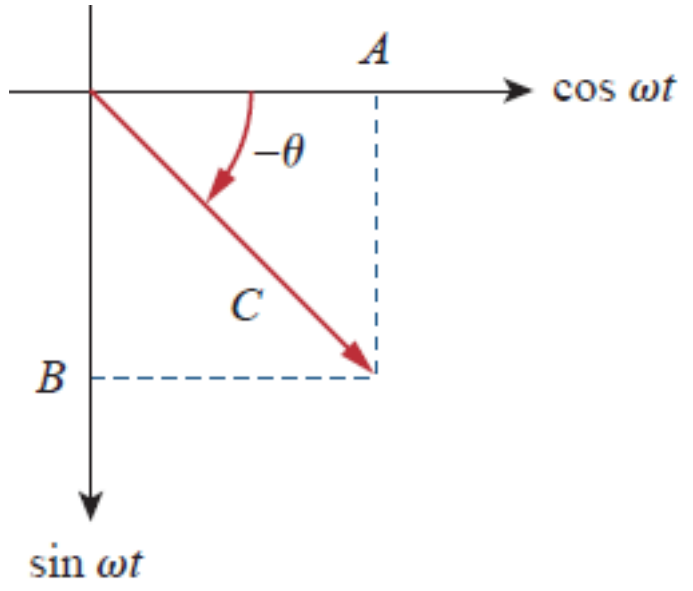
$$C = \sqrt{A^2 + B^2}, \quad \Theta = \tan^{-1} \frac{B}{A}$$




# Phasors 1

- ❑ Phasor  $\rightarrow$  complex number ... representing amplitude and phase of a sinusoid
- ❑ Suppressing time factor  $\rightarrow$  transforming sinusoid from time domain to phasor domain.

*rectangular*  $\rightarrow x + j \cdot y$   
*polar*  $\rightarrow r \cdot e^{j\varphi}, (r/\varphi)$

$$j = \sqrt{-1} \quad z = x + j \cdot y = r \cdot (\cos \varphi + j \cdot \sin \varphi) = r \cdot e^{j\varphi}$$
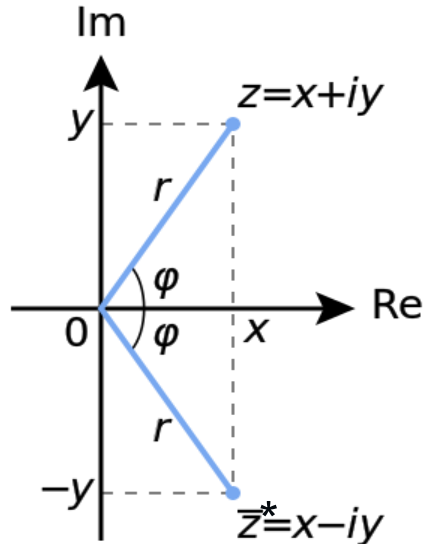
$$e^{j\varphi} = \cos \varphi + j \cdot \sin \varphi \leftarrow \text{Euler's identity}$$



$$r = \sqrt{x^2 + y^2}, \quad \varphi = \tan^{-1} \frac{y}{x}$$

$$x = r \cdot \cos \varphi, \quad y = r \cdot \sin \varphi$$

$$\cos \varphi = \frac{e^{j\varphi} + e^{-j\varphi}}{2}$$

$$\sin \varphi = \frac{e^{j\varphi} - e^{-j\varphi}}{j \cdot 2}$$

## Calculations

$$z_1 = x_1 + j \cdot y_1, \quad z_2 = x_2 + j \cdot y_2$$

$$z_1 + z_2 = (x_1 + x_2) + j \cdot (y_1 + y_2)$$

$$z_1 \cdot z_2 = r_1 \cdot r_2 \cdot e^{j(\varphi_1 + \varphi_2)}$$


$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \cdot e^{j(\varphi_1 - \varphi_2)}$$

$$z^* = x - j \cdot y = r \cdot e^{-j\varphi}$$

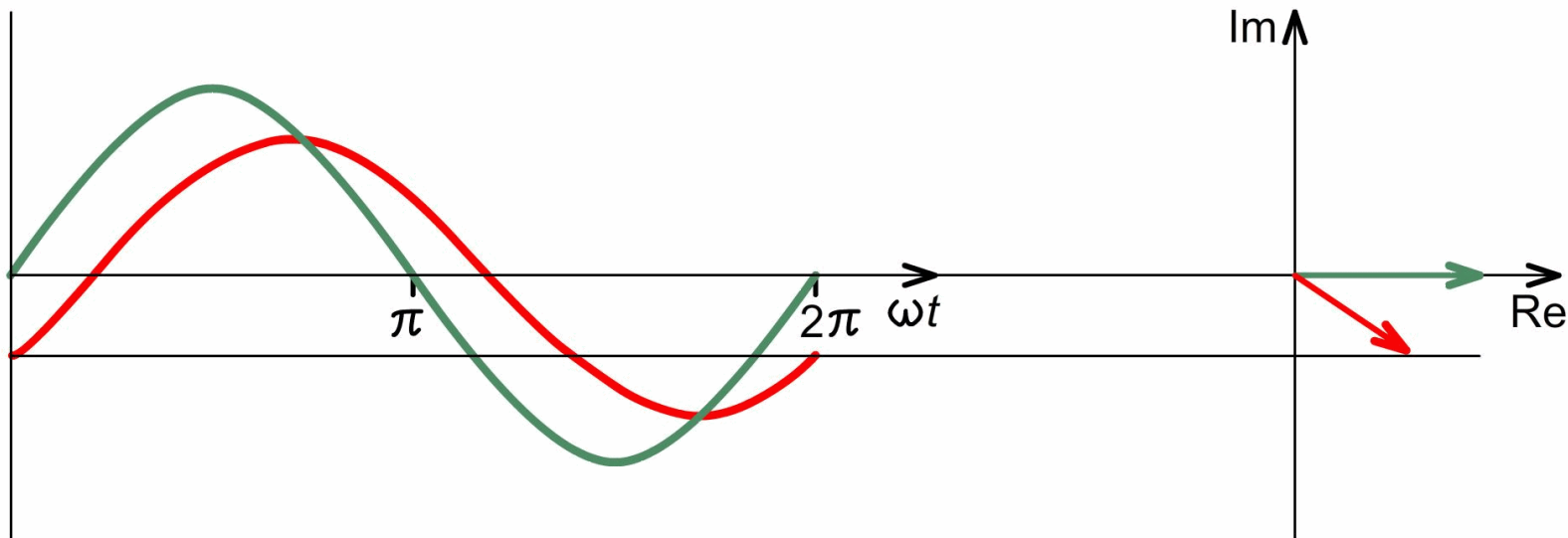
## Phasors 2

$$v(t) = V_m \cos(\omega t + \varphi) \xrightarrow{\text{transf.}} v(t) = V_m [\cos(\omega t + \varphi) + j \sin(\omega t + \varphi)]$$


(time dept. cpx. function)  $v(t) = V_m e^{j(\omega t + \varphi)} = V_m e^{j\varphi} e^{j\omega t}$


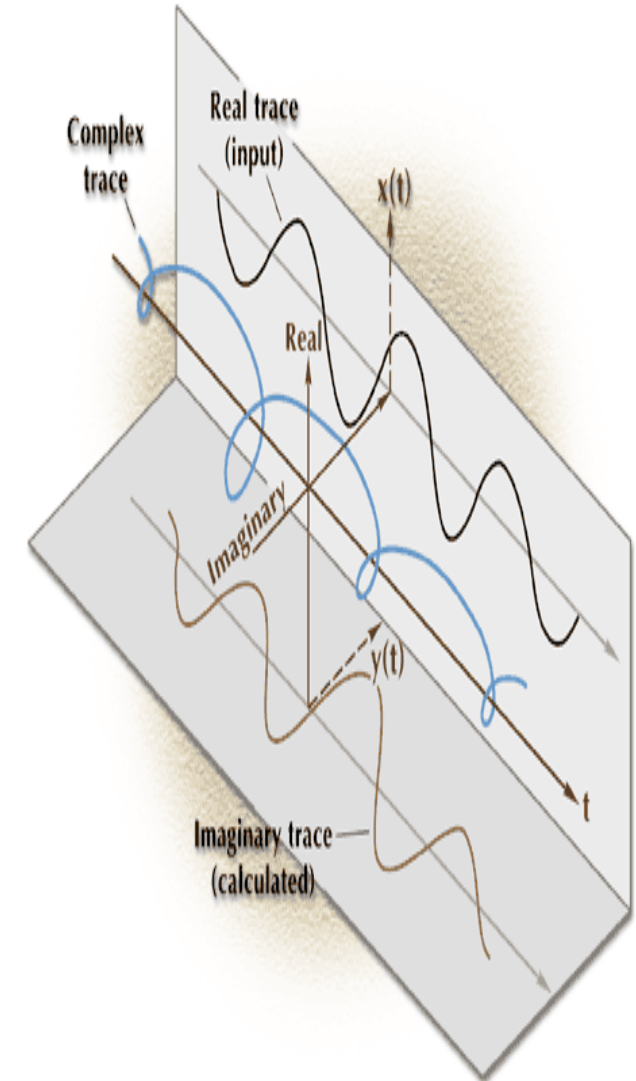
$$v(t) = \text{Re} \{v(t)\} \quad \text{PHASOR (suppressing time factor)} \rightarrow V_m = V_m e^{j\varphi}$$



## Phasor 3 (illustration)

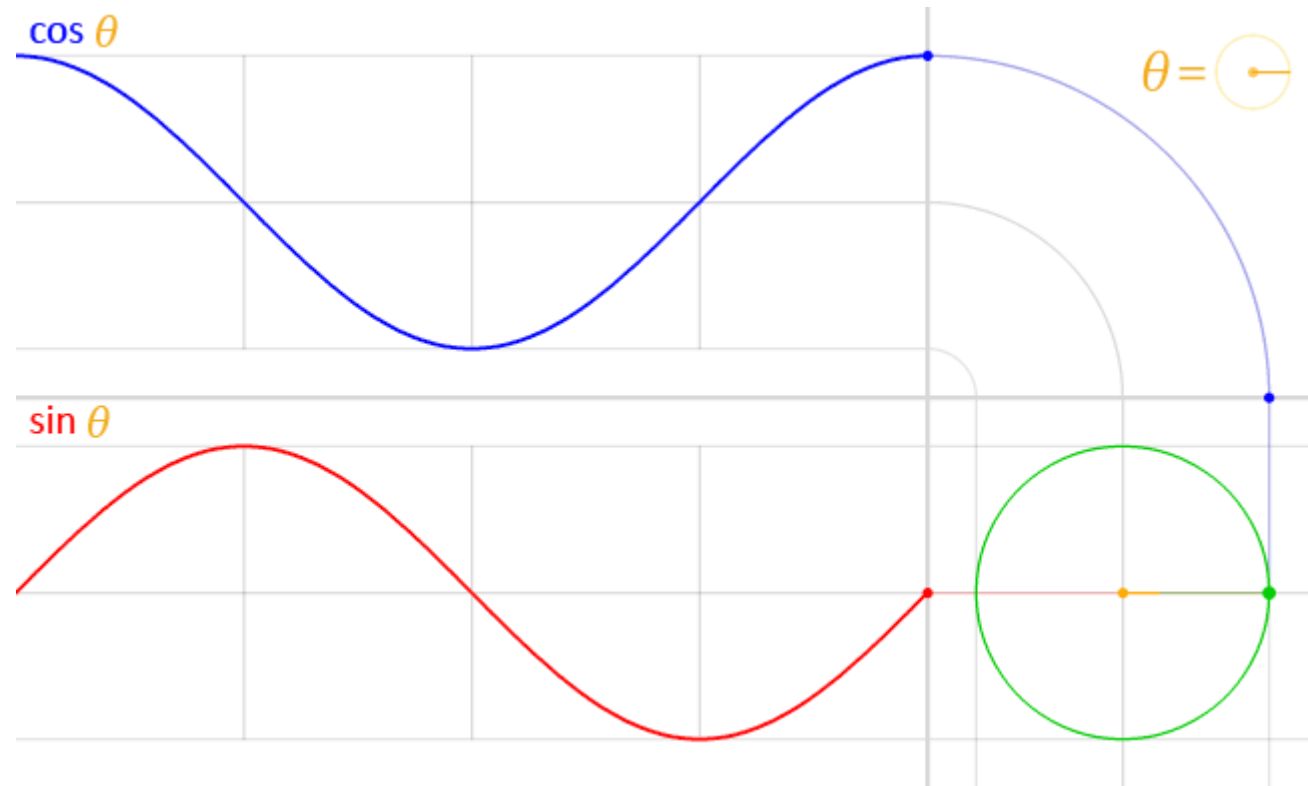



## Transform (time domain $\rightarrow$ phasor domain)

$$v = V_m \cos(\omega t + \varphi) \rightarrow \frac{dv}{dt} =? \rightarrow \frac{dv}{dt} = -\omega V_m \sin(\omega t + \varphi)$$

$$= \omega V_m \cos(\omega t + \varphi + 90^\circ) = \operatorname{Re} \{ \omega V_m e^{j\omega t} e^{j\varphi} e^{j90^\circ} \}$$

$$= \operatorname{Re} \{ j\omega \mathbf{V} e^{j\omega t} \}$$

Time domain	Phasor domain
$v(t) = V_m \cos(\omega t + \varphi)$	$\mathbf{V} = V_m e^{j\varphi}$
$\frac{dv(t)}{dt}$	$j\omega \mathbf{V}$
$\int v(t) \cdot dt$	$\frac{1}{j\omega} \mathbf{V}$

### COMMENTS

- Complex number  $\rightarrow$  scalar! (,normal' z)
- Phasor  $\rightarrow$  ,vector-like' behavior (,bold'  $\mathbf{V}$ )

### CONDITION!

Phasor analysis  $\rightarrow$  frequency is the same

### Properties of , $v(t)$ '

- Instantaneous or time domain represent.
- Time dependent
- Always real



### Properties of , $\mathbf{V}$ '

- Frequency or phasor domain represent.
- Time independent
- Generally complex



- Sinusoids and Phasors
- Circuit Elements in the Phasor Domain**
- Kirchhoff's Laws in the Phasor Domain
- Application Example – Phase Shifters



# Resistor in the Phasor Domain

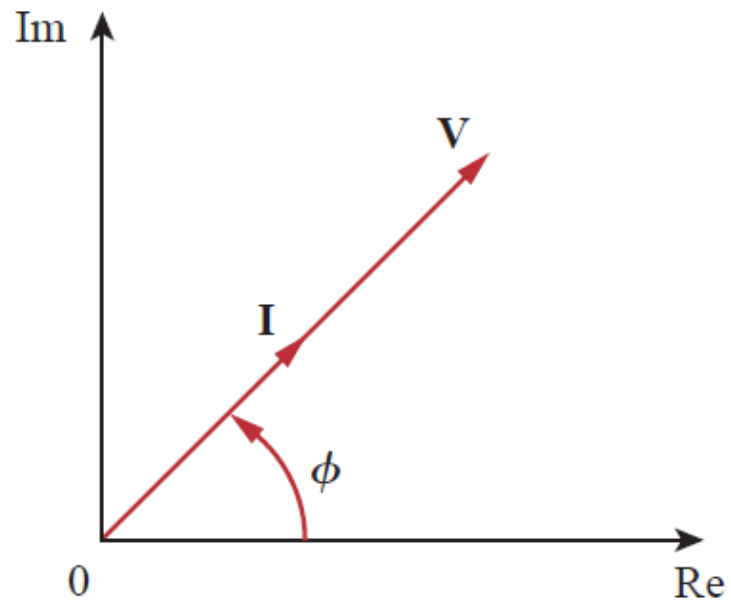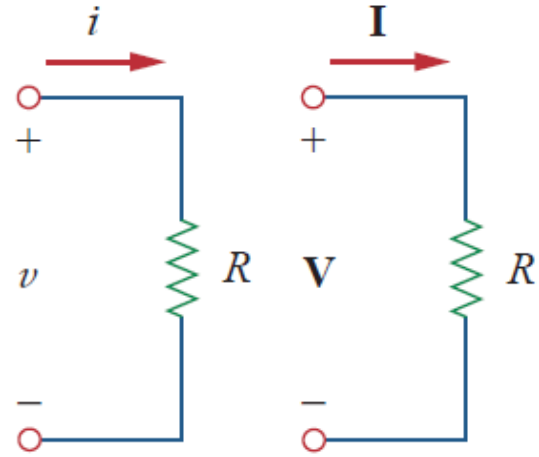

$$i = I_m \cdot \cos(\omega t + \varphi)$$
$$v = R \cdot i = R \cdot I_m \cdot \cos(\omega t + \varphi)$$
$$\mathbf{V} = R \cdot I_m \cdot e^{j\varphi}$$
$$\mathbf{I} = I_m \cdot e^{j\varphi} \rightarrow \mathbf{V} = R \cdot \mathbf{I}$$

# Inductor in the Phasor Domain

'ELI'

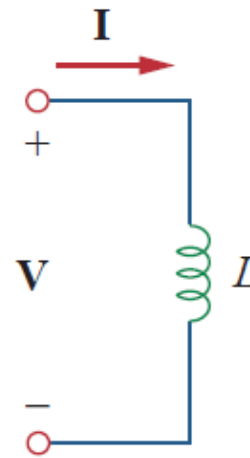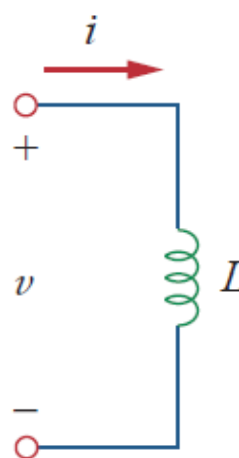


$$i = I_m \cdot \cos(\omega t + \varphi)$$

$$v = L \cdot \frac{di}{dt} = -\omega \cdot L \cdot I_m \cdot \sin(\omega t + \varphi)$$

$$v = L \cdot \frac{di}{dt} = \omega \cdot L \cdot I_m \cdot \cos(\omega t + \varphi + 90^\circ)$$

$$V = \omega \cdot L \cdot I_m \cdot e^{j(\varphi+90^\circ)} = \omega \cdot L \cdot I_m \cdot e^{j\varphi} \cdot e^{j90^\circ}$$
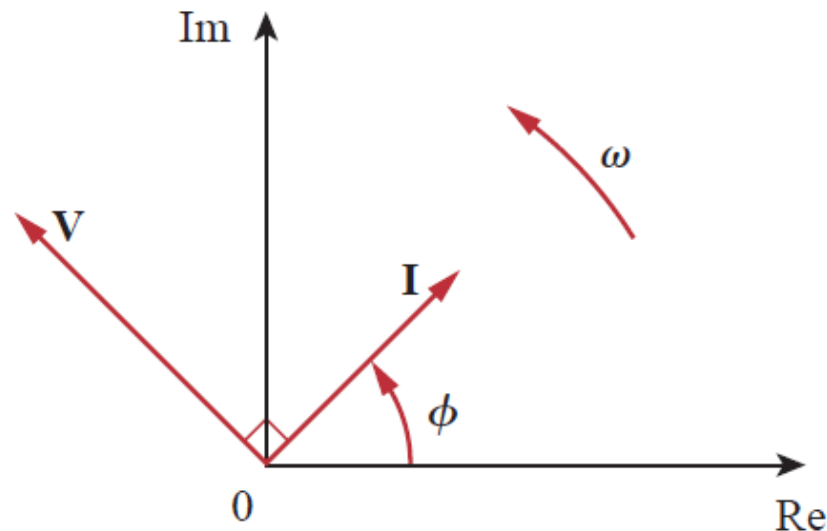
$$I = I_m \cdot e^{j\varphi}, e^{j90^\circ} = j \rightarrow V = j \cdot \omega \cdot L \cdot I$$



# Capacitor in the Phasor Domain

', ICE'




$$v = V_m \cdot \cos(\omega t + \varphi)$$

$$i = C \frac{dv}{dt} = -\omega \cdot C \cdot V_m \cdot \sin(\omega t + \varphi)$$

$$i = C \cdot \frac{dv}{dt} = \omega \cdot C \cdot V_m \cdot \cos(\omega t + \varphi + 90^\circ)$$


$$I = \omega \cdot C \cdot V_m \cdot e^{j(\varphi+90^\circ)} = \omega \cdot C \cdot V_m \cdot e^{j\varphi} \cdot e^{j90^\circ}$$
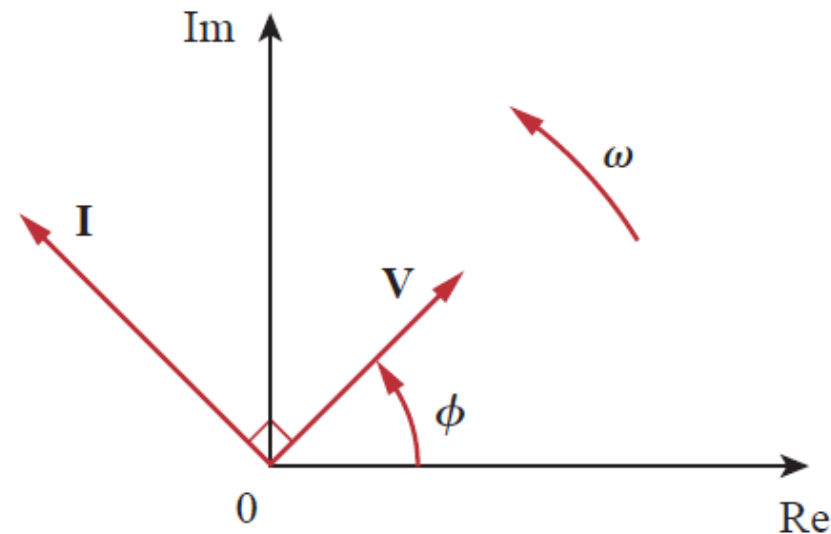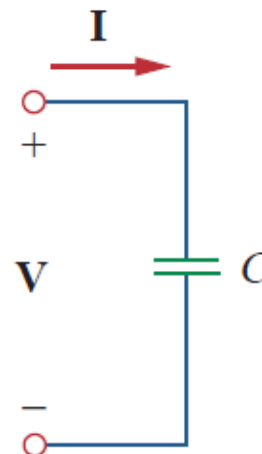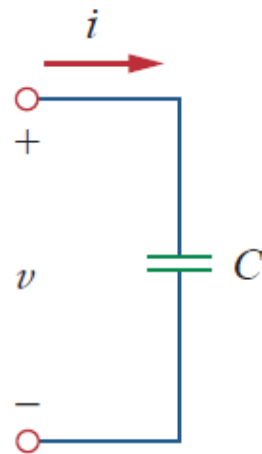
$$I = j \cdot \omega \cdot C \cdot V \Rightarrow V = \frac{1}{j \cdot \omega \cdot C} \cdot I$$



# RLC Elements in the Time and the Phasor Domains (Summary)

Element	Time Domain	Frequency Domain
$R$	$v = R \cdot i$	$V = R \cdot I$
$L$	$v = L \cdot \frac{di}{dt}$	$V = j \cdot \omega \cdot L \cdot I$
$C$	$i = C \cdot \frac{dv}{dt}$	$V = \frac{1}{j \cdot \omega \cdot C} \cdot I$

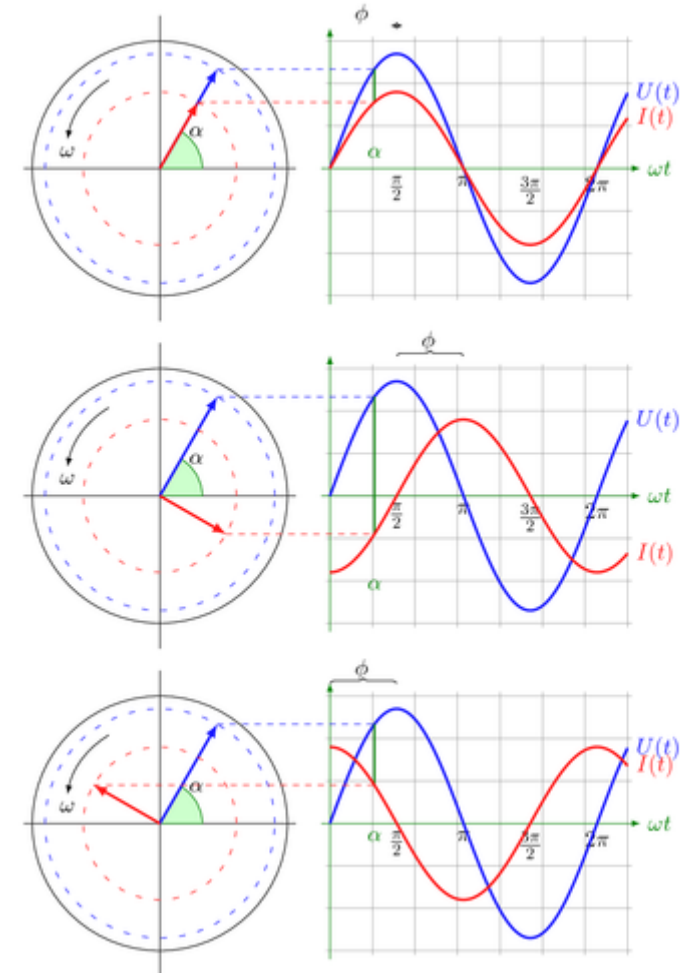

## Impedance and Admittance 1

Element	Time Domain	Frequency Domain
$R$	$v = R \cdot i$	$V = R \cdot I$
$L$	$v = L \cdot \frac{di}{dt}$	$V = j \cdot \omega \cdot L \cdot I$
$C$	$i = C \cdot \frac{dv}{dt}$	$V = \frac{1}{j \cdot \omega \cdot C} \cdot I$

*Ohm's law in phasor form*  $\rightarrow \mathbf{Z} = \frac{V}{I}, \quad \mathbf{Y} = \frac{I}{V}$

$$\mathbf{Z} = R + j \cdot X, \quad \mathbf{Y} = G + j \cdot B$$

### Impedance

- Denoted by the letter  $\mathbf{Z}$  (complex)
- Ratio of the phasor  $V$  to the phasor  $I$
- Measured in ohms ( $\Omega$ )

### Admittance


- Reciprocal of impedance
- Denoted by the letter  $\mathbf{Y}$  (complex)
- Measured in siemens (S).
- $R$ : resistance (real part of the impedance)
- $X$ : reactance (imaginary part of the impedance)
- $G$ : conductance (real part of the admittance)
- $B$ : susceptance (imaginary part of the admittance)

$$\mathbf{Z}_R = R, \quad \mathbf{Z}_L = j\omega L = jX_L, \quad \mathbf{Z}_C = \frac{1}{j\omega C} = -jX_C, \quad \mathbf{Y}_R = G, \quad \mathbf{Y}_L = \frac{1}{j\omega L} = -jB_L, \quad \mathbf{Y}_C = j\omega C = jB_C$$



## Impedance and Admittance 2



$$\mathbf{Z}_L = jX_L = j\omega L$$

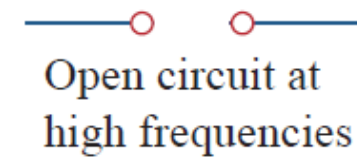
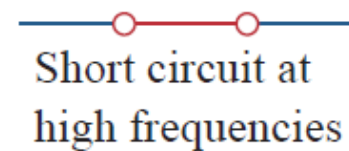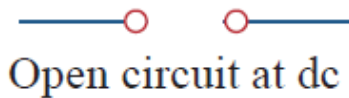
$$\mathbf{Z}_C = \frac{1}{j\omega C} = -jX_C$$



$$\mathbf{Z} = R + jX \rightarrow \begin{cases} Z = |\mathbf{Z}| = \sqrt{R^2 + X^2} & R = Z \cos \Theta \\ \Theta = \tan^{-1} \frac{X}{R} & X = Z \sin \Theta \end{cases}$$

$$\mathbf{Y} = G + jB \rightarrow \begin{cases} Y = |\mathbf{Y}| = \sqrt{G^2 + B^2} & G = Y \cos \Theta \\ \Theta = \tan^{-1} \frac{B}{G} & B = Y \sin \Theta \end{cases}$$

$$G + jB = \frac{1}{R + jX} \rightarrow G + jB = \frac{1}{R + jX} \cdot \frac{R - jX}{R - jX} = \frac{R - jX}{R^2 + X^2}$$

$$G = \frac{R}{R^2 + X^2}, \quad B = -\frac{X}{R^2 + X^2}$$





- Sinusoids and Phasors
- Circuit Elements in the Phasor Domain
- Kirchhoff's Laws in the Phasor Domain**
- Application Example – Phase Shifters

## Kirchhoff's Laws in the Frequency Domain

$$\square \text{ KCL} \rightarrow i_1 + i_2 + i_3 + \dots + i_n = 0$$

$$I_{m1} \cdot \cos(\omega t + \varphi_1) + I_{m2} \cdot \cos(\omega t + \varphi_2) + I_{m3} \cdot \cos(\omega t + \varphi_3) + \dots + I_{mn} \cdot \cos(\omega t + \varphi_n) = 0$$


$$\text{Re}\{I_{m1} \cdot e^{j\varphi_1} \cdot e^{j\omega t}\} + \text{Re}\{I_{m2} \cdot e^{j\varphi_2} \cdot e^{j\omega t}\} + \text{Re}\{I_{m3} \cdot e^{j\varphi_3} \cdot e^{j\omega t}\} + \dots + \text{Re}\{I_{mn} \cdot e^{j\varphi_n} \cdot e^{j\omega t}\} = 0$$

$$\mathbf{I_k = I_{mk} \cdot e^{j\varphi_k} \rightarrow \text{Re}\{(I_1 + I_2 + I_3 + \dots + I_n) \cdot e^{j\omega t}\} = 0}$$

$$e^{j\omega t} \neq 0 \rightarrow \mathbf{I_1 + I_2 + I_3 + \dots + I_n = 0}$$


$$\square \text{ KVL} \rightarrow v_1 + v_2 + v_3 + \dots + v_n = 0 \rightarrow \dots \rightarrow \mathbf{V_1 + V_2 + V_3 + \dots + V_n = 0}$$
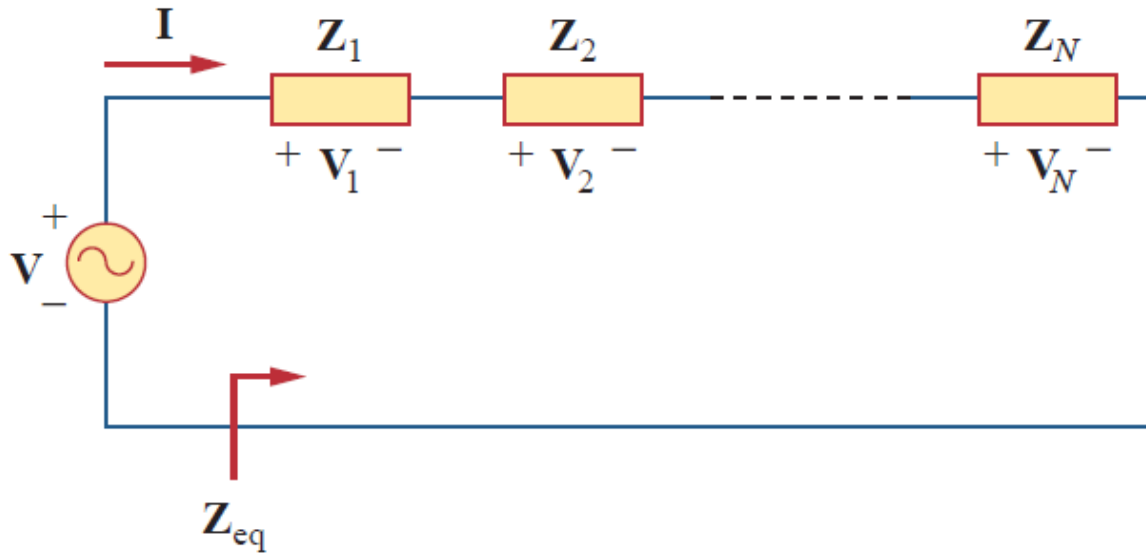
## Series Connected Impedances – Voltage Division



$$V = V_1 + V_2 + V_3 + \dots + V_N = I(Z_1 + Z_2 + Z_3 + \dots + Z_N)$$


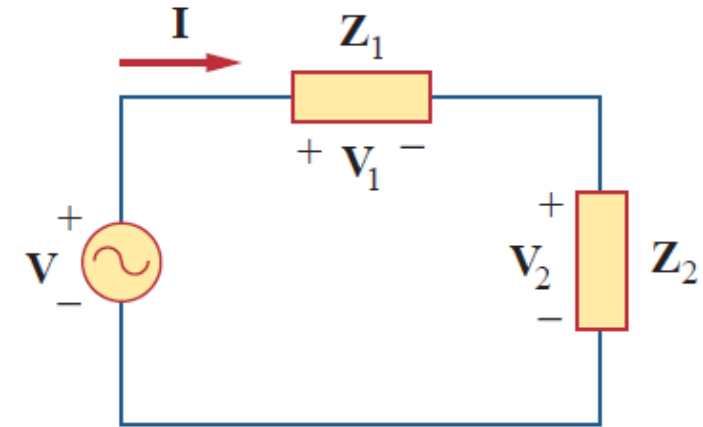
$$Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + Z_3 + \dots + Z_N \rightarrow Z_{eq} = \sum_{i=1}^N Z_i$$



$$I = \frac{V}{Z_1 + Z_2}, V_1 = IZ_1, V_2 = IZ_2$$

$$V_1 = V \frac{Z_1}{Z_1 + Z_2}, V_2 = V \frac{Z_2}{Z_1 + Z_2}$$
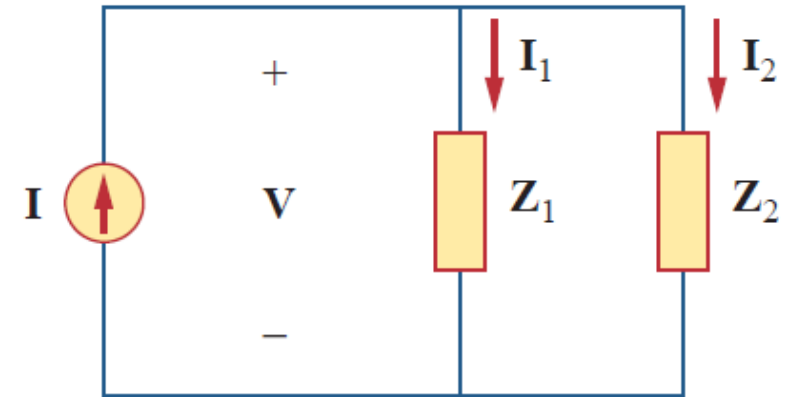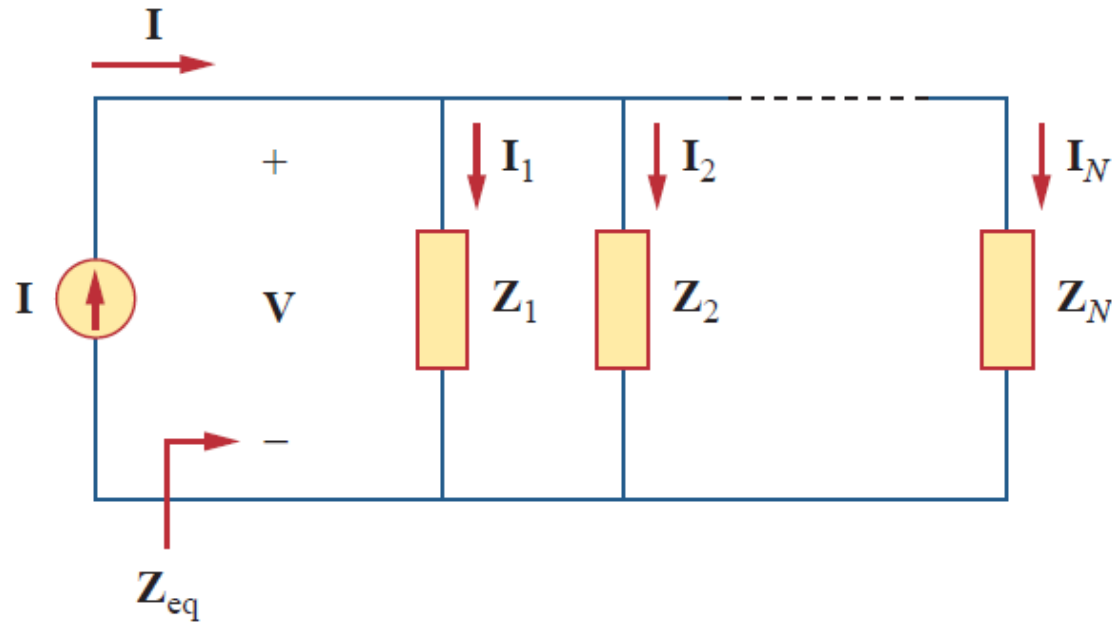
## Parallel Connected Impedances – Current Division




$$I = I_1 + I_2 + \dots + I_N = V \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right)$$

$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{Z_1 Z_2}{Z_1 + Z_2}, \quad V = I Z_{eq} = I_1 Z_1 = I_2 Z_2$$

$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \rightarrow Y_{eq} = \sum_{i=1}^N Y_i$$

$$I_1 = I \frac{Z_2}{Z_1 + Z_2}, \quad I_2 = I \frac{Z_1}{Z_1 + Z_2}$$

# Wye – Delta Transformation

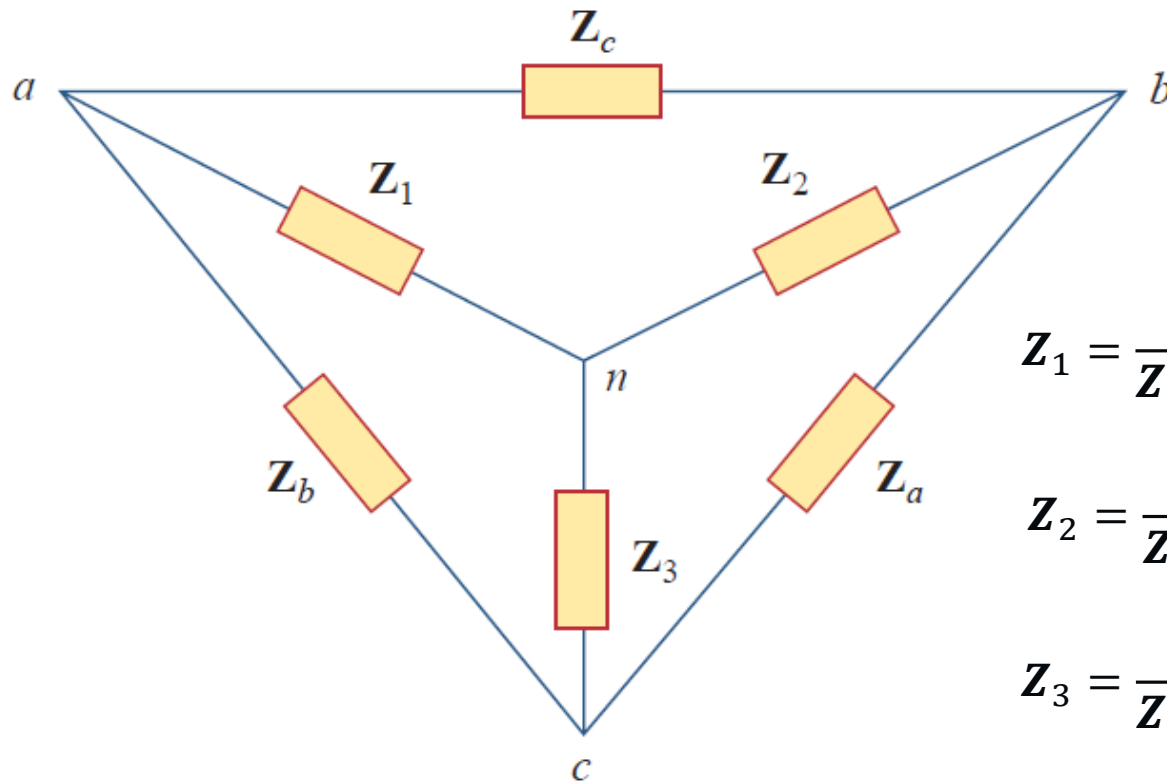

(like it is in DC circuits...)

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_1}$$





$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_3}$$



- Sinusoids and Phasors
- Circuit Elements in the Phasor Domain
- Kirchhoff's Laws in the Phasor Domain
- Application Example – Phase Shifters**

# Applications – Phase Shifters

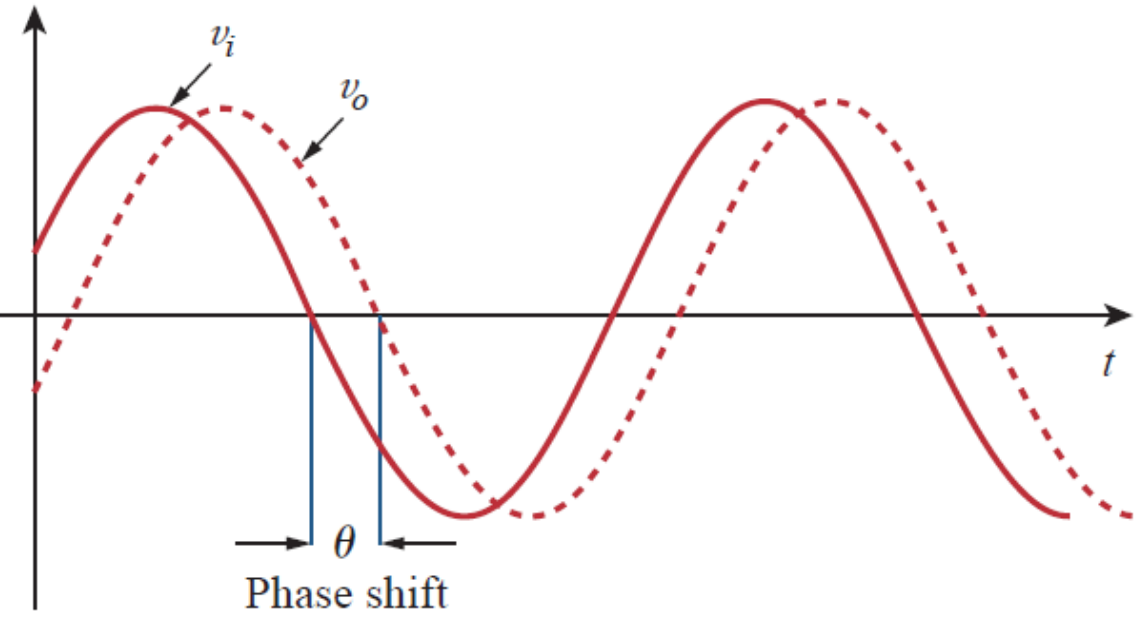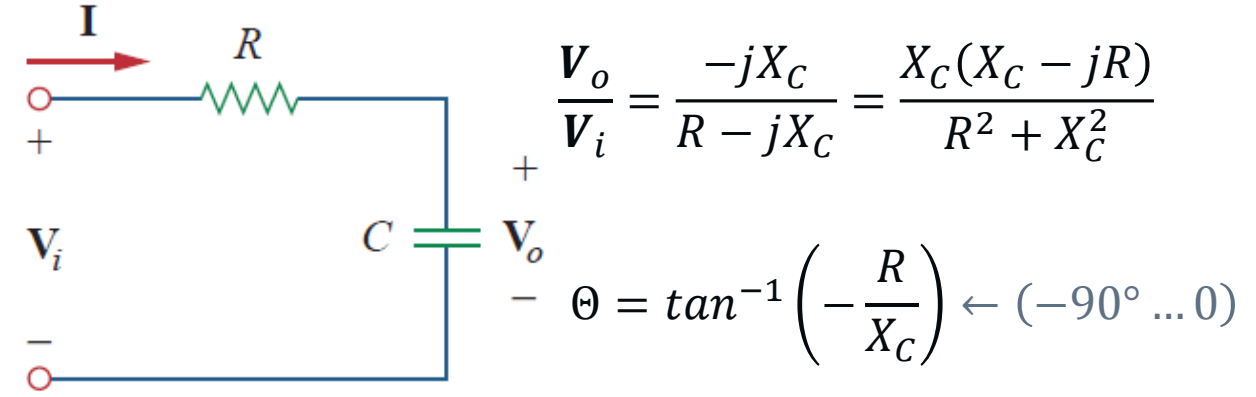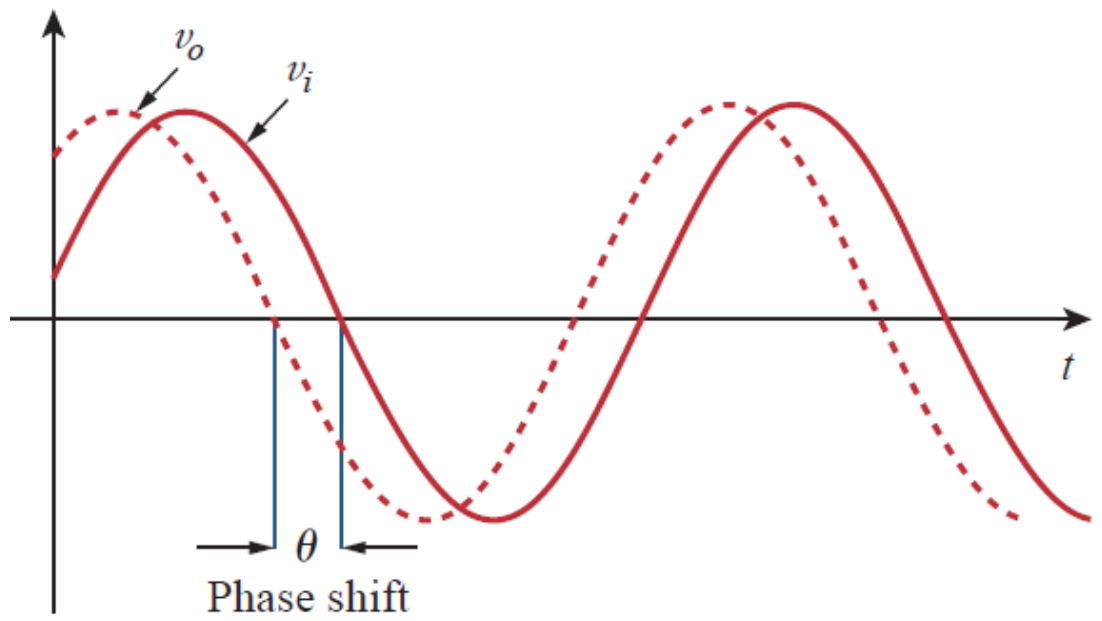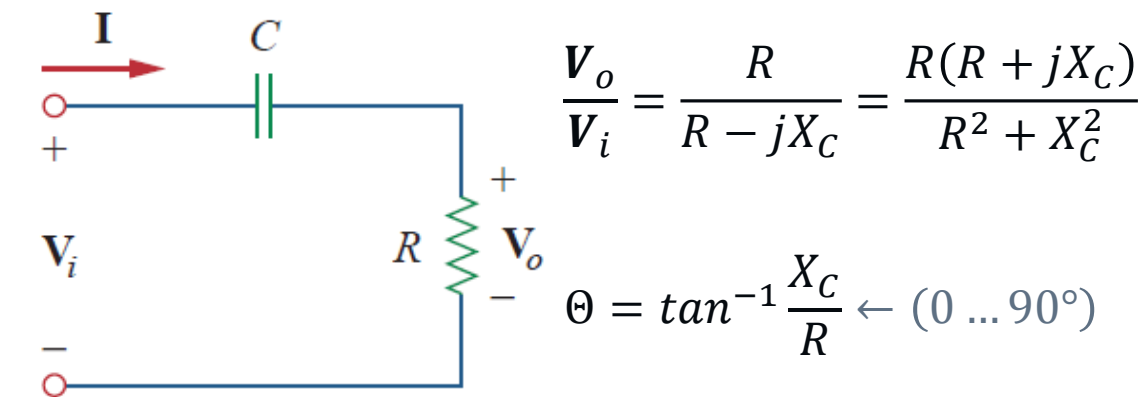

# Questions

