



DR. GYURCSEK ISTVÁN

Sinusoids and Phasors

Sources and additional materials (recommended)

- ❑ *Dr. Gyurcsek – Dr. Elmer: Theories in Electric Circuits, GlobeEdit, 2016, ISBN:978-3-330-71341-3*
- ❑ *Ch. Alexander, M. Sadiku: Fundamentals of Electric Circuits, 6th Ed., McGraw Hill NY 2016, ISBN: 978-0078028229*
- ❑ *Simonyi K.: Villamosságatan. AK Budapest 1983, ISBN:9630534134*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságatan 1. MK Budapest 2002, TK szám: 49203/I*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságatan 2. TK Budapest 2002, ISBN:9631026043*
- ❑ *Zombory L.: Elektromágneses terek. MK Budapest 2006, (www.electro.uni-miskolc.hu)*



Sinusoids and Phasors

- Circuit Elements in the Phasor Domain
- Kirchhoff's Laws in the Phasor Domain
- Application Example – Phase Shifters

Sinusoids 1



(Homework: overview the math. functions)

Periodic function $v(t) = v(t + nT)$

□ \rightarrow all t , \rightarrow all integers n

$$v(t) = V_m \sin \omega t = V_m \sin\{\omega(t + nT)\}$$



□ Amplitude $\rightarrow V_m$ (V)

□ Argument $\rightarrow \omega t$ (rad)

□ Angular frequency $\rightarrow \omega$ (rad/s)

$$\omega T = 2\pi \quad f = \frac{1}{T} \rightarrow \omega = 2\pi f$$

$$\left(\text{wave propagation} \rightarrow \lambda = c \cdot T = \frac{c}{f} \right)$$

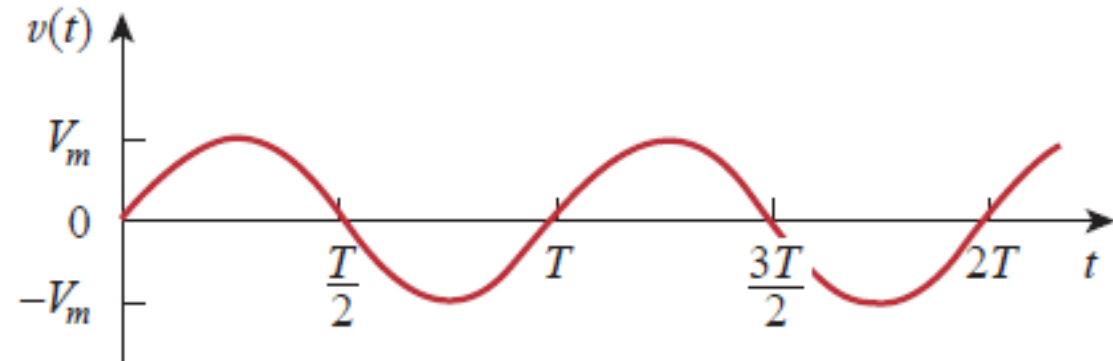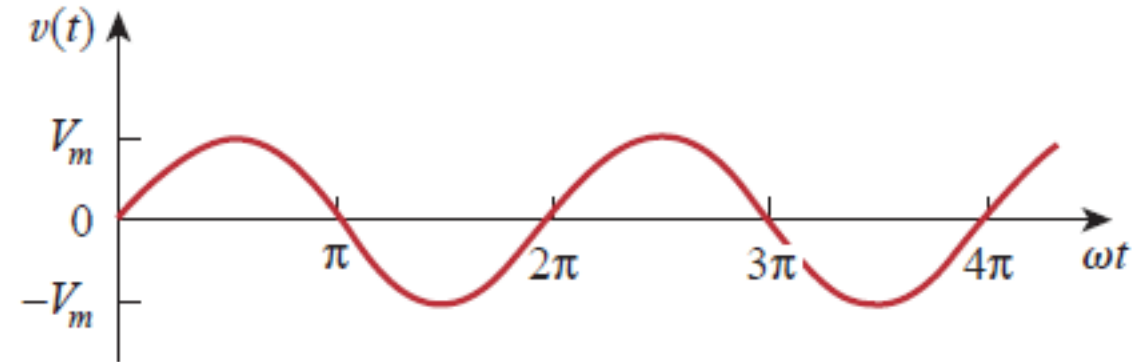

Sinusoids 2



General expression for sinusoid

$$v(t) = V_m \sin(\omega t + \phi)$$

Argument $\rightarrow \omega t + \phi$

v_2 leads v_1 by ϕ

Same (sin or cos) forms \rightarrow in calculations

$$\sin(\alpha \pm \beta) = \sin \alpha \cos \beta \pm \cos \alpha \sin \beta$$


$$\cos(\alpha \pm \beta) = \cos \alpha \cos \beta \mp \sin \alpha \sin \beta$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$
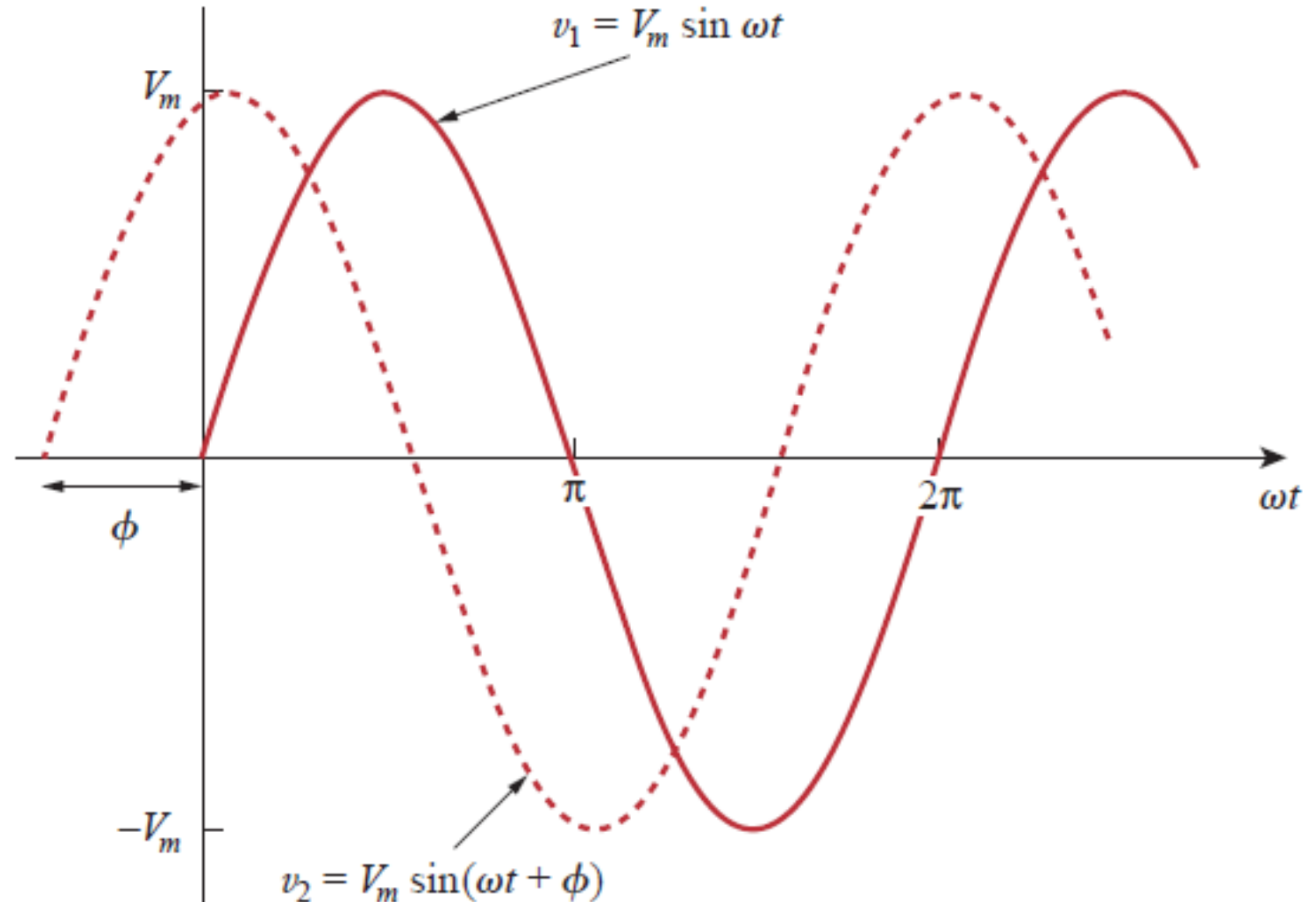
$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$




Graphical Representation




$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$
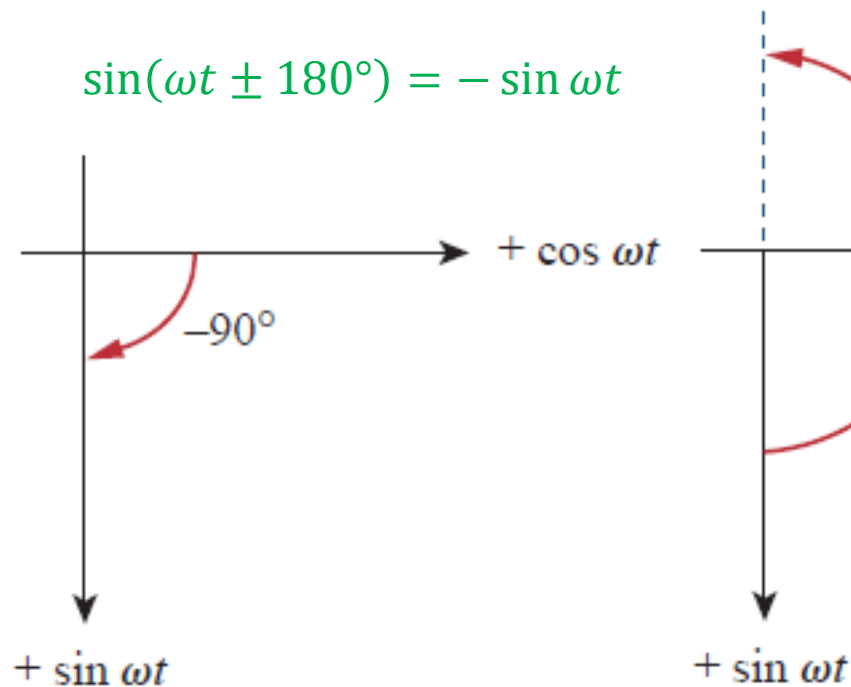
$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$



$$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \Theta)$$

$$C = \sqrt{A^2 + B^2}, \quad \Theta = \tan^{-1} \frac{B}{A}$$

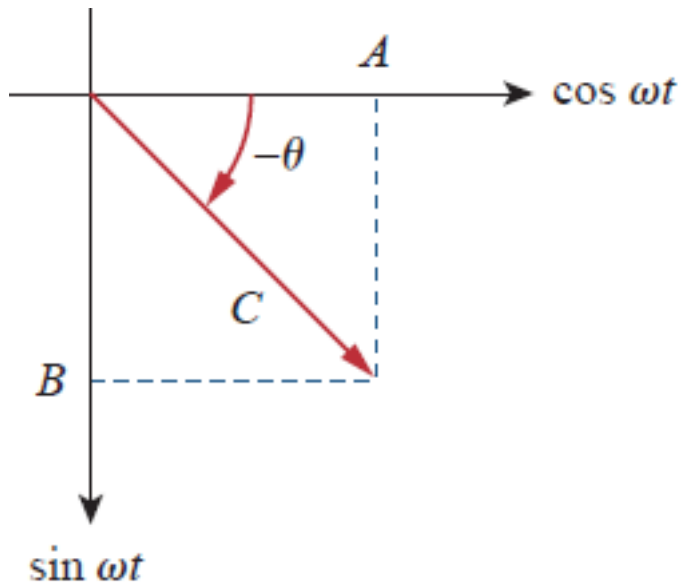

Phasors 1




- Phasor → complex number ... representing amplitude and phase of a sinusoid
- Suppressing time factor → transforming sinusoid from time domain to phasor domain.

rectangular → $x + j \cdot y$
 polar → $r \cdot e^{j\varphi}$, (r/φ)

$$j = \sqrt{-1} \quad z = x + j \cdot y = r \cdot (\cos \varphi + j \cdot \sin \varphi) = r \cdot e^{j\varphi}$$
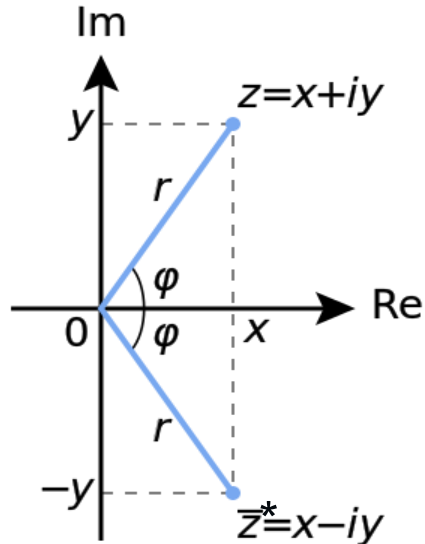
$$e^{j\varphi} = \cos \varphi + j \cdot \sin \varphi \leftarrow \text{Euler's identity}$$



$$r = \sqrt{x^2 + y^2}, \quad \varphi = \tan^{-1} \frac{y}{x}$$

$$x = r \cdot \cos \varphi, \quad y = r \cdot \sin \varphi$$

$$\cos \varphi = \frac{e^{j\varphi} + e^{-j\varphi}}{2}$$

$$\sin \varphi = \frac{e^{j\varphi} - e^{-j\varphi}}{j \cdot 2}$$

Calculations

$$z_1 = x_1 + j \cdot y_1, \quad z_2 = x_2 + j \cdot y_2$$

$$z_1 + z_2 = (x_1 + x_2) + j \cdot (y_1 + y_2)$$

$$z_1 \cdot z_2 = r_1 \cdot r_2 \cdot e^{j(\varphi_1 + \varphi_2)}$$

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \cdot e^{j(\varphi_1 - \varphi_2)}$$


$$z^* = x - j \cdot y = r \cdot e^{-j\varphi}$$

Phasors 2




$$v(t) = V_m \cos(\omega t + \varphi) \xrightarrow{\text{transf.}} v(t) = V_m [\cos(\omega t + \varphi) + j \sin(\omega t + \varphi)]$$

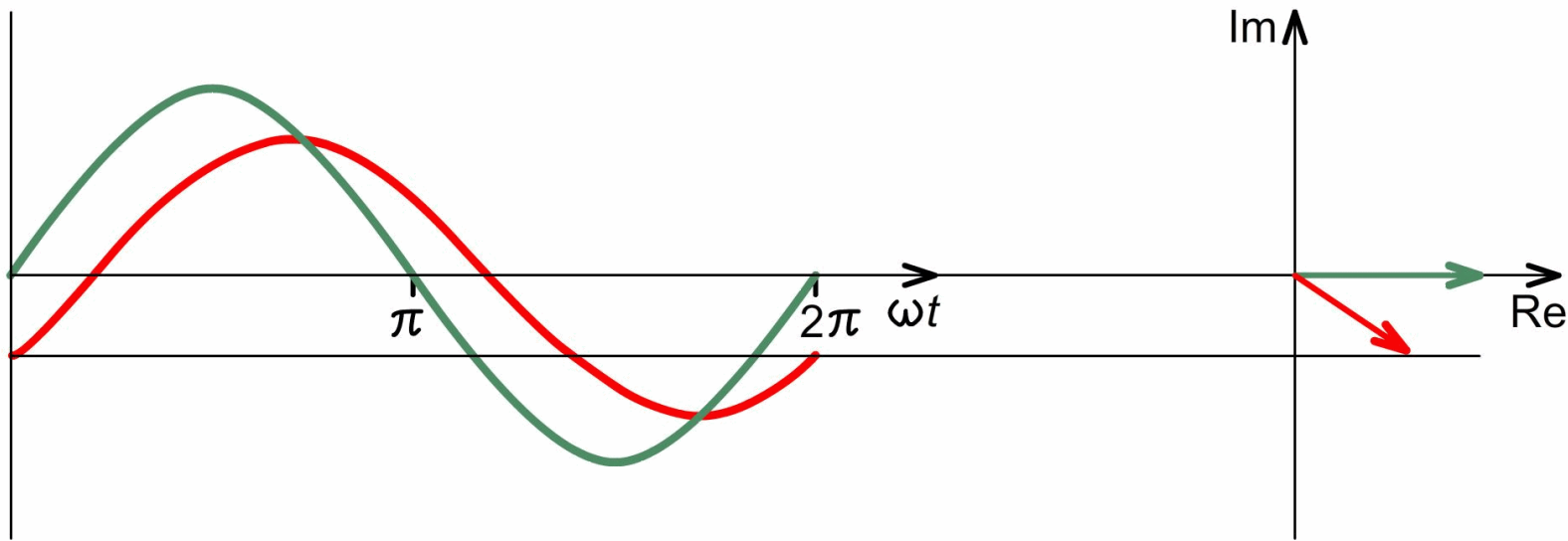
(time dept. cpx. function) $v(t) = V_m e^{j(\omega t + \varphi)} = V_m e^{j\varphi} e^{j\omega t}$



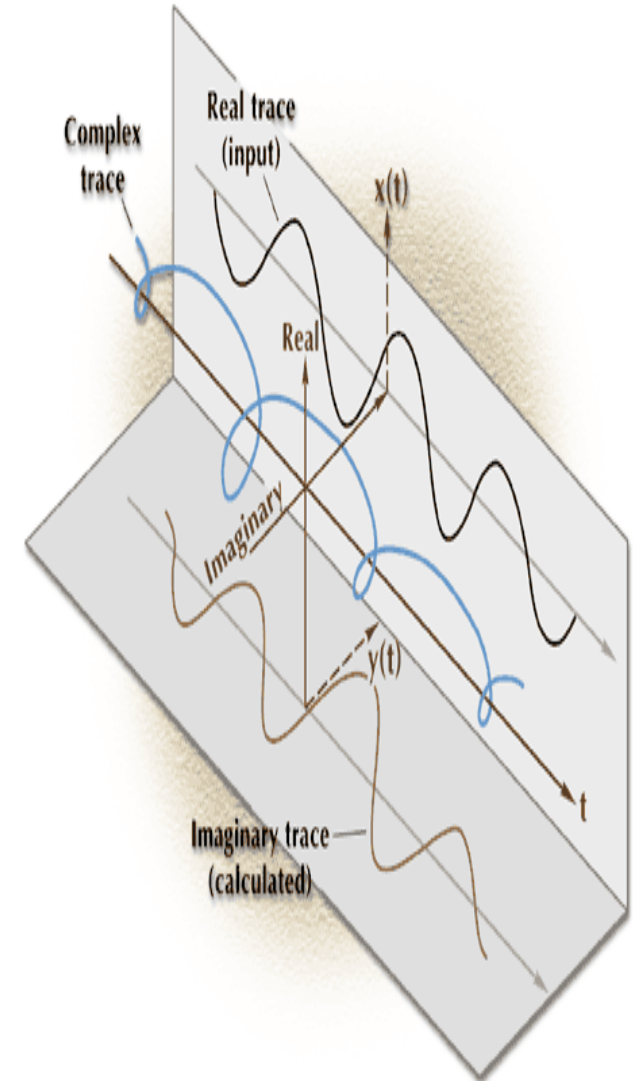
$$v(t) = \text{Re} \{v(t)\} \quad \text{PHASOR (suppressing time factor)} \rightarrow V_m = V_m e^{j\varphi}$$



Phasor 3 (illustration)

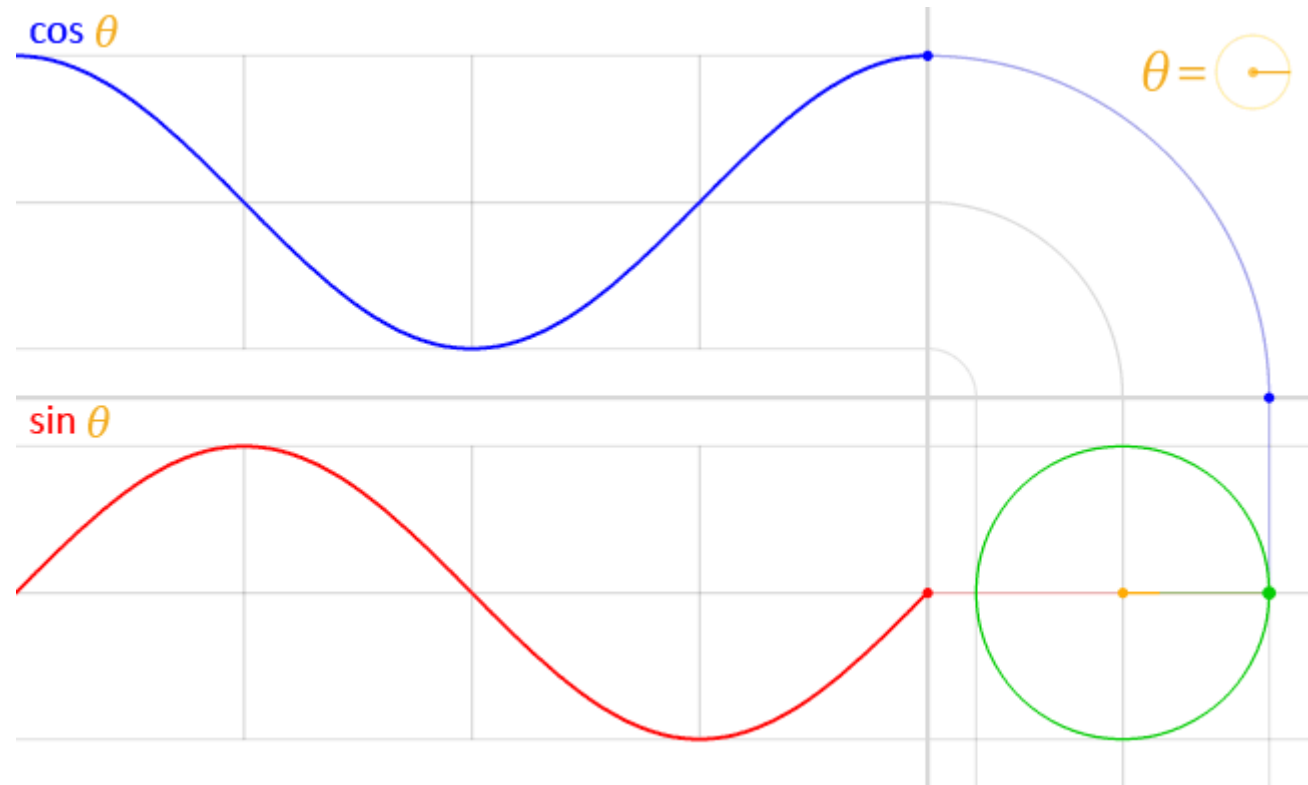

Transform time to phasor domain

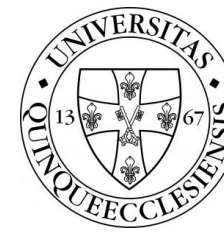

$$v = V_m \cos(\omega t + \varphi) \rightarrow \frac{dv}{dt} =? \rightarrow \frac{dv}{dt} = -\omega V_m \sin(\omega t + \varphi)$$

$$= \omega V_m \cos(\omega t + \varphi + 90^\circ) = \operatorname{Re} \{ \omega V_m e^{j\omega t} e^{j\varphi} e^{j90^\circ} \}$$

$$= \operatorname{Re} \{ j\omega \mathbf{V} e^{j\omega t} \}$$

COMMENTS

- Complex number \rightarrow scalar! (,normal' z)
- Phasor \rightarrow ,vector-like' behavior (,bold' \mathbf{V})

CONDITION!

Phasor analysis \rightarrow frequency is the same

Time domain	Phasor domain
$v(t) = V_m \cos(\omega t + \varphi)$	$\mathbf{V} = V_m e^{j\varphi}$
$\frac{dv(t)}{dt}$	$j\omega \mathbf{V}$
$\int v(t) \cdot dt$	$\frac{1}{j\omega} \mathbf{V}$

Properties of , $v(t)$ '

- Instantaneous or time domain represent.
- Time dependent
- Always real



Properties of , \mathbf{V} '

- Frequency or phasor domain represent.
- Time independent
- Generally complex



- Sinusoids and Phasors
- Circuit Elements in the Phasor Domain**
- Kirchhoff's Laws in the Phasor Domain
- Application Example – Phase Shifters

Resistor in Phasor Domain

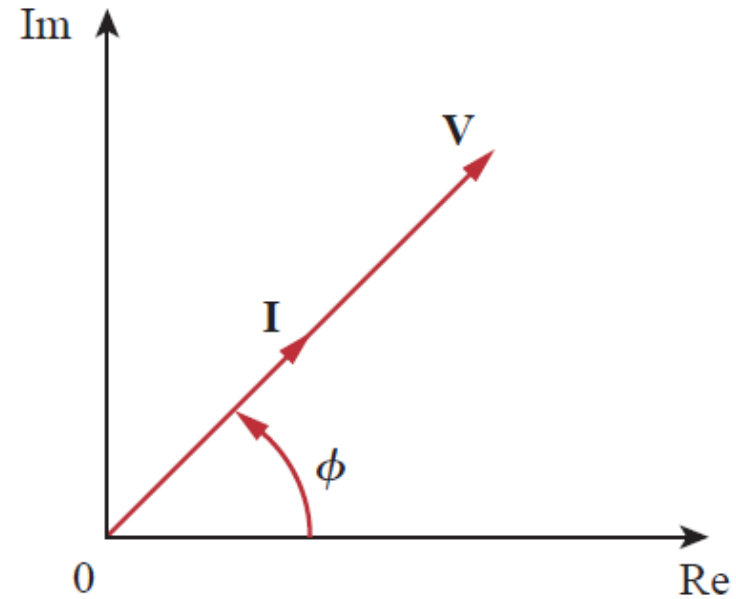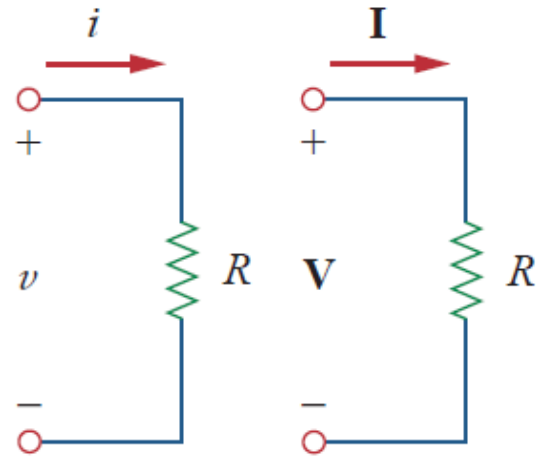

$$i = I_m \cdot \cos(\omega t + \varphi)$$

$$v = R \cdot i = R \cdot I_m \cdot \cos(\omega t + \varphi)$$

$$\mathbf{V} = R \cdot I_m \cdot e^{j\varphi}$$

$$\mathbf{I} = I_m \cdot e^{j\varphi} \rightarrow \mathbf{V} = R \cdot \mathbf{I}$$

Inductor in Phasor Domain



'ELI'



$$i = I_m \cdot \cos(\omega t + \varphi)$$

$$v = L \cdot \frac{di}{dt} = -\omega \cdot L \cdot I_m \cdot \sin(\omega t + \varphi)$$

$$v = L \cdot \frac{di}{dt} = \omega \cdot L \cdot I_m \cdot \cos(\omega t + \varphi + 90^\circ)$$

$$V = \omega \cdot L \cdot I_m \cdot e^{j(\varphi+90^\circ)} = \omega \cdot L \cdot I_m \cdot e^{j\varphi} \cdot e^{j90^\circ}$$
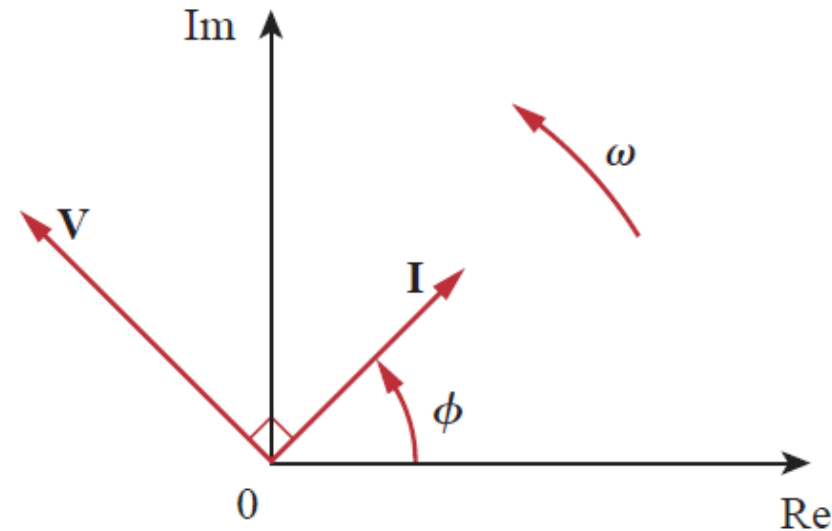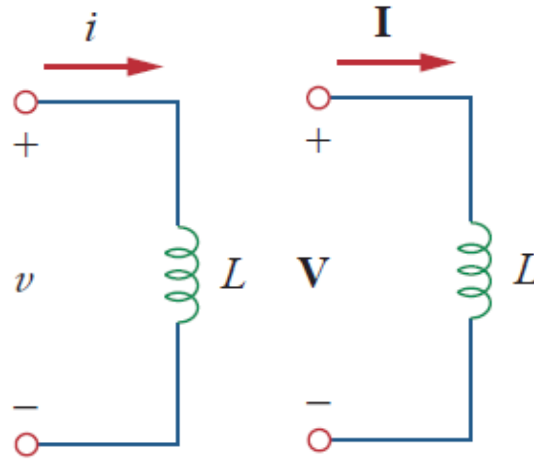
$$I = I_m \cdot e^{j\varphi}, e^{j90^\circ} = j \rightarrow \mathbf{V = j \cdot \omega \cdot L \cdot I}$$



Capacitor in Phasor Domain



'ICE'



$$v = V_m \cdot \cos(\omega t + \varphi)$$

$$i = C \frac{dv}{dt} = -\omega \cdot C \cdot V_m \cdot \sin(\omega t + \varphi)$$

$$i = C \cdot \frac{dv}{dt} = \omega \cdot C \cdot V_m \cdot \cos(\omega t + \varphi + 90^\circ)$$

$$I = \omega \cdot C \cdot V_m \cdot e^{j(\varphi+90^\circ)} = \omega \cdot C \cdot V_m \cdot e^{j\varphi} \cdot e^{j90^\circ}$$

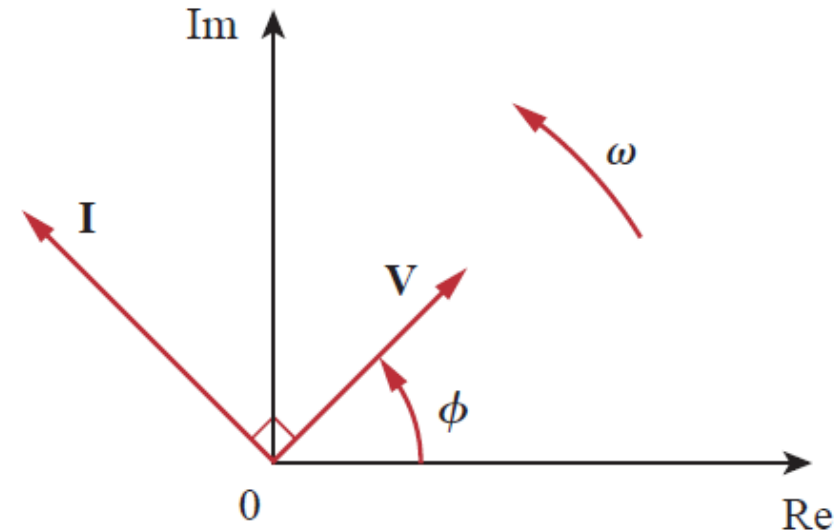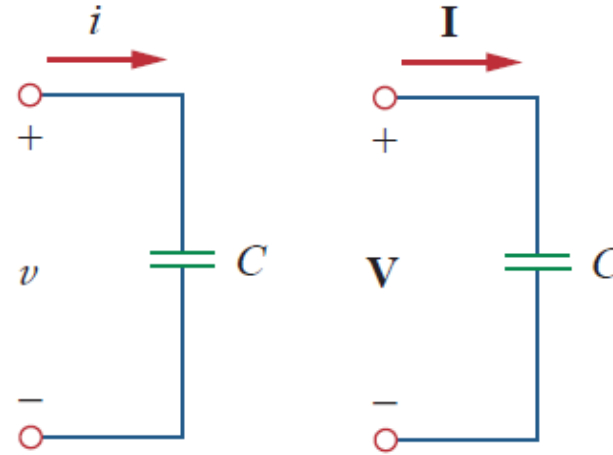
$$I = j \cdot \omega \cdot C \cdot V \Rightarrow V = \frac{1}{j \cdot \omega \cdot C} \cdot I$$




Summary



Element	Time Domain	Frequency Domain
R	$v = R \cdot i$	$V = R \cdot I$
L	$v = L \cdot \frac{di}{dt}$	$V = j \cdot \omega \cdot L \cdot I$
C	$i = C \cdot \frac{dv}{dt}$	$V = \frac{1}{j \cdot \omega \cdot C} \cdot I$

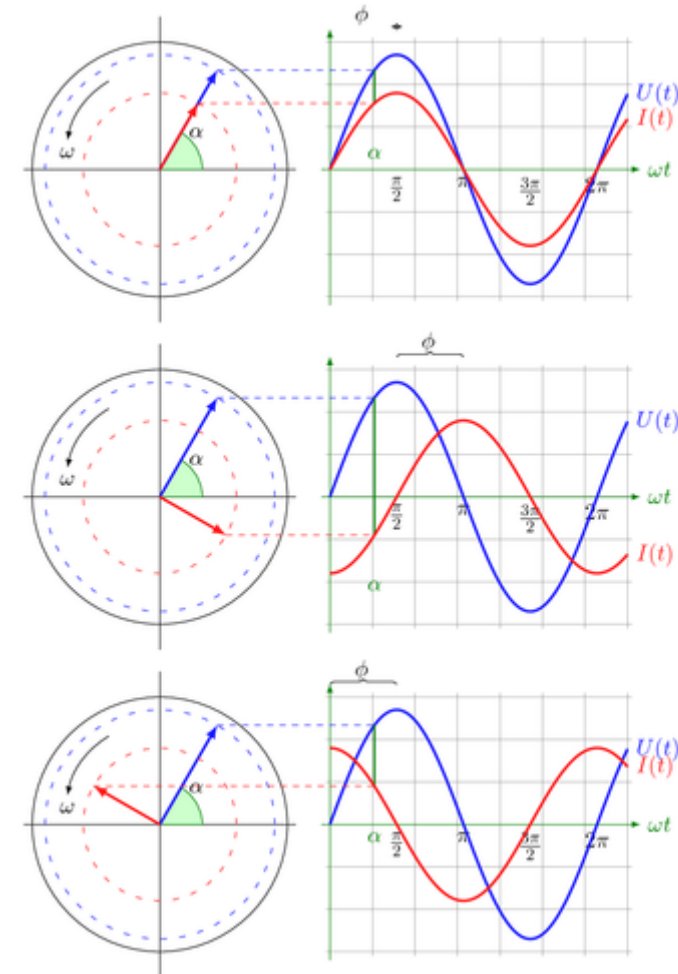

Impedance and Admittance

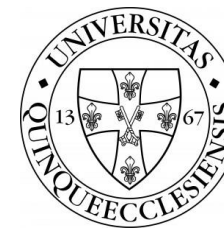

Element	Time Domain	Frequency Domain
R	$v = R \cdot i$	$V = R \cdot I$
L	$v = L \cdot \frac{di}{dt}$	$V = j\omega L \cdot I$
C	$i = C \cdot \frac{dv}{dt}$	$V = \frac{1}{j\omega C} \cdot I$

Ohm's law in phasor form $\rightarrow Z = \frac{V}{I}, \quad Y = \frac{I}{V}$

$$Z = R + j \cdot X, \quad Y = G + j \cdot B$$

Impedance

- Denoted by the letter **Z** (complex)
- Ratio of the phasor **V** to the phasor **I**
- Measured in ohms (Ω)

Admittance



- Reciprocal of impedance
- Denoted by the letter **Y** (complex)
- Measured in siemens (S).
- R : resistance (real part of the impedance)
- X : reactance (imaginary part of the impedance)
- G : conductance (real part of the admittance)
- B : susceptance (imaginary part of the admittance)

$$Z_R = R, \quad Z_L = j\omega L = jX_L, \quad Z_C = \frac{1}{j\omega C} = -jX_C, \quad Y_R = G, \quad Y_L = \frac{1}{j\omega L} = -jB_L, \quad Y_C = j\omega C = jB_C$$



Impedance and Admittance



$$Z_L = jX_L = j\omega L$$

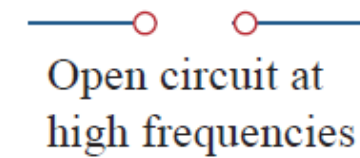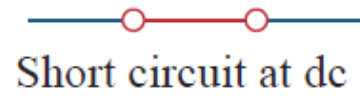

$$Z_C = \frac{1}{j\omega C} = -jX_C$$

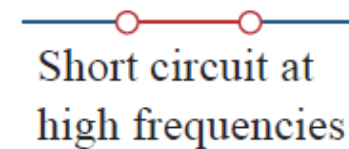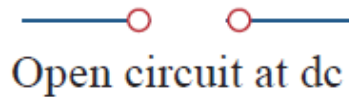

$$Z = R + jX \rightarrow \begin{cases} Z = |Z| = \sqrt{R^2 + X^2} & R = Z \cos \Theta \\ \Theta = \tan^{-1} \frac{X}{R} & X = Z \sin \Theta \end{cases}$$

$$Y = G + jB \rightarrow \begin{cases} Y = |Y| = \sqrt{G^2 + B^2} & G = Y \cos \Theta \\ \Theta = \tan^{-1} \frac{B}{G} & B = Y \sin \Theta \end{cases}$$

$$G + jB = \frac{1}{R + jX} \rightarrow G + jB = \frac{1}{R + jX} \cdot \frac{R - jX}{R - jX} = \frac{R - jX}{R^2 + X^2}$$

$$G = \frac{R}{R^2 + X^2}, \quad B = -\frac{X}{R^2 + X^2}$$



- Sinusoids and Phasors
- Circuit Elements in the Phasor Domain
- Kirchhoff's Laws in the Phasor Domain**
- Application Example – Phase Shifters

Kirchhoff's Laws in Freq. Domain



□ KCL $\rightarrow i_1 + i_2 + i_3 + \dots + i_n = 0$

$$I_{m1} \cdot \cos(\omega t + \varphi_1) + I_{m2} \cdot \cos(\omega t + \varphi_2) + I_{m3} \cdot \cos(\omega t + \varphi_3) + \dots + I_{mn} \cdot \cos(\omega t + \varphi_n) = 0$$



$$\operatorname{Re}\{I_{m1} \cdot e^{j\varphi_1} \cdot e^{j\omega t}\} + \operatorname{Re}\{I_{m2} \cdot e^{j\varphi_2} \cdot e^{j\omega t}\} + \operatorname{Re}\{I_{m3} \cdot e^{j\varphi_3} \cdot e^{j\omega t}\} + \dots + \operatorname{Re}\{I_{mn} \cdot e^{j\varphi_n} \cdot e^{j\omega t}\} = 0$$

$$I_k = I_{mk} \cdot e^{j\varphi_k} \rightarrow \operatorname{Re}\{(I_1 + I_2 + I_3 + \dots + I_n) \cdot e^{j\omega t}\} = 0$$

$$e^{j\omega t} \neq 0 \rightarrow I_1 + I_2 + I_3 + \dots + I_n = 0$$

□ KVL $\rightarrow v_1 + v_2 + v_3 + \dots + v_n = 0 \rightarrow \dots \rightarrow V_1 + V_2 + V_3 + \dots + V_n = 0$

Series Impedances, Voltage Division

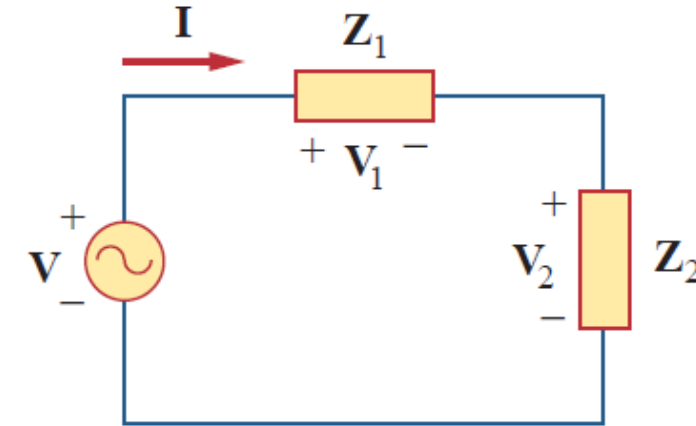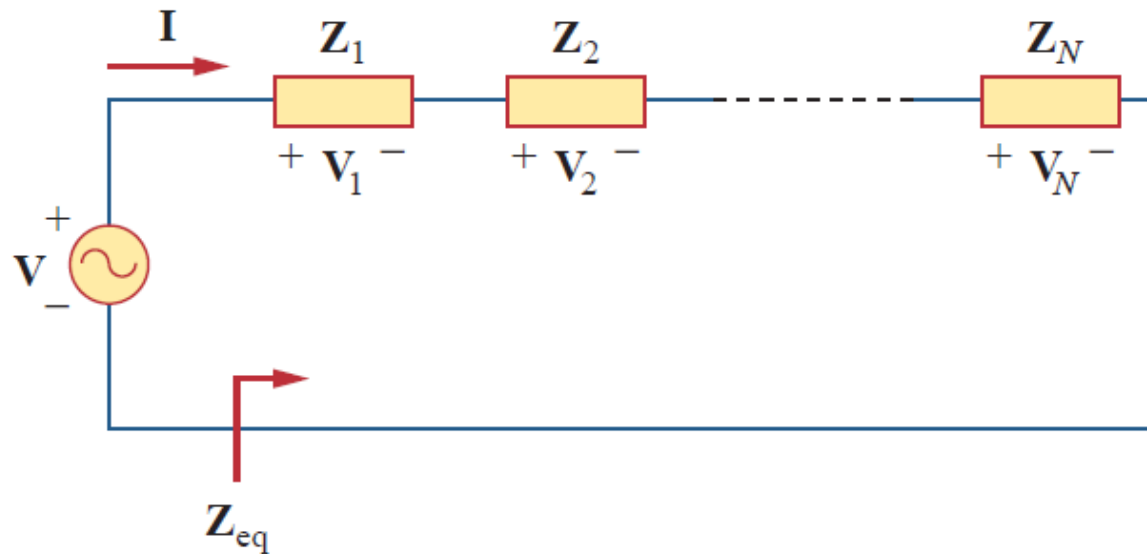



$$V = V_1 + V_2 + V_3 + \dots + V_N = I(Z_1 + Z_2 + Z_3 + \dots + Z_N)$$

$$I = \frac{V}{Z_1 + Z_2}, V_1 = IZ_1, V_2 = IZ_2$$

$$Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + Z_3 + \dots + Z_N \rightarrow Z_{eq} = \sum_{i=1}^N Z_i$$

$$V_1 = V \frac{Z_1}{Z_1 + Z_2}, V_2 = V \frac{Z_2}{Z_1 + Z_2}$$

Parallel Impedances, Current Division

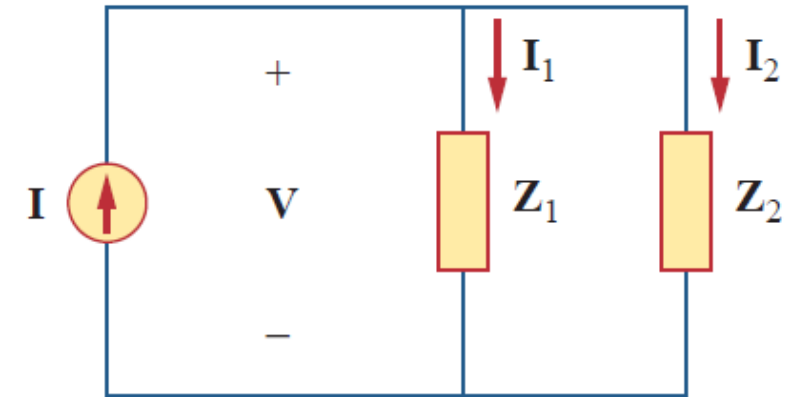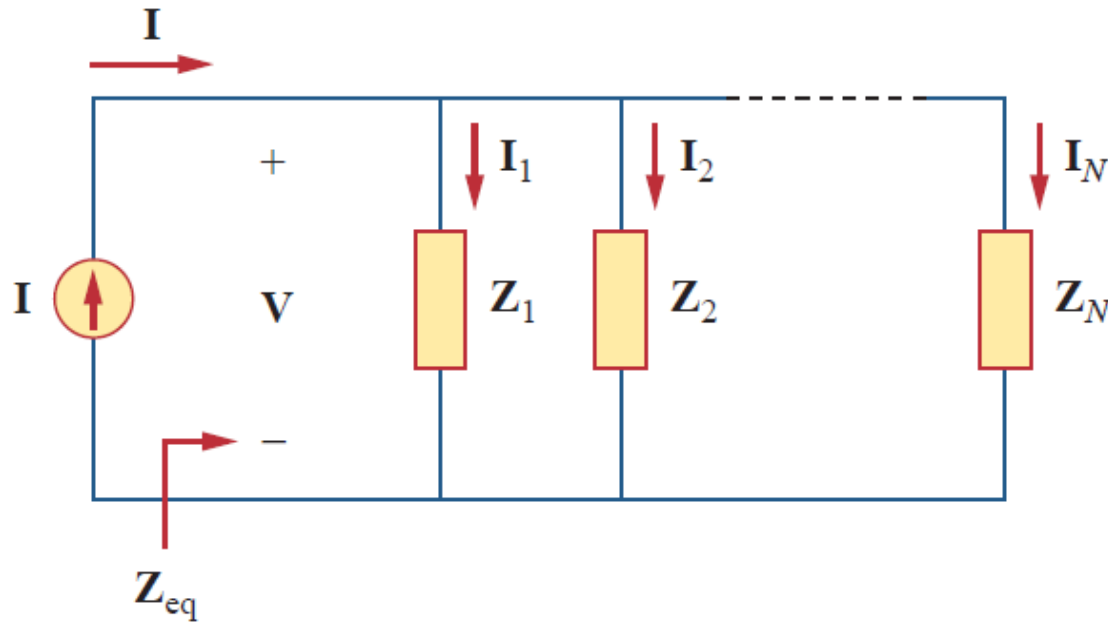


$$I = I_1 + I_2 + \dots + I_N = V \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right)$$

$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{Z_1 Z_2}{Z_1 + Z_2}, \quad V = I Z_{eq} = I_1 Z_1 = I_2 Z_2$$

$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \rightarrow Y_{eq} = \sum_{i=1}^N Y_i$$

$$I_1 = I \frac{Z_2}{Z_1 + Z_2}, \quad I_2 = I \frac{Z_1}{Z_1 + Z_2}$$

Wye – Delta Transform

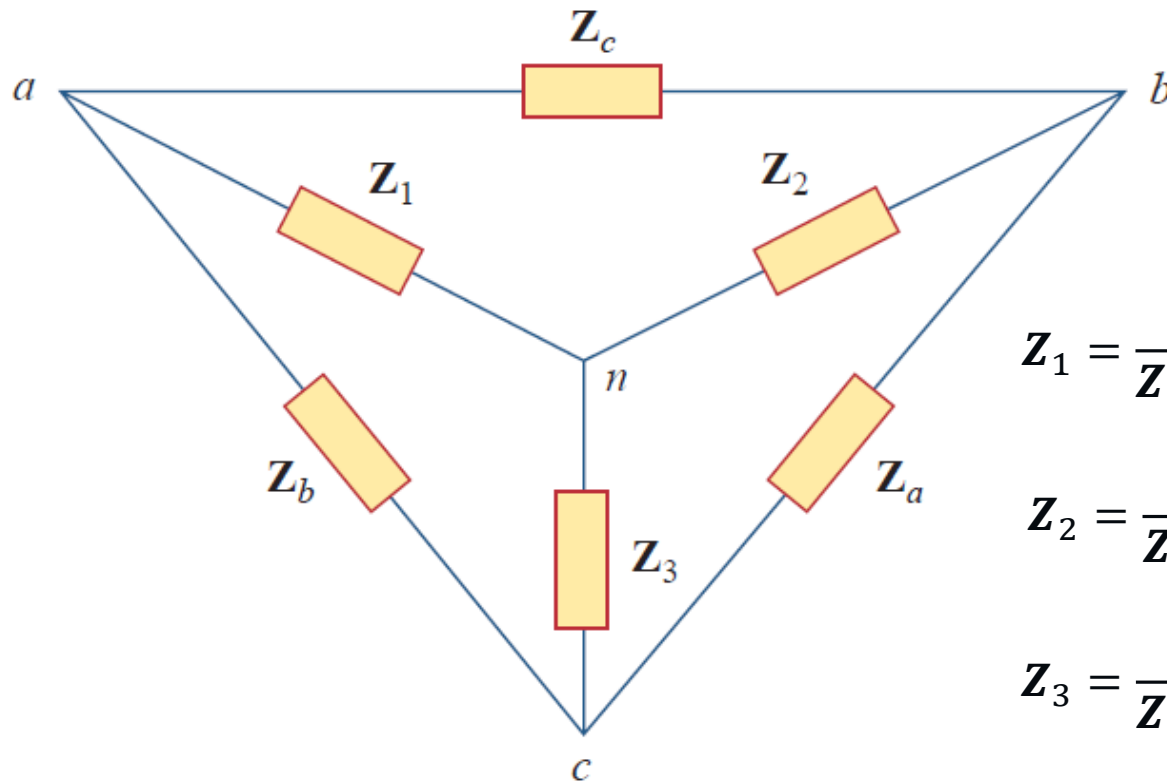

(like it is in DC circuits...)

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_1}$$


$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_3}$$





- ❑ Sinusoids and Phasors
- ❑ Circuit Elements in the Phasor Domain
- ❑ Kirchhoff's Laws in the Phasor Domain
- ❑ **Application Example – Phase Shifters**

App. – Phase Shifters

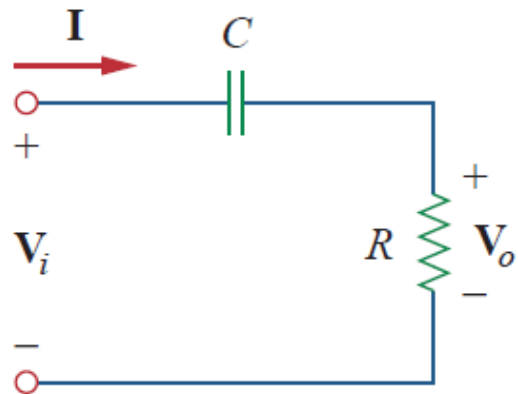


$$\frac{V_o}{V_i} = \frac{R}{R - jX_C} = \frac{R(R + jX_C)}{R^2 + X_C^2}$$
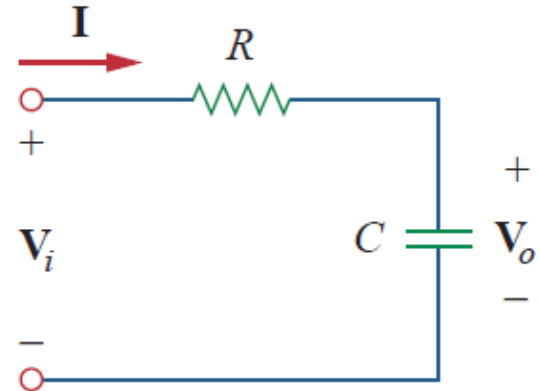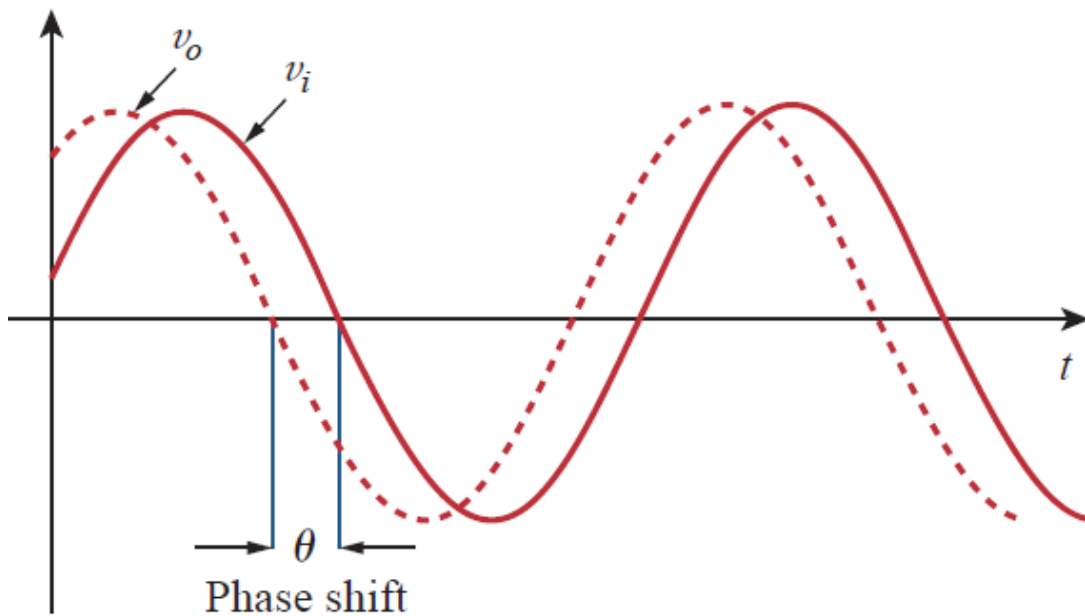
$$\Theta = \tan^{-1} \frac{X_C}{R} \leftarrow (0 \dots 90^\circ)$$



$$\frac{V_o}{V_i} = \frac{-jX_C}{R - jX_C} = \frac{X_C(X_C - jR)}{R^2 + X_C^2}$$
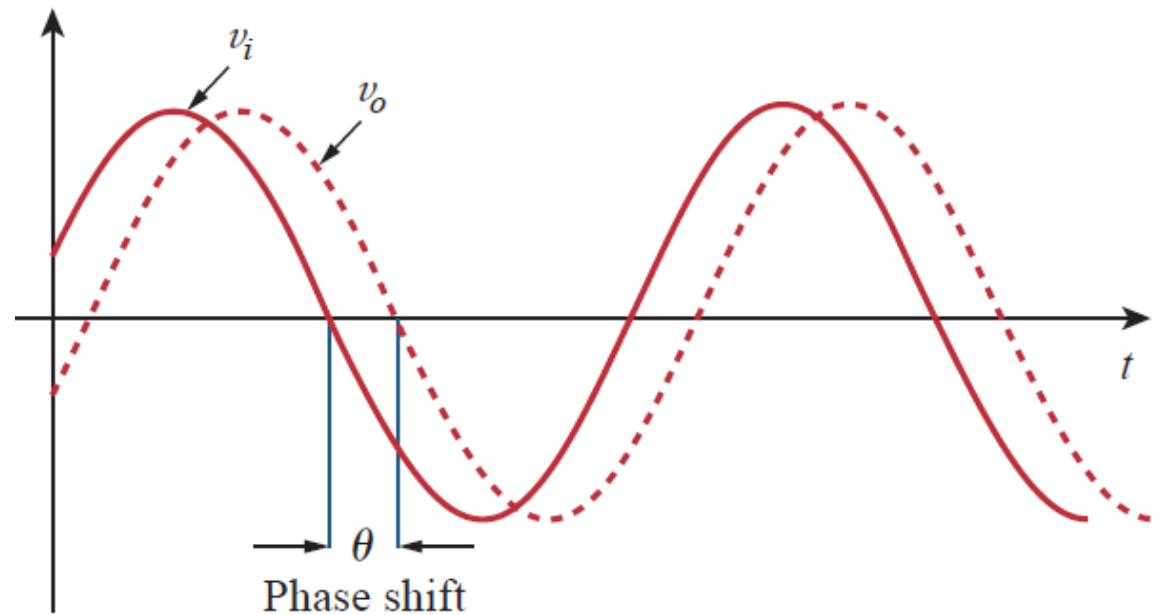
$$\Theta = \tan^{-1} \left(-\frac{R}{X_C} \right) \leftarrow (-90^\circ \dots 0)$$



Questions

