

DR. GYURCSEK ISTVÁN

Magnetically Coupled Circuits

Sources and additional materials (recommended)

- ❑ *Dr. Gyurcsek – Dr. Elmer: Theories in Electric Circuits, GlobeEdit, 2016, ISBN:978-3-330-71341-3*
- ❑ *Ch. Alexander, M. Sadiku: Fundamentals of Electric Circuits, 6th Ed., McGraw Hill NY 2016, ISBN: 978-0078028229*
- ❑ *W. M. Flanagan, Handbook of Transformer Design and Applications, 2nd ed. (New York: McGraw-Hill, 1993)*
- ❑ *Mayergoyz - Lawson: Basic Electric Circuit Theory (ISBN13: 978-0124808652)*
- ❑ *Simonyi K.: Villamosságtan. AK Budapest 1983, ISBN:9630534134*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságtan 1. MK Budapest 2002, TK szám: 49203/I*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságtan 2. TK Budapest 2002, ISBN:9631026043*
- ❑ *Zombory L.: Elektromágneses terek. MK Budapest 2006, (www.electro.uni-miskolc.hu)*



Coupled Inductances


- Linear Transformers
- Ideal Transformers
- Three-Phase Transformers
- Transformer Applications

Self-Inductance (*Recall*)



$$v = N \frac{d\Phi}{dt} = N \frac{d\Phi}{di} \frac{di}{dt} = L \frac{di}{dt}$$
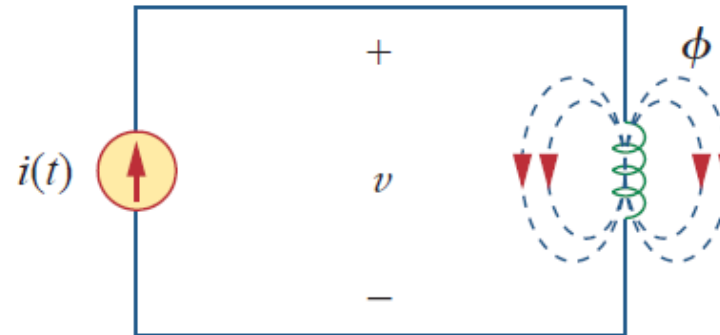
$$\text{Self-inductance } L = N \frac{d\Phi}{di}$$



Mutual Inductance (*Recall*)

$\Phi_1 = \Phi_{11} + \Phi_{12}$ Φ_{11} : links only coil 1, Φ_{12} : links both coils

$$v_1 = N_1 \frac{d\Phi_1}{dt} = N_1 \frac{d\Phi_{11}}{di_1} \frac{di_1}{dt} = L_1 \frac{di_1}{dt}$$

$$v_2 = N_2 \frac{d\Phi_{12}}{dt} = N_2 \frac{d\Phi_{12}}{di_1} \frac{di_1}{dt} = M_{21} \frac{di_1}{dt}$$


Mutual inductance $M_{21} = N_2 \frac{d\Phi_{12}}{di_1}$

$$\Phi_2 = \Phi_{21} + \Phi_{22}$$

$$v_2 = N_2 \frac{d\Phi_2}{dt} = N_2 \frac{d\Phi_{22}}{di_2} \frac{di_2}{dt} = L_2 \frac{di_2}{dt}$$


$$v_1 = N_1 \frac{d\Phi_{21}}{dt} = N_1 \frac{d\Phi_{21}}{di_2} \frac{di_2}{dt} = M_{12} \frac{di_2}{dt}$$

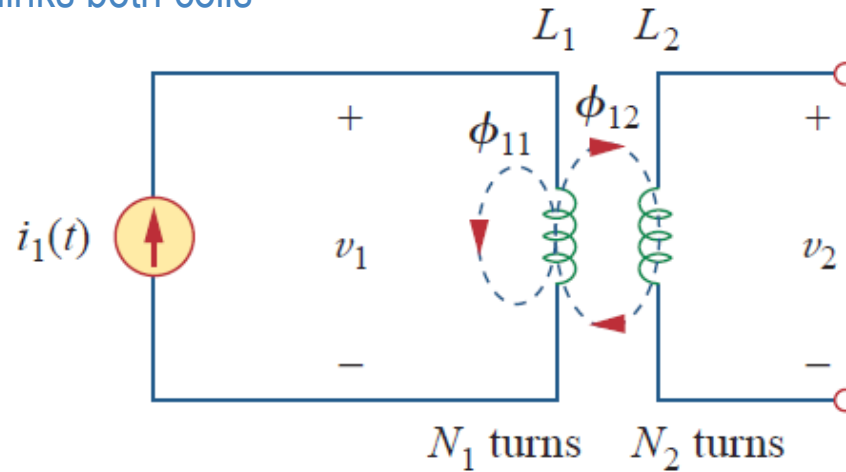Mutual inductance $M_{12} = N_1 \frac{d\Phi_{21}}{di_2}$



OC mutual (*induced*) voltage

$$v_2 = M_{21} \frac{di_1}{dt}$$

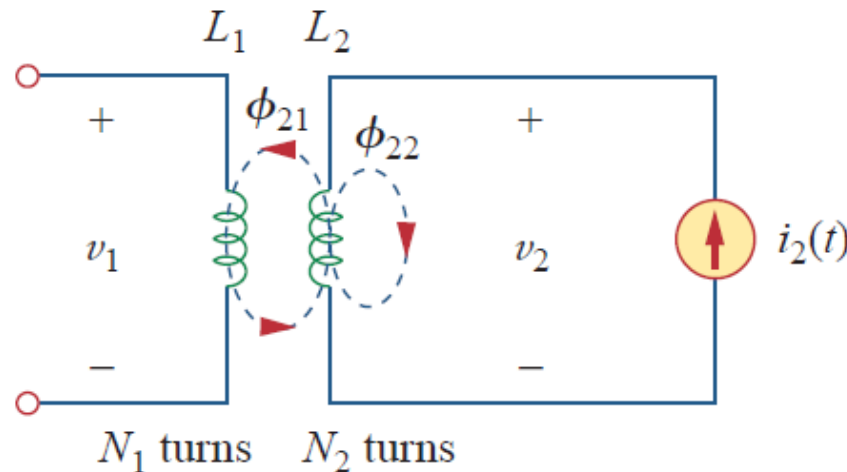


OC mutual (*induced*) voltage

$$v_1 = M_{12} \frac{di_2}{dt}$$




$(M_{12} = M_{21} = M)$

Dot Convention



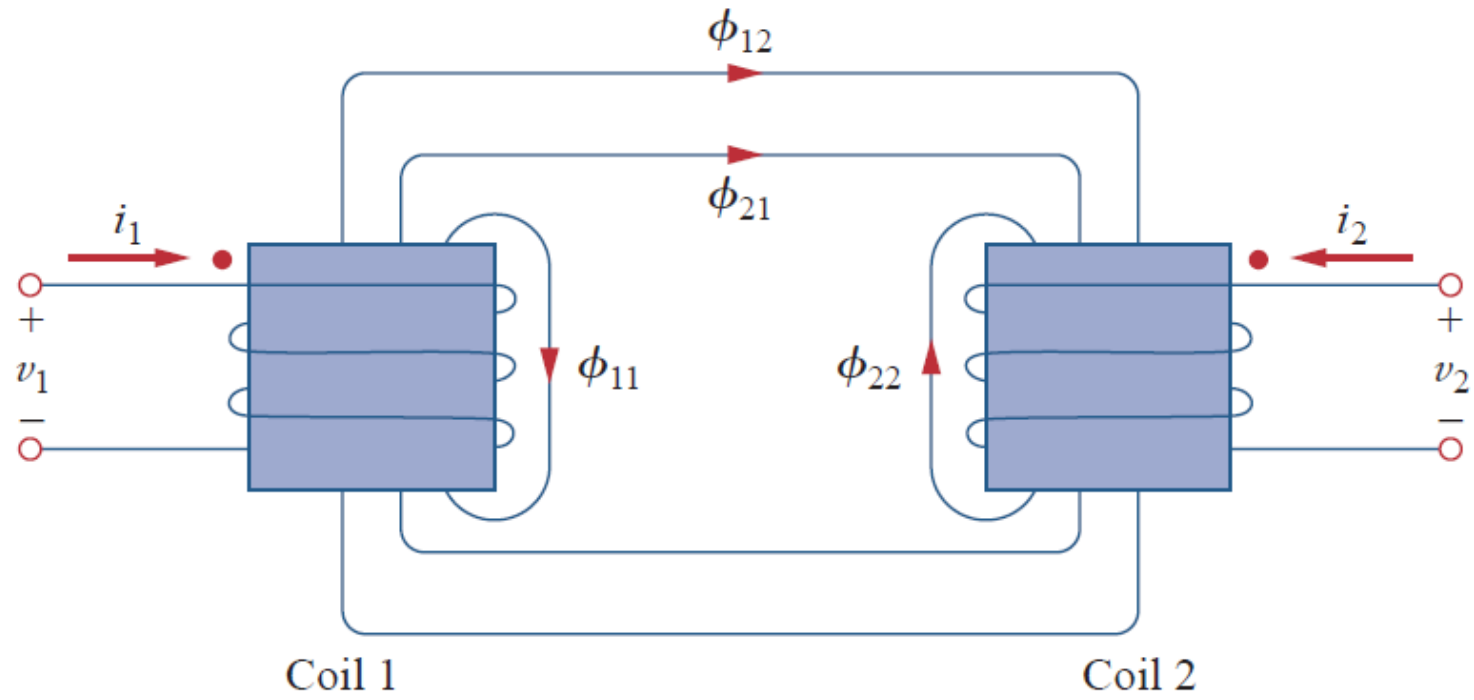


[current enters at dot] → [mutual voltage positive at dot]

Dot Convention - Examples

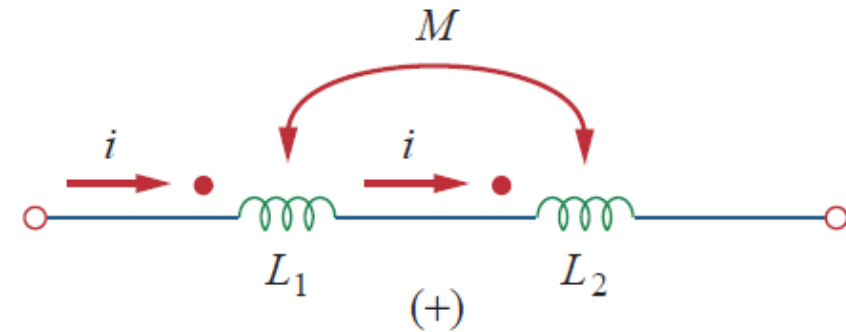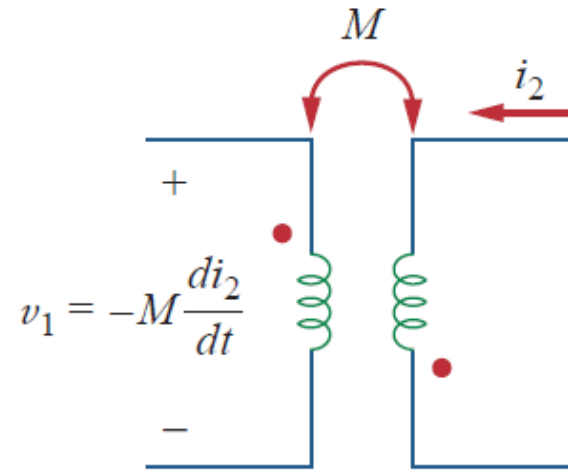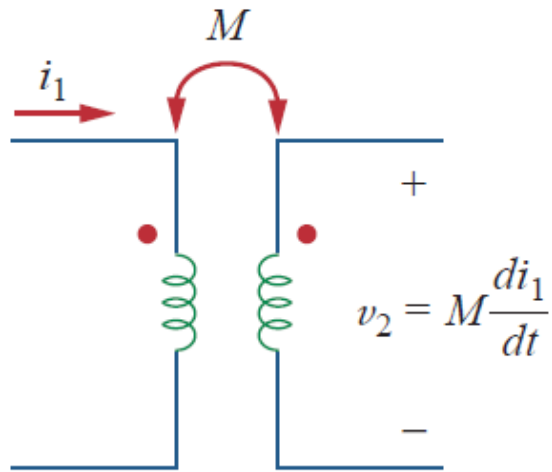


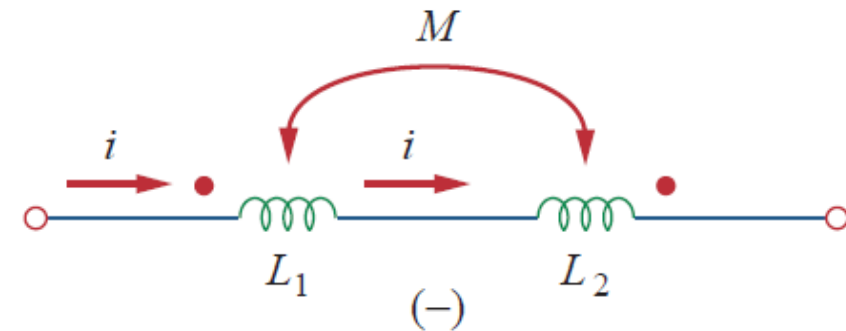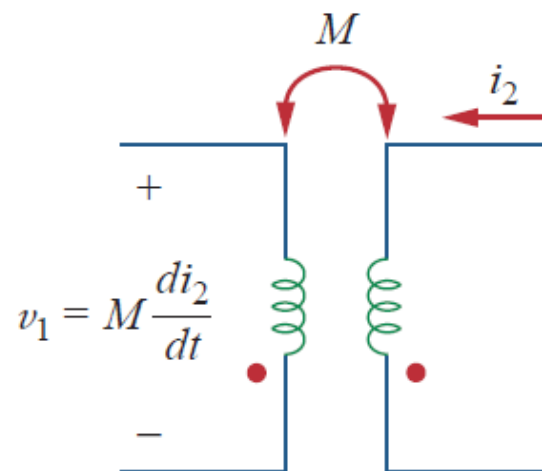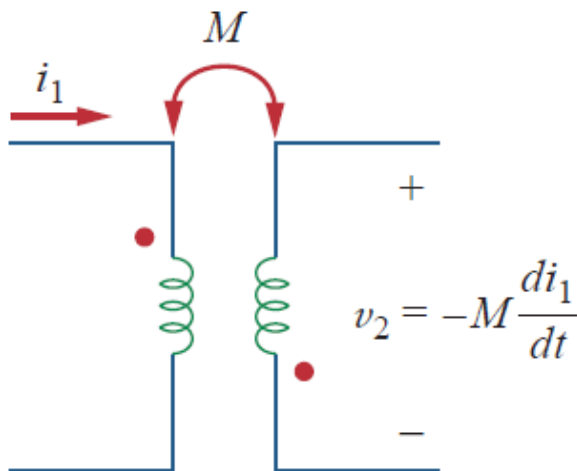Series-aiding connection $\rightarrow L = L_1 + L_2 + 2M$



Series-opposing connection $\rightarrow L = L_1 + L_2 - 2M$

Time and Frequency Domain Analysis

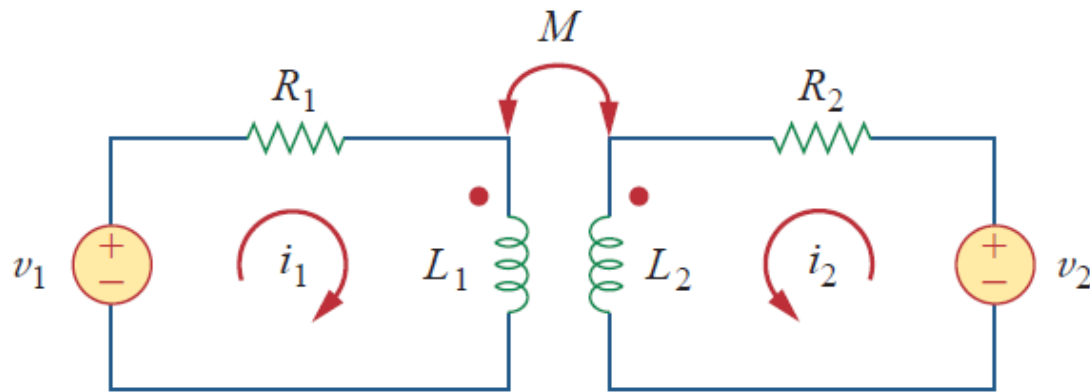


$$v_1 = i_1 R_1 + L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = i_2 R_2 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$\mathbf{V}_1 = (R_1 + j\omega L_1) \mathbf{I}_1 + j\omega M \mathbf{I}_2$$
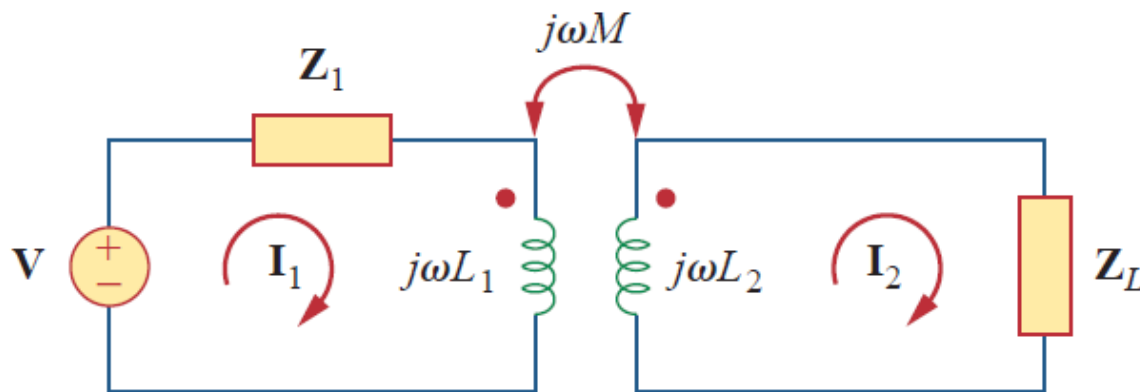
$$\mathbf{V}_2 = j\omega M \mathbf{I}_1 + (R_2 + j\omega L_2) \mathbf{I}_2$$




$$\mathbf{V} = (\mathbf{Z}_1 + j\omega L_1) \mathbf{I}_1 - j\omega M \mathbf{I}_2$$

$$0 = -j\omega M \mathbf{I}_1 + (\mathbf{Z}_L + j\omega L_2) \mathbf{I}_2$$

Energy in Coupled Circuit



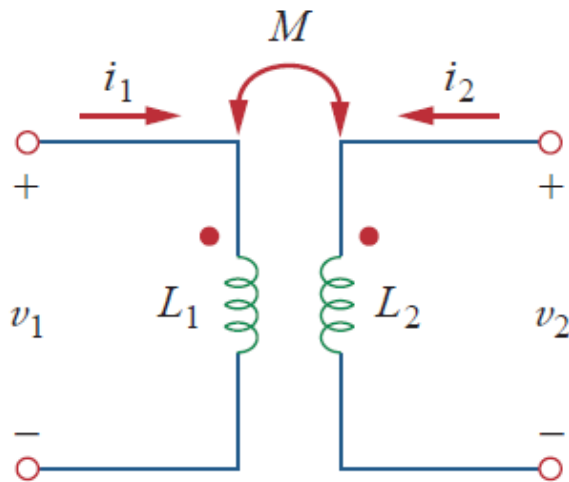Approaching in two steps... (1): $i_1 = (0 \rightarrow I_1), i_2 = 0 \rightarrow p_1(t) = v_1 i_1 = i_1 L_1 \frac{di_1}{dt}$



$$\rightarrow w_1 = \int p_1 dt = L_1 \int_0^{I_1} i_1 di_1 = \frac{1}{2} L_1 I_1^2$$

(2): $i_1 = I_1, i_2 = (0 \rightarrow I_2) \rightarrow p_2(t) = i_1 M \frac{di_2}{dt} + i_2 L_2 \frac{di_2}{dt}$

$$\rightarrow w_2 = \int p_2 dt = M I_1 \int_0^{I_2} di_2 + L_2 \int_0^{I_2} i_2 di_2 = M I_1 I_2 + \frac{1}{2} L_2 I_2^2$$

Total w (both of currents \rightarrow max value) $w = w_1 + w_2 = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 \pm M I_1 I_2 \dots (\pm \leftarrow \text{dot convention!})$

Coupling Coefficient



$$w = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 \pm Mi_1i_2$$

Passive circuit $\rightarrow \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 - Mi_1i_2 \geq 0$

$$(a - b)^2 = a^2 - 2ab + b^2$$

$$\rightarrow \frac{1}{2}(i_1\sqrt{L_1} - i_2\sqrt{L_2})^2 + i_1i_2(\sqrt{L_1L_2} - M) \geq 0$$

$$\rightarrow \sqrt{L_1L_2} - M \geq 0$$

$$M \leq \sqrt{L_1L_2} \rightarrow M = k\sqrt{L_1L_2}$$


$k \rightarrow$ measure of the magn. coupling bw. coils (0 - 1)

$$k = \frac{\Phi_{12}}{\Phi_1} = \frac{\Phi_{12}}{\Phi_{12} + \Phi_{11}} = \frac{\Phi_{21}}{\Phi_2} = \frac{\Phi_{21}}{\Phi_{21} + \Phi_{22}}$$

Coupling coefficient

- Perfekt coupling... ($k = 1$)
- Tight coupling ($k > 0.5$)
- Loose coupling ($k < 0.5$)

Air or ferrite core

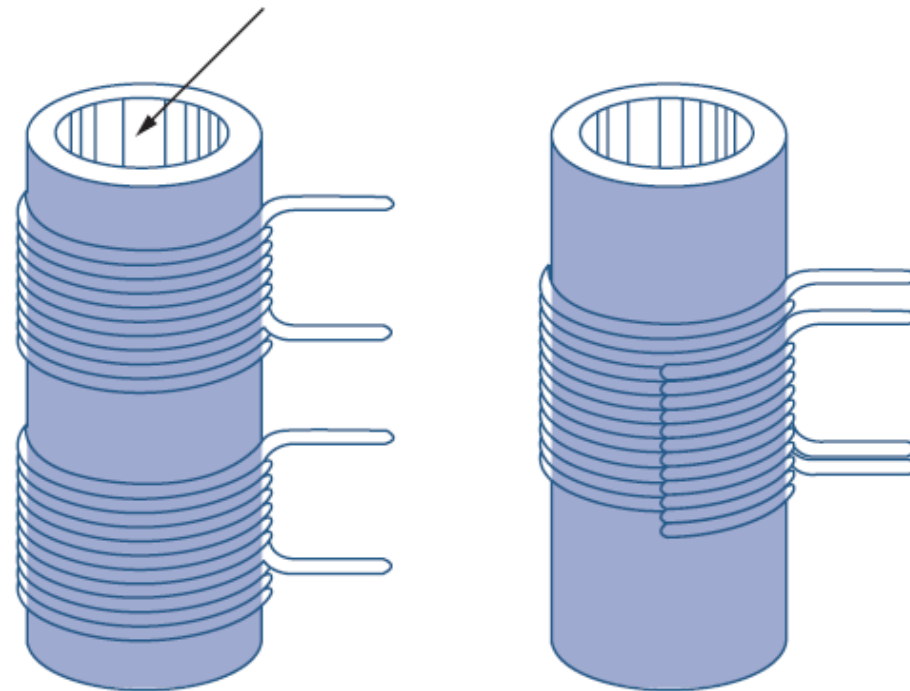




- Coupled Inductances
- Linear Transformers**
- Ideal Transformers
- Three-Phase Transformers
- Transformer Applications

Linear Transformers



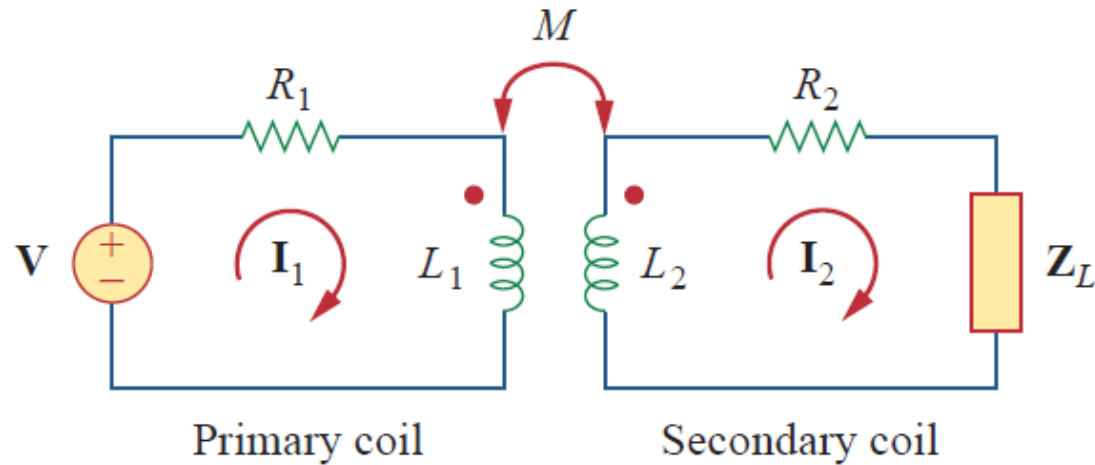Linear transformer $\rightarrow \Phi \sim I$



$$V = (R_1 + j\omega L_1)I_1 - j\omega M I_2$$

$$0 = -j\omega M I_1 + (R_2 + j\omega L_2 + Z_L)I_2$$

$$Z_{in} = \frac{V}{I_1} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

Primary impedance

$$Z_{PR} = R_1 + j\omega L_1$$


Reflected (coupled) impedance

$$Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$


Equivalent T - Circuit



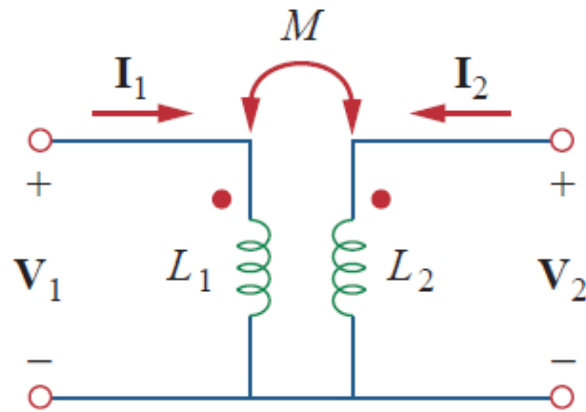Equivalent circuits → convenient analysis


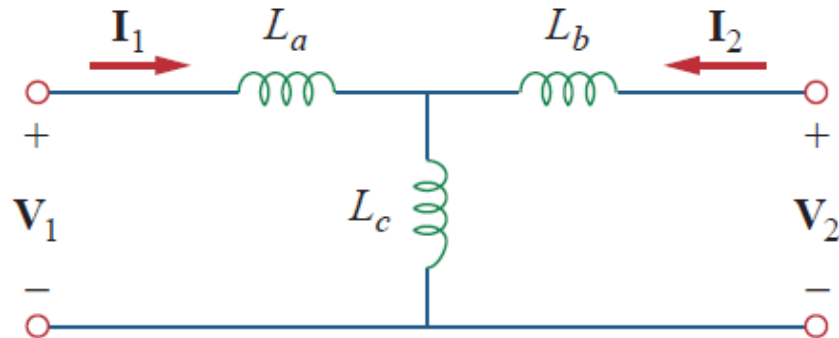
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



mesh analysis →

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$L_a = L_1 - M, \quad L_b = L_2 - M, \quad L_c = M$$

Equivalent Π - Circuit




Recall maths \rightarrow $M = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix}$


$$\Delta = a_{11}a_{22} - a_{12}a_{21}$$

$$M^{-1} = \frac{1}{\Delta} \text{adj}M = \begin{bmatrix} a_{22}/\Delta & -(a_{12}/\Delta) \\ -(a_{21}/\Delta) & a_{11}/\Delta \end{bmatrix}$$
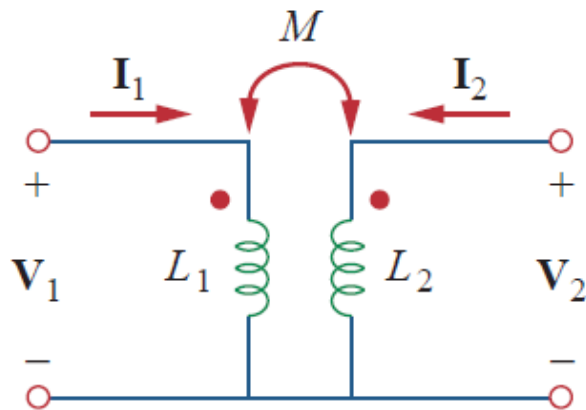
$$\text{adj}M = \begin{bmatrix} a_{22} & -a_{12} \\ -a_{21} & a_{11} \end{bmatrix}$$



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{L_2}{j\omega(L_1L_2 - M^2)} & \frac{-M}{j\omega(L_1L_2 - M^2)} \\ \frac{-M}{j\omega(L_1L_2 - M^2)} & \frac{L_1}{j\omega(L_1L_2 - M^2)} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

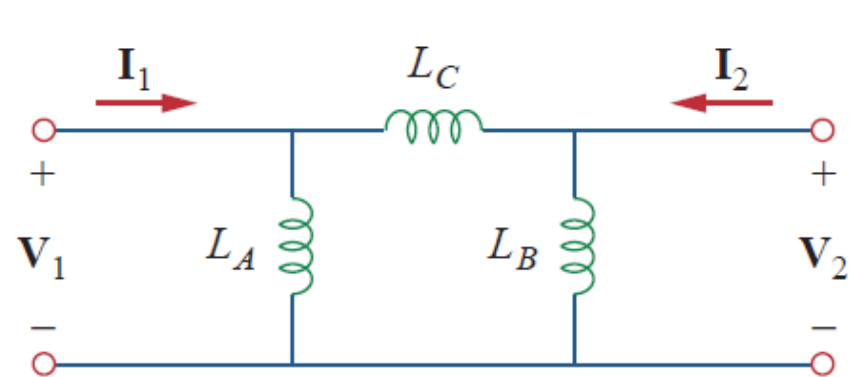

mesh analysis \rightarrow $\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{j\omega L_A} + \frac{1}{j\omega L_C} & -\frac{1}{j\omega L_C} \\ -\frac{1}{j\omega L_C} & \frac{1}{j\omega L_B} + \frac{1}{j\omega L_C} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$

$$L_A = \frac{L_1L_2 - M^2}{L_2 - M}, \quad L_B = \frac{L_1L_2 - M^2}{L_1 - M}, \quad L_C = \frac{L_1L_2 - M^2}{M}$$



- Coupled Inductances
- Linear Transformers
- Ideal Transformers**
- Three-Phase Transformers
- Transformer Applications

Ideal Transformers



Let's see... $k = 1 \leftarrow \mu \approx \infty$

$$(1): \mathbf{V}_1 = j\omega L_1 \mathbf{I}_1 + j\omega M \mathbf{I}_2 \rightarrow \mathbf{I}_1 = \frac{(\mathbf{V}_1 - j\omega M \mathbf{I}_2)}{j\omega L_1}$$

$$(2): \mathbf{V}_2 = j\omega M \mathbf{I}_1 + j\omega L_2 \mathbf{I}_2$$

$$(1 \rightarrow 2): \mathbf{V}_2 = j\omega L_2 \mathbf{I}_2 + \frac{M \mathbf{V}_1}{L_1} - \frac{j\omega M^2 \mathbf{I}_2}{L_1}$$


$$k = 1 \rightarrow M = \sqrt{L_1 L_2}$$

$$\mathbf{V}_2 = j\omega L_2 \mathbf{I}_2 + \frac{\sqrt{L_1 L_2} \mathbf{V}_1}{L_1} - \frac{j\omega L_1 L_2 \mathbf{I}_2}{L_1} = \sqrt{\frac{L_2}{L_1}} \mathbf{V}_1 = n \mathbf{V}_1$$

n (turns ratio) = constant, even if $L_1, L_2, M \rightarrow \infty$

Ideal transformer

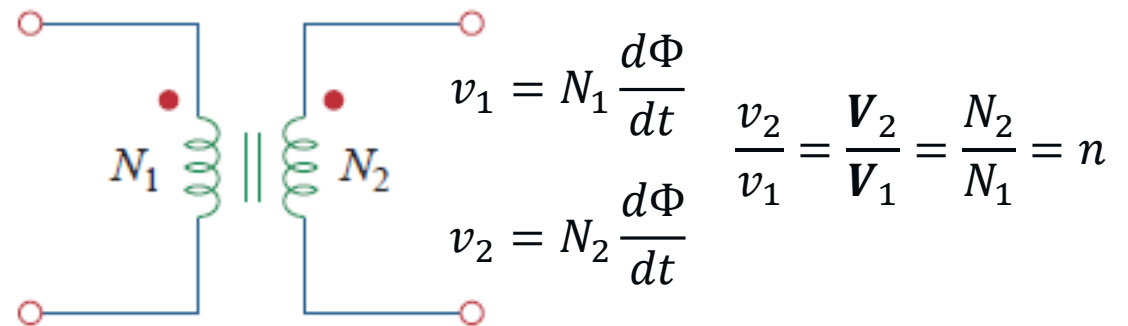- Coils have very large reactances $L_1, L_2, M \rightarrow \infty$
- Coupling coefficient is equal to unity $k = 1$
- Primary and secondary coils are lossless $R_1 = R_2 = 0$



- Isolation transformer $\rightarrow n = 1, (V_2 = V_1)$
- Step-up transformer $\rightarrow n > 1, (V_2 > V_1)$
- Step-down transformer $\rightarrow n < 1, (V_2 < V_1)$

Ideal Transformers



□ Power conservation $\rightarrow v_1 i_1 = v_2 i_2 \rightarrow V_1 I_1 = V_2 I_2$

$$\frac{I_1}{I_2} = \frac{V_2}{V_1} = n \rightarrow \frac{V_2}{V_1} = \frac{N_2}{N_1}, \quad \frac{I_2}{I_1} = \frac{N_1}{N_2}$$

□ Sign convention \rightarrow (four figures...)


□ Complex power ...

$$S_1 = V_1 I_1^* = \frac{V_2}{n} (n I_2)^* = V_2 I_2^* = S_2$$


□ Impedance transform

(imp. matching i.e. for max PWR transfer)
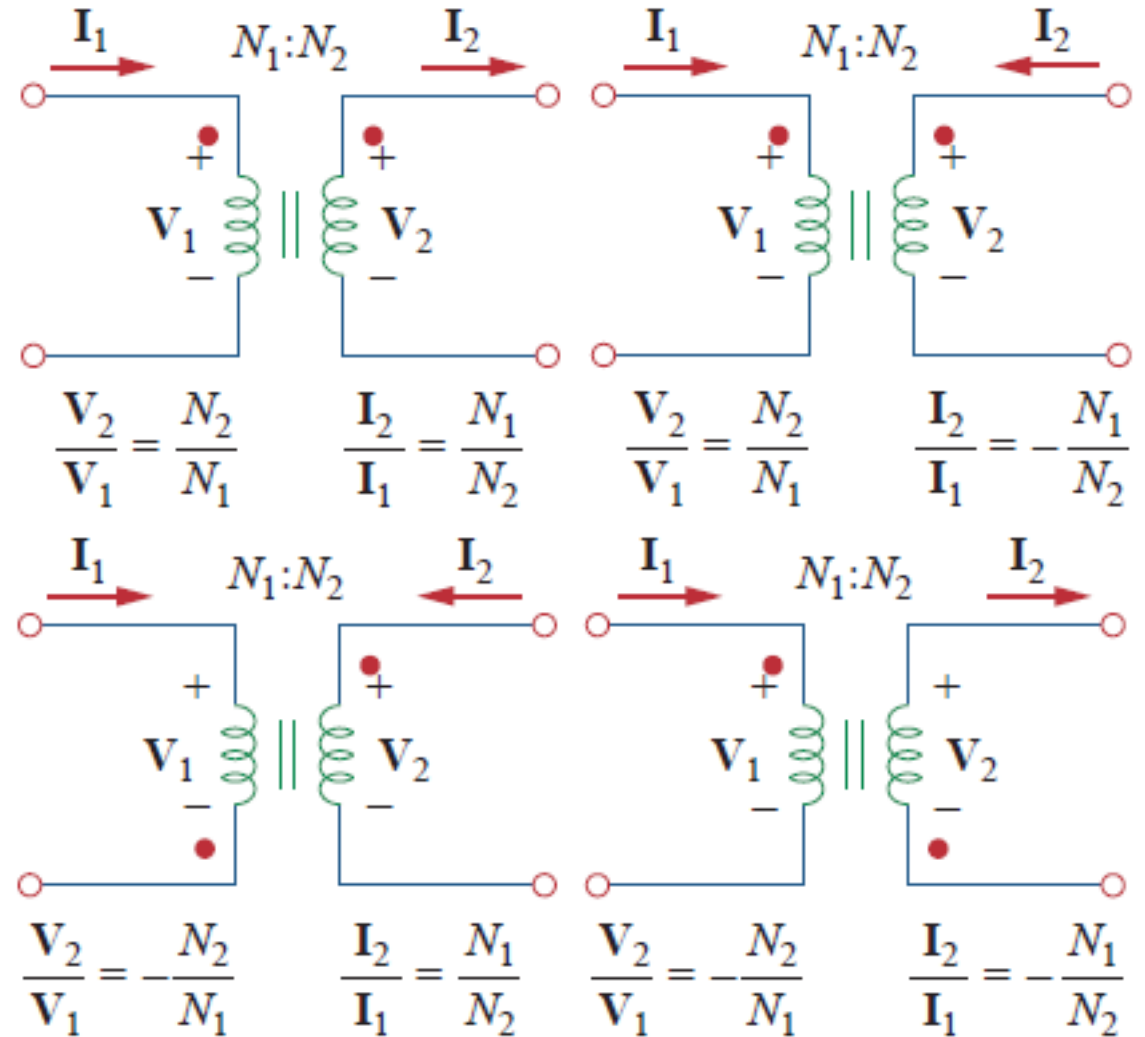
$$Z_{in} = \frac{V_1}{I_1} = \frac{1}{n^2} \frac{V_2}{I_2} = \frac{Z_L}{n^2}$$



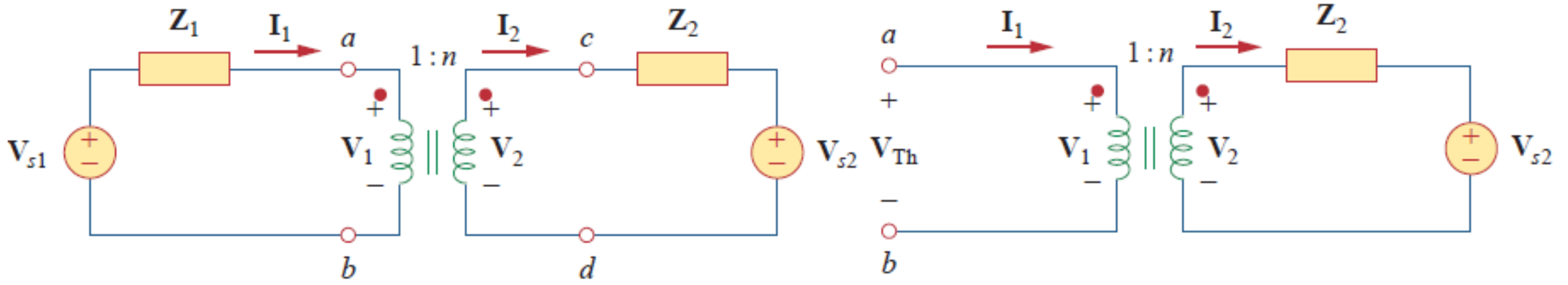
Ideal Transformers – Equivalent Circuit 1



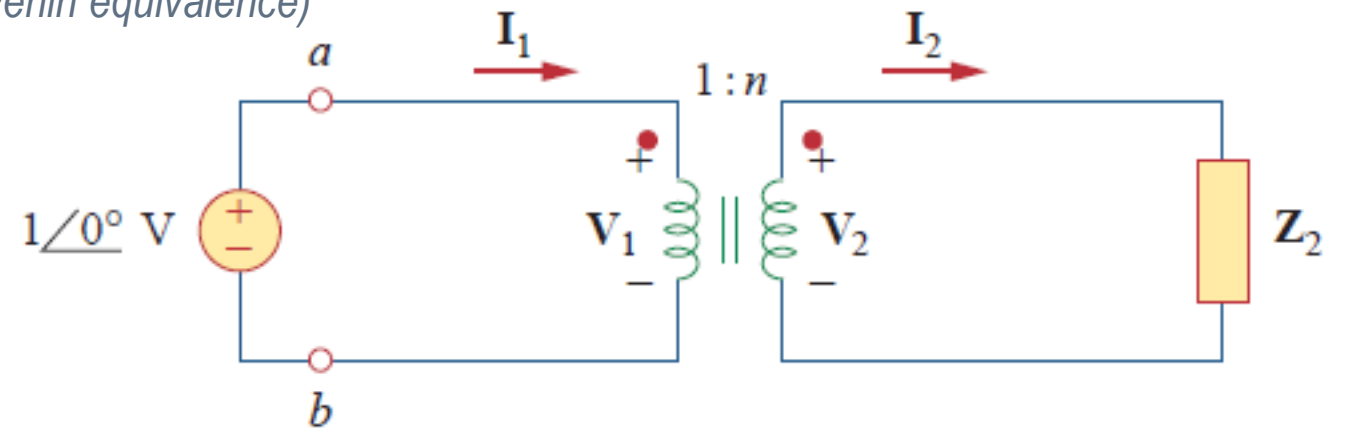
(1) Reflecting secondary to the primer circuit (*Thevenin equivalence*)

$$I_1 = 0 \rightarrow I_2 = 0 \rightarrow V_{Th} = V_1 = \frac{V_2}{n} = \frac{V_{s2}}{n}$$

$$Z_{Th} = \frac{V_1}{I_1} = \frac{V_2/n}{nI_2} = \frac{Z_2}{n^2}, \quad V_2 = Z_2 I_2$$





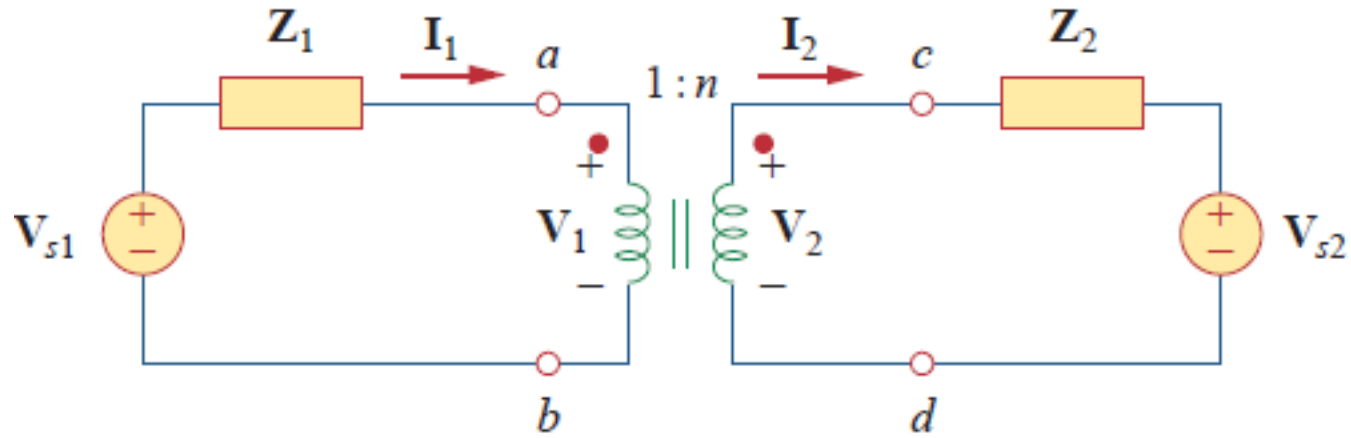Ideal Transformers – Equivalent Circuit 2



(1) Reflecting secondary to the primary circuit (result)

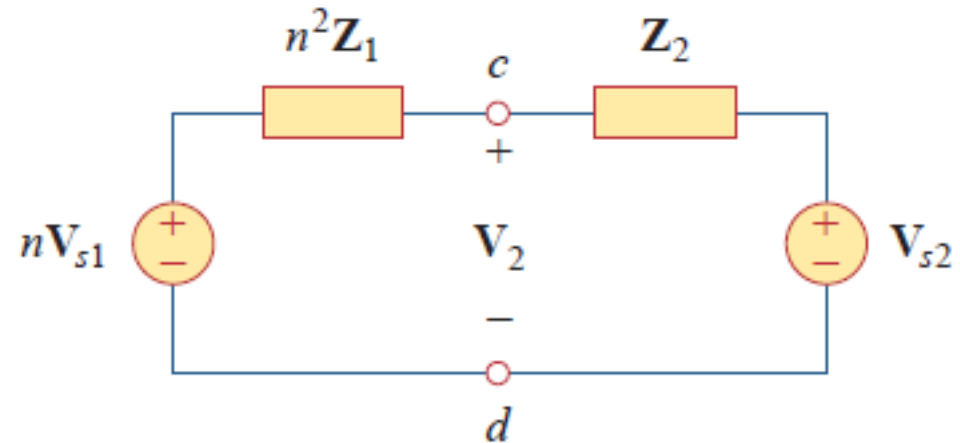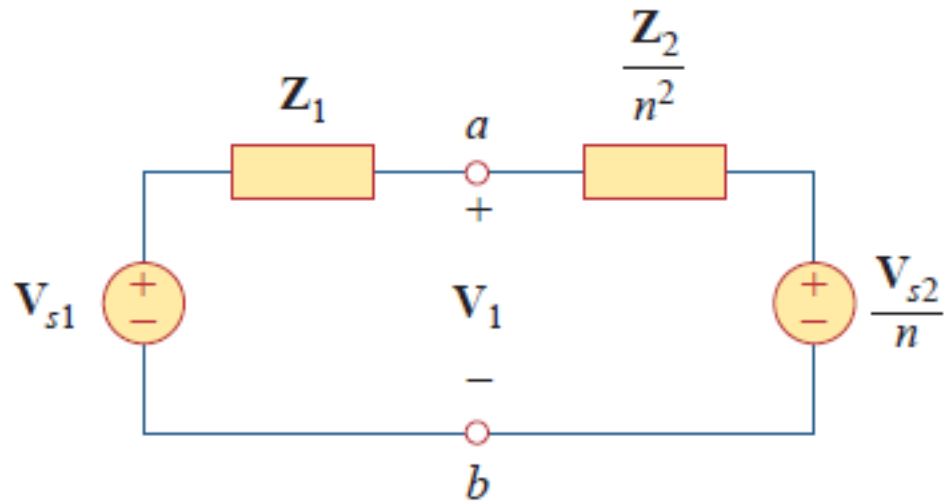(2) Reflecting primary to the secondary circuit





Ideal Autotransformers



Autotransformer → single coil with (variable) tap

❑ Electric isolation is lost

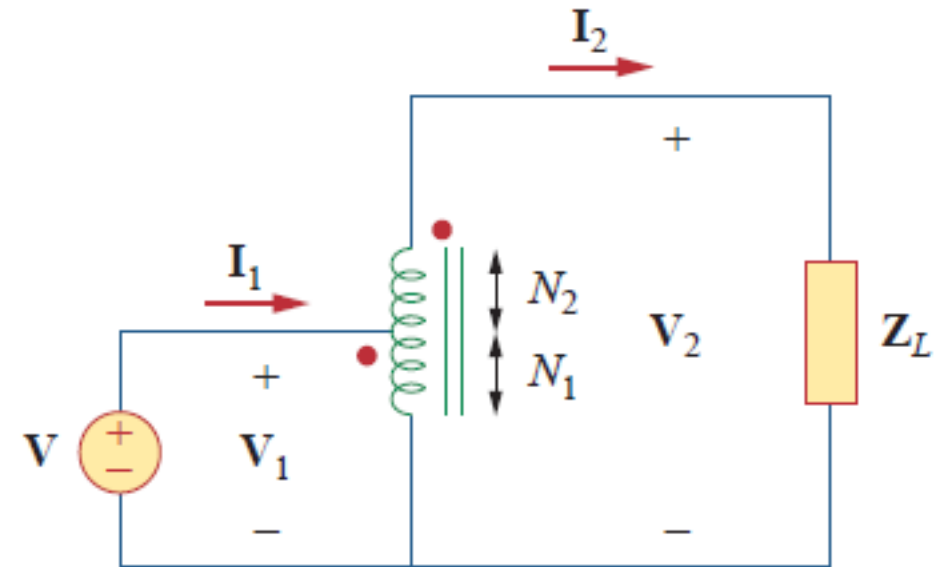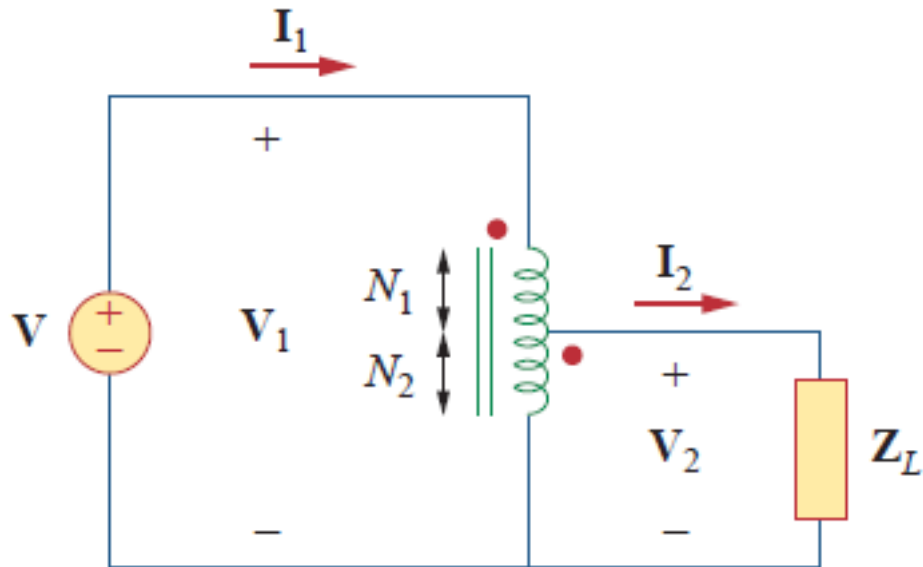❑ Step-down transformer → ← Step-up transformer



$$\frac{V_1}{V_2} = \frac{N_1 + N_2}{N_2} = 1 + \frac{N_1}{N_2}, \quad S_1 = S_2 \rightarrow \frac{I_1}{I_2} = \frac{N_2}{N_1 + N_2}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_1 + N_2}, \quad S_1 = S_2 \rightarrow \frac{I_1}{I_2} = \frac{N_1 + N_2}{N_1} = 1 + \frac{N_2}{N_1}$$



- Coupled Inductances
- Linear Transformer
- Ideal Transformer
- Three-Phase Transformers**
- Transformer Applications

Three-Phase Transformers 1




Three-phase transformer


- ❑ Smaller and cheaper than *transformer bank*
- ❑ Four connections (YY, DD, DY, YD)

❑ For any connection $P_{total} = S_{total} \cos \theta = \sqrt{3}V_L I_L \cos \theta$ $Q_{total} = S_{total} \sin \theta = \sqrt{3}V_L I_L \sin \theta$

$$S_{total} = \sqrt{3}V_L I_L$$

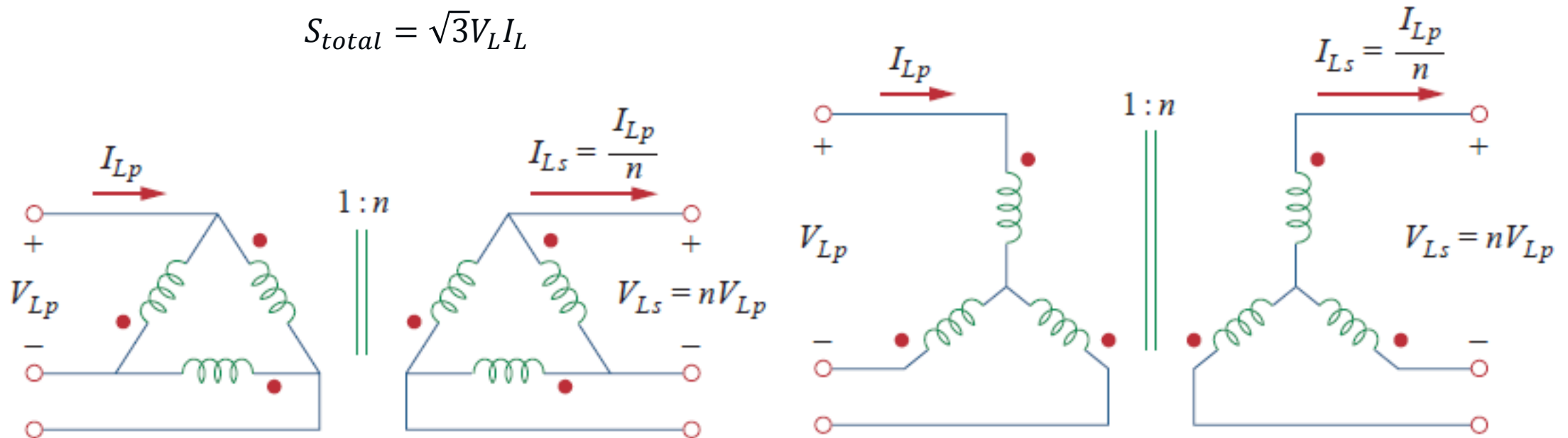




Three-Phase Transformers 2

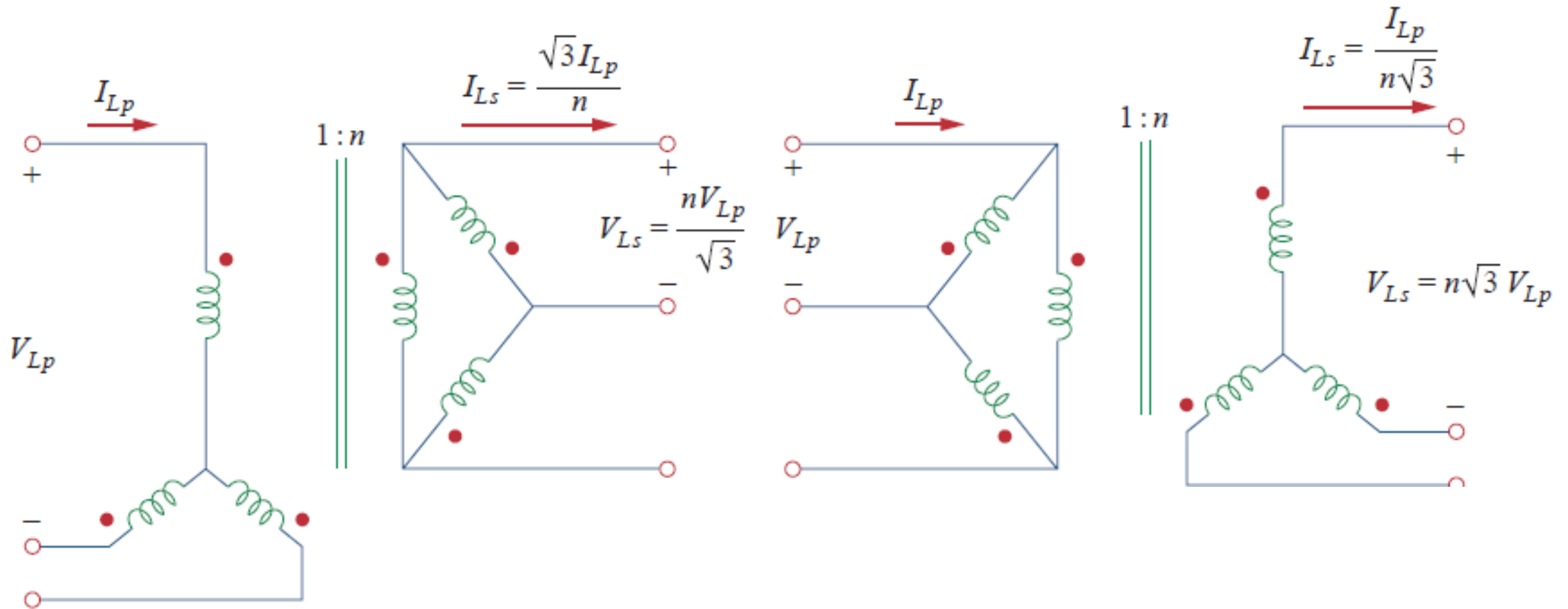



- Coupled Inductances
- Linear Transformer
- Ideal Transformer
- Three-Phase Transformers
- Transformer Applications**


App. – Isolation Device

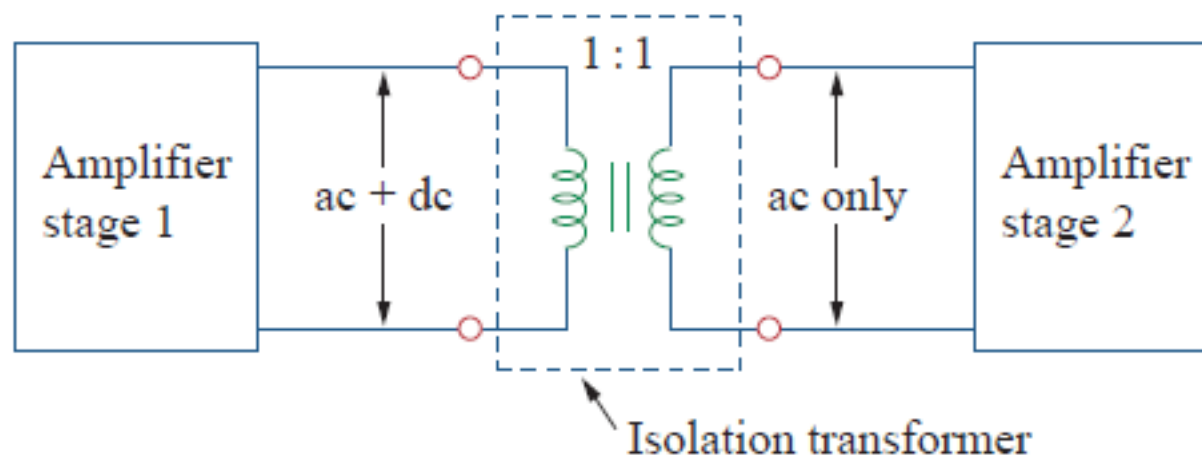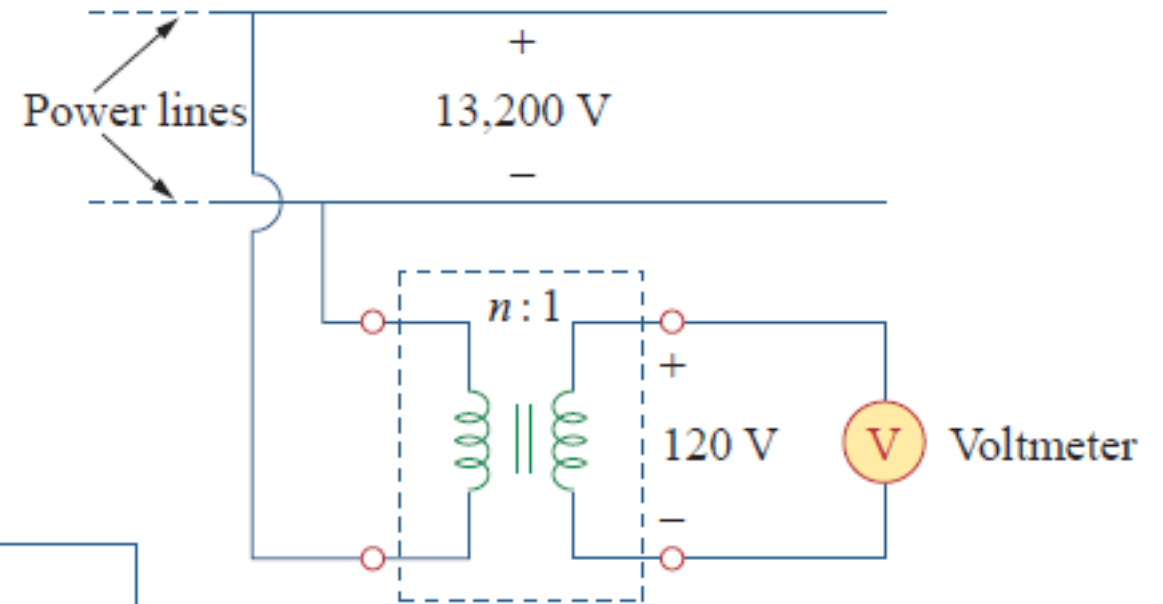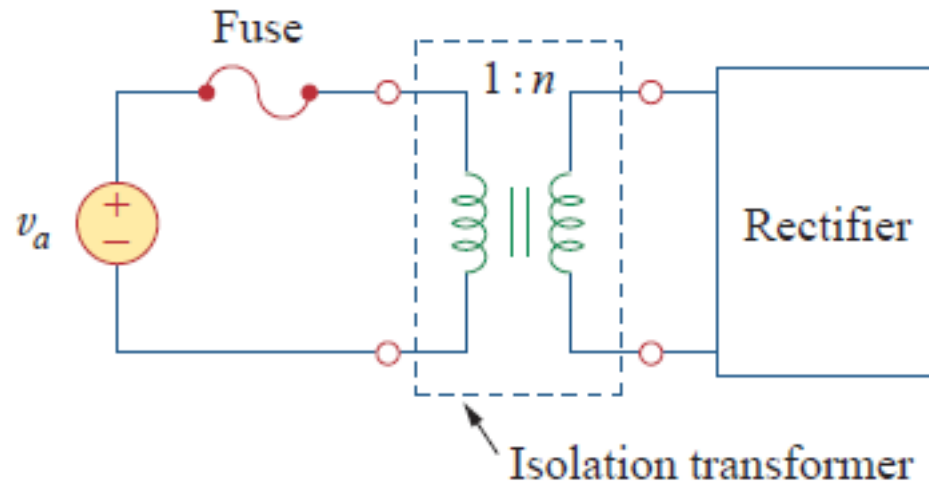

App. – Matching Device



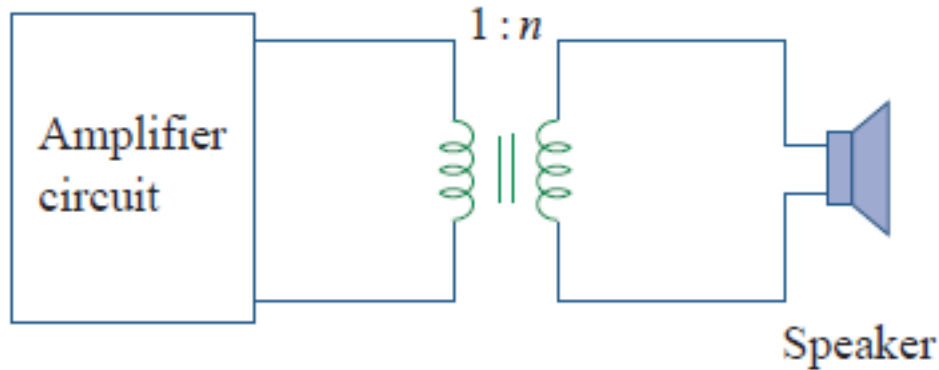Matching transformer for maximum power transfer




$$Z_{Th} = \frac{Z_L}{n^2} \rightarrow n = \sqrt{\frac{Z_L}{Z_{Th}}}$$

$$I_p = \frac{V_{Th}}{Z_{Th} + Z_L/n^2} \rightarrow I_s = \frac{I_p}{n} = \frac{V_{Th}/n}{Z_{Th} + Z_L/n^2}$$

□ With matching transformer...

Equivalent circuit

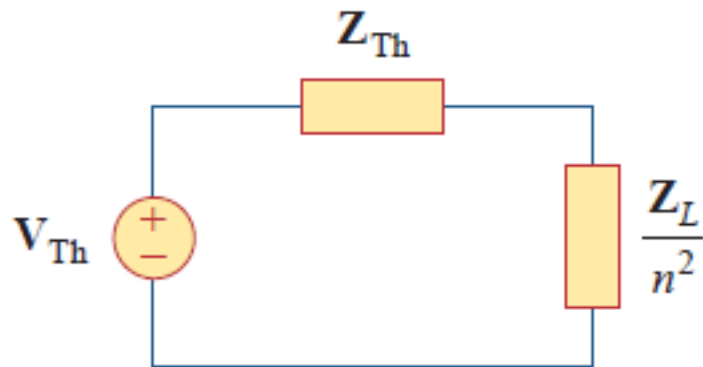


$$P_L = I_s^2 Z_L = \left(\frac{V_{Th}/n}{Z_{Th} + Z_L/n^2} \right)^2 Z_L = \left(\frac{nV_{Th}}{n^2 Z_{Th} + Z_L} \right)^2 Z_L$$

□ Without matching transformer...

$$P_L = I^2 Z_L = \left(\frac{V_{Th}}{Z_{Th} + Z_L} \right)^2 Z_L$$

App. - Power Distribution

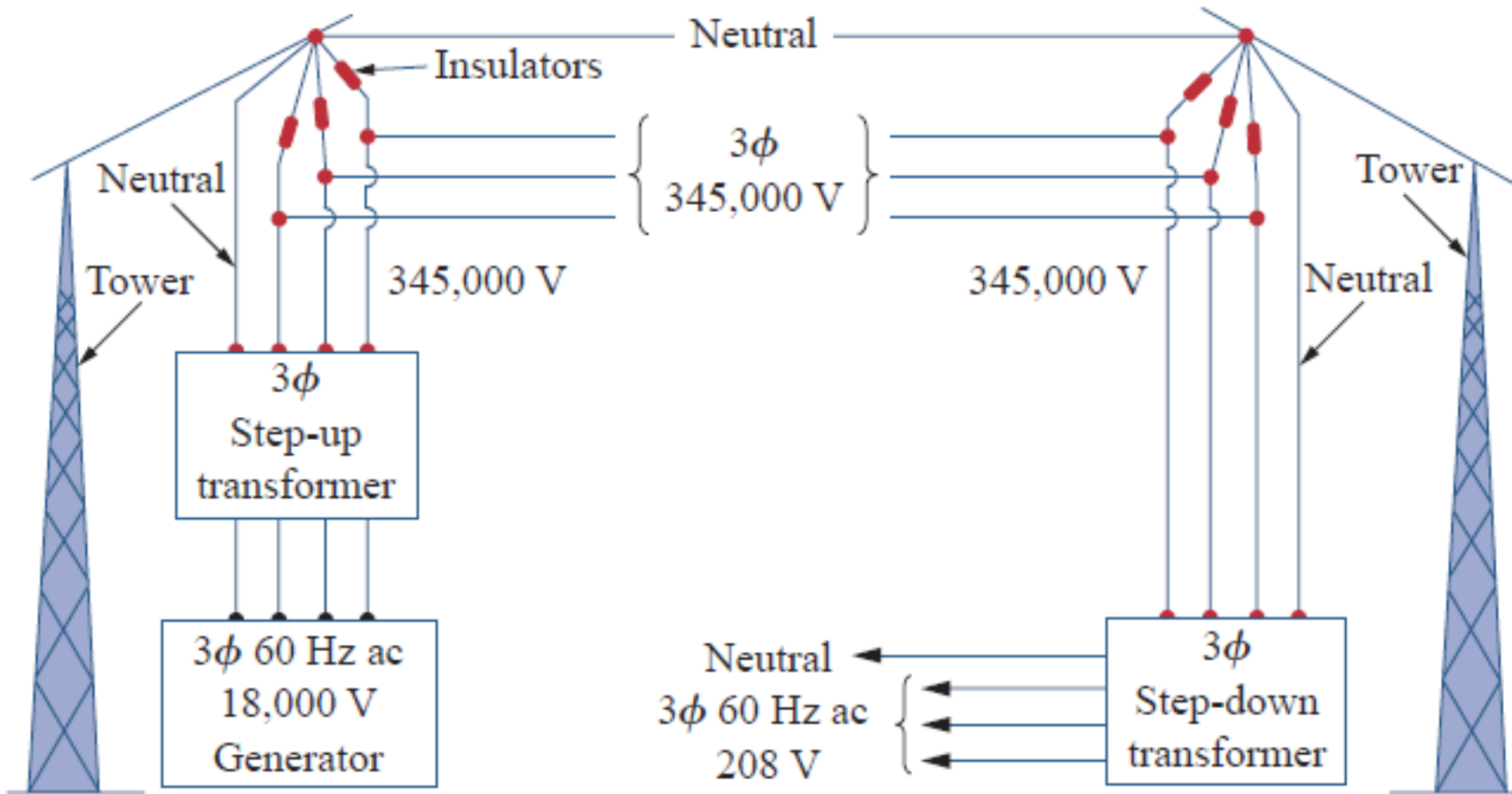

$$P_{loss} = I^2 R_w = \frac{(\Delta V)^2}{R_w}$$

$$\Delta V = V_{send} - V_{rec}$$

Step-up transforming...

$$V_{send} \approx V_{rec} \rightarrow P_{loss} \approx 0$$

Questions

