




DR. GYURCSEK ISTVÁN

# Second-Order Dynamic Circuits

## *Sources and additional materials (recommended)*

- ❑ *Dr. Gyurcsek – Dr. Elmer: Theories in Electric Circuits, GlobeEdit, 2016, ISBN:978-3-330-71341-3*
- ❑ *Ch. Alexander, M. Sadiku: Fundamentals of Electric Circuits, 6th Ed., McGraw Hill NY 2016, ISBN: 978-0078028229*
- ❑ *Prof. Townsend: Series RC, RL, and RLC Circuits, MTH 352 Fall 2005*
- ❑ *Parallel RC, RL, and RLC Circuits MTH 352 Fall 2005*
- ❑ *<http://www.ece.tufts.edu/~hopwood/downloads/es3/SecondOrderCircuits.ppt>*
- ❑ *<https://voer.edu.vn/c/second-order-circuits/24240886/072b46c4>*
- ❑ *Ormándlaky Zsolt: Átmeneti jelenségek*

# Introduction

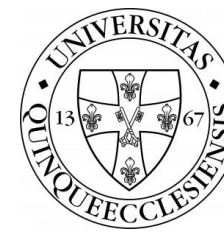

## Static circuit

- ❑ COND1 - no storage element
- ❑ algebraic equations
- ❑ *DC circuit*

## Dynamic circuit

- ❑ COND1: capacitor **and/or** inductor
- ❑ COND2: time var. source **and/or** time var. Structure (*switch*)
- ❑ differential equations
- ❑ *AC* → *part of DYN*


## Transient Analysis 2

### *Second-order circuit*





- ❑ *Two independent (equivalent) reactive components*
- ❑ *Characterized by 2nd-order diff. equations*

Mech. Component	Electric Component
Mass ( $m$ )	Inductor ( $L$ )
Spring ( $k$ )	Capacitor ( $C$ )
Shock absorber ( $B$ )	Resistor ( $R$ )
Force ( $F$ )	Voltage ( $V$ )
Velocity ( $dx/dt$ )	Current ( $dq/dt$ )

**Mechanical – electrical analogy**

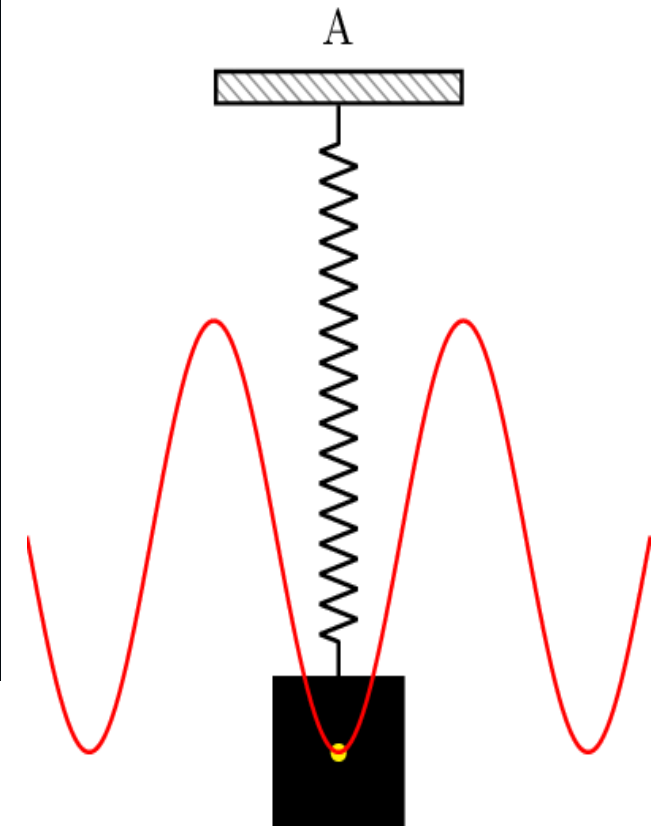

# Second-Order Circuits

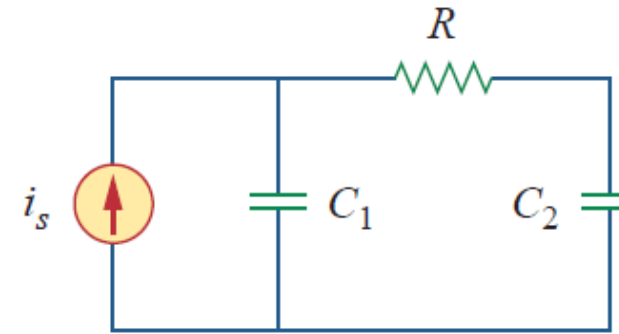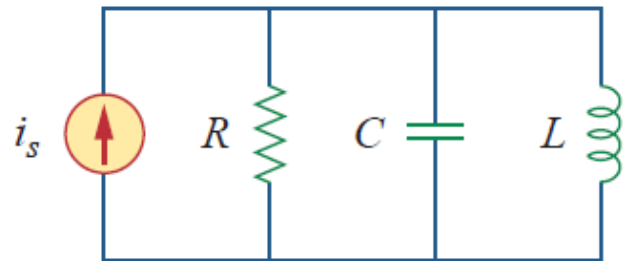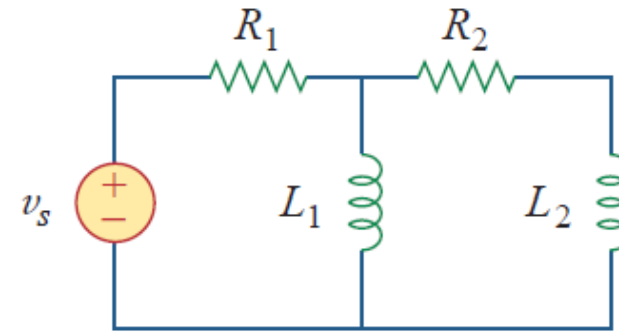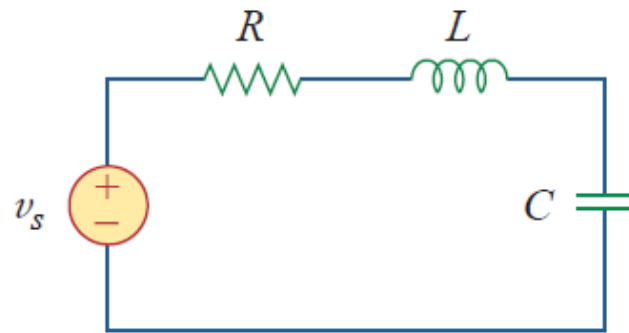





## **The Source-Free Series RLC Circuit**

- Duality in Electric Circuits
- The Source-Free Parallel RLC Circuit
- Step Response of a Series RLC Circuit
- Step Response of a Parallel RLC Circuit
- General Second-Order Circuits

# Source-Free Series RLC Circuit

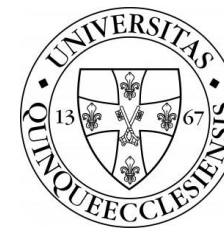

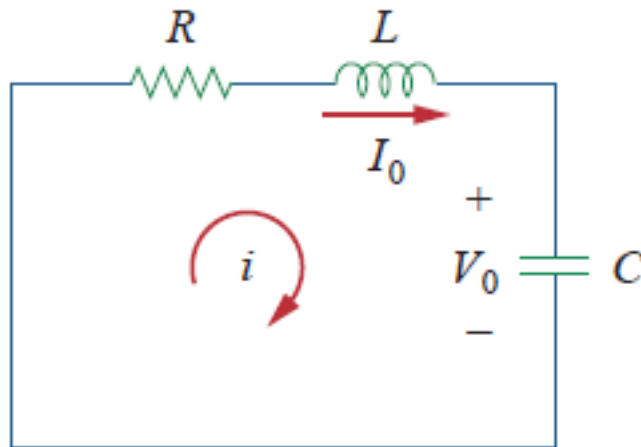- ❑ Two separate 'legs' of initial energy → **two initial conditions**
- ❑ To solve second-order equation there must be two initial values (*known from maths*)



$$v_L = L \frac{di}{dt}, \quad i = C \frac{dv_C}{dt}$$

$$v_L + v_R + v_C = 0 \quad v_L + RC \frac{dv_C}{dt} + v_C = 0$$

$$v_L = LC \frac{d^2 v_C}{dt^2} \quad LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = 0$$

$$w_L(0) = \frac{1}{2} L i_L^2(0) \rightarrow i_L(0) = I_0$$

$$w_C(0) = \frac{1}{2} C v_C^2(0) \rightarrow v_C(0) = V_0$$

$$\frac{dv_C(0)}{dt} = \frac{1}{C} i(0) = \frac{I_0}{C}$$

**'Complementary' solution**

$$v_C(t) = K e^{st}$$

- ❑  $K$  - from initial conditions
- ❑  $s$  - from coefficients of diff. equation

# Source-Free Series RLC Circuit



$$LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = 0$$

□ Complementary solution form

$$v_C(t) = K e^{st} \rightarrow K e^{st} (LCs^2 + RCs + 1) = 0$$

□ Characteristic equation

$$LCs^2 + RCs + 1 = 0$$

□ Quadratic characteristic eq.  $\rightarrow$  two roots

$$s_{1,2} = \frac{-RC \pm \sqrt{(RC)^2 - 4LC}}{2LC} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$


□ Introducing damping factor and natural frequency

$$\delta = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}} \rightarrow s_{1,2} = -\delta \pm \sqrt{\delta^2 - \omega_0^2}$$

□ Each root contributes in complementary solution

$$v_C(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

# Source-Free Series RLC Circuit

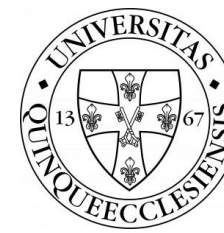



$$s_{1,2} = -\delta \pm \sqrt{\delta^2 - \omega_0^2}$$

CASE A	CASE B	CASE C	CASE D
$\delta^2 - \omega_0^2 > 0$	$\delta^2 - \omega_0^2 = 0$	$\delta^2 - \omega_0^2 < 0$	$\delta = 0$
$s_1 = -\delta + \sqrt{\delta^2 - \omega_0^2}$ $s_2 = -\delta - \sqrt{\delta^2 - \omega_0^2}$	$s_1 = s_2 = -\delta$	$s_1 = -\delta - j\sqrt{\omega_0^2 - \delta^2}$ $s_2 = -\delta + j\sqrt{\omega_0^2 - \delta^2}$	$s_1 = +j\omega_0$ $s_2 = -j\omega_0$
Two real unequal roots Overdamped circuit	Two real equal roots Critically damped circuit	Two cpx. conjugate roots Underdamped circuit	Two imaginary roots Undamped circuit (free-oscillation)
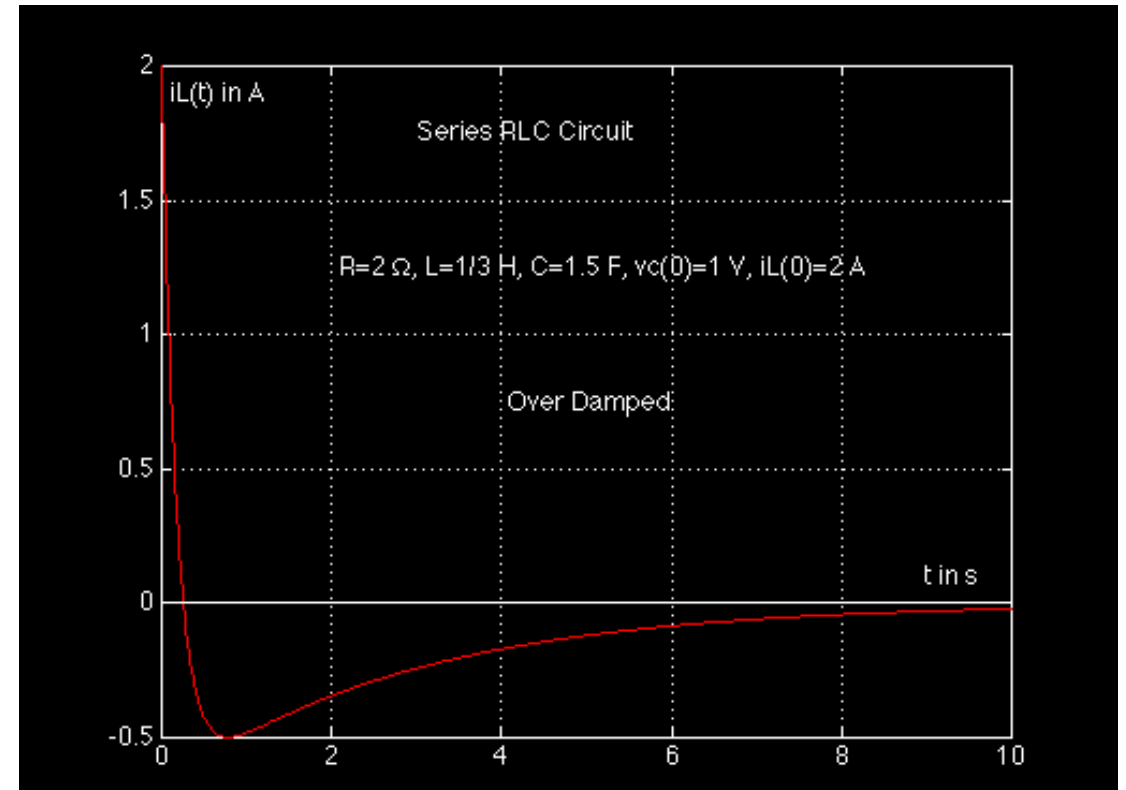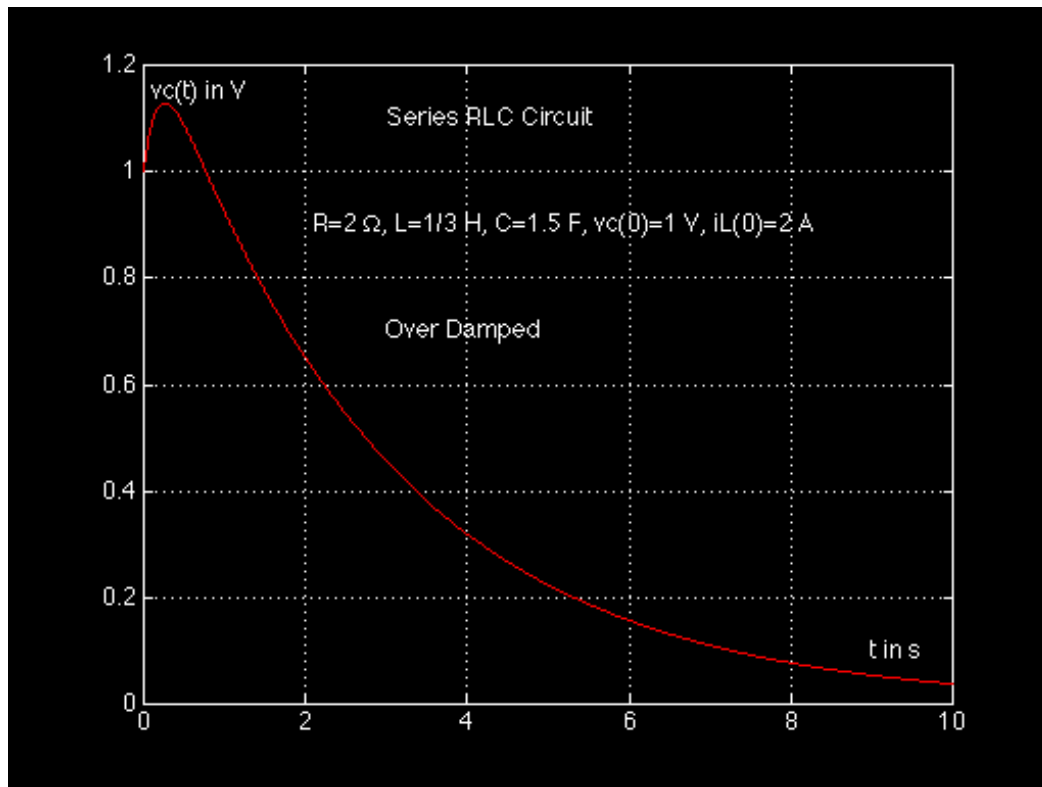
# Case A – Overdamped Circuit



$$\delta^2 - \omega_0^2 > 0 \rightarrow s_{1,2} = -\delta \pm \sqrt{\delta^2 - \omega_0^2} \rightarrow v_C(t) = K_1 e^{(-\delta + \sqrt{\delta^2 - \omega_0^2})t} + K_2 e^{(-\delta - \sqrt{\delta^2 - \omega_0^2})t}$$




$$v_C(t) = (1.318e^{-0.35t} - 0.318e^{-5.646t}) V, \quad i_L(t) = (-0.7e^{-0.35t} + 2.7e^{-5.646t}) A$$



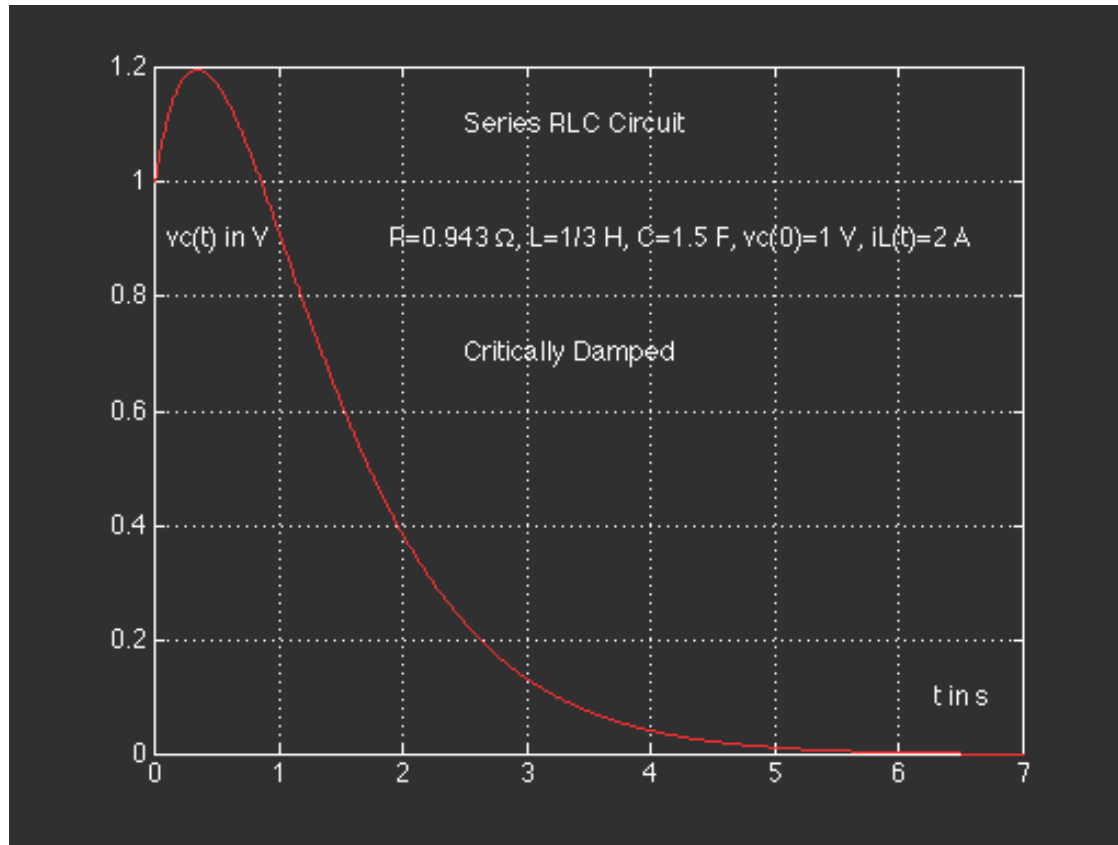
# Case B – Critically Damped Circuit



$$\delta^2 - \omega_0^2 = 0 \rightarrow s_1 = s_2 = -\delta \rightarrow v_C(t) = K_1 e^{-\delta t} + K_2 t e^{-\delta t}$$


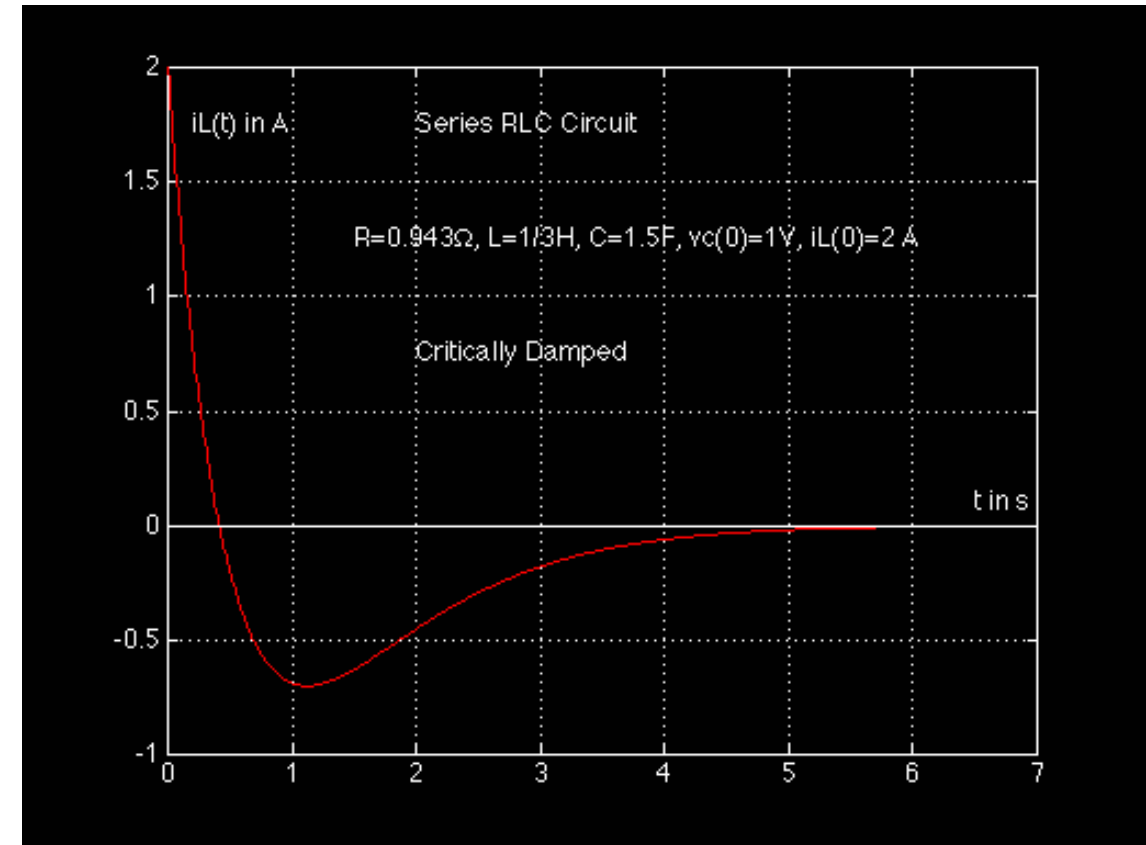
$$v_C(t) = (1.0e^{-1.414t} + 2.75te^{-1.414t}) \text{ V},$$





$$i_L(t) = (2e^{-1.414t} - 5.83te^{-1.414t}) \text{ A}$$
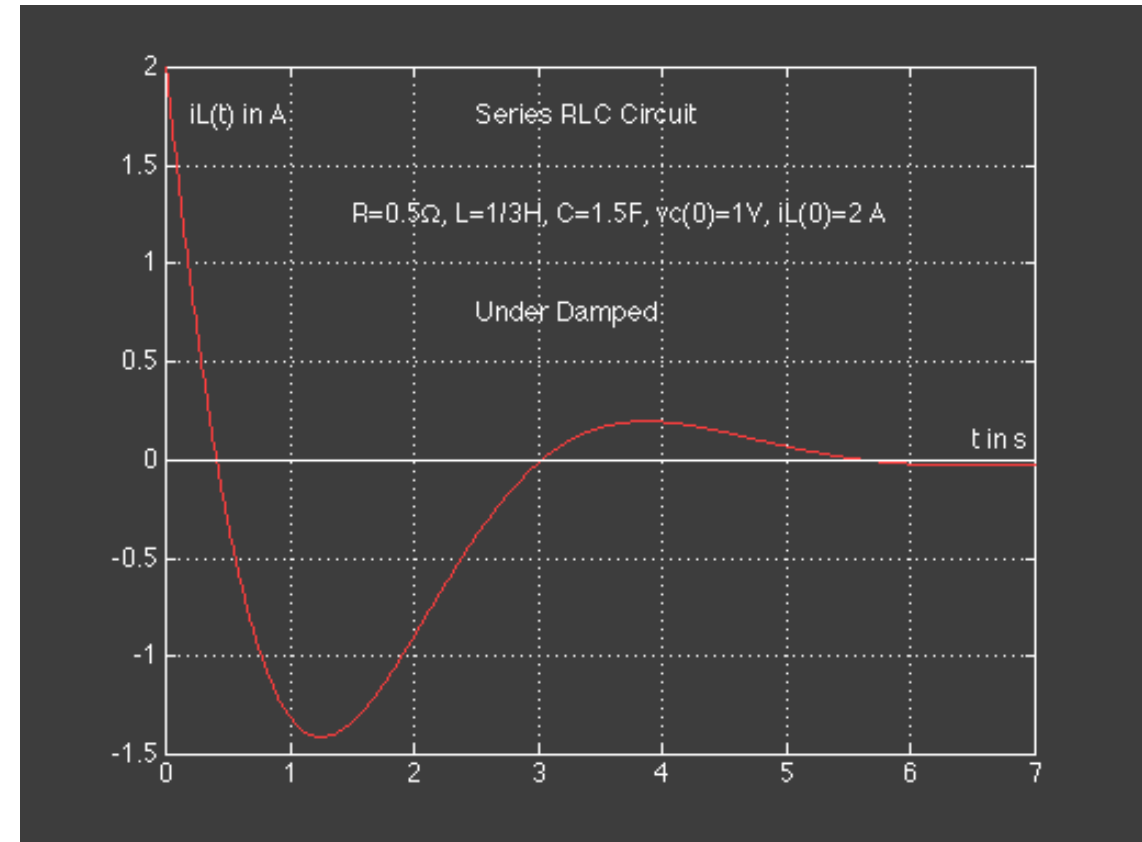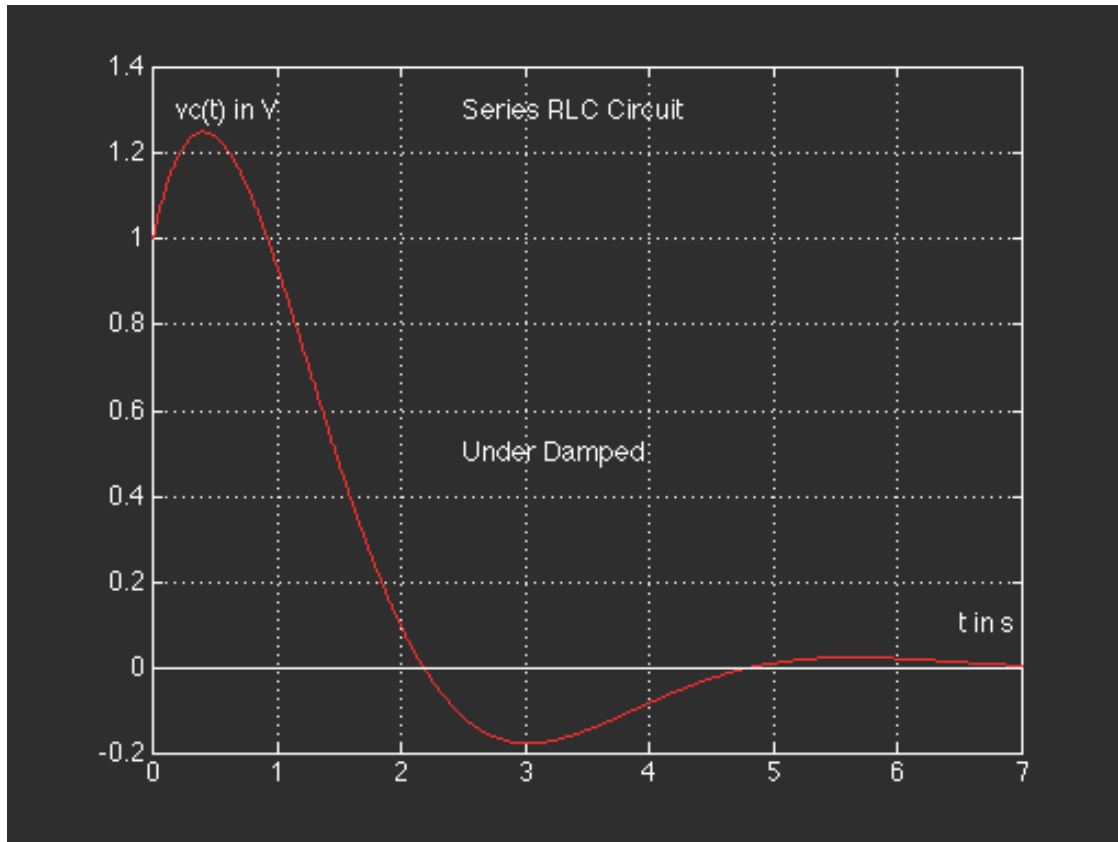
# Case C – Underdamped Circuit



$$\delta^2 - \omega_0^2 < 0 \rightarrow s_{1,2} = -\delta \pm j\sqrt{\omega_0^2 - \delta^2} = -\delta \pm j\omega_d \rightarrow v_C(t) = e^{-\delta t}(A_1 \cos \omega_d t + A_2 \sin \omega_d t) = Ae^{-\delta t} \cos(\omega_d t + \varphi)$$





$$v_C(t) = 2e^{-0.75t} \cos(1.2t - 1.047) \text{ V}, \quad i_L(t) = 4.25e^{-0.75t} \cos(1.2t + 1.081) \text{ A}$$
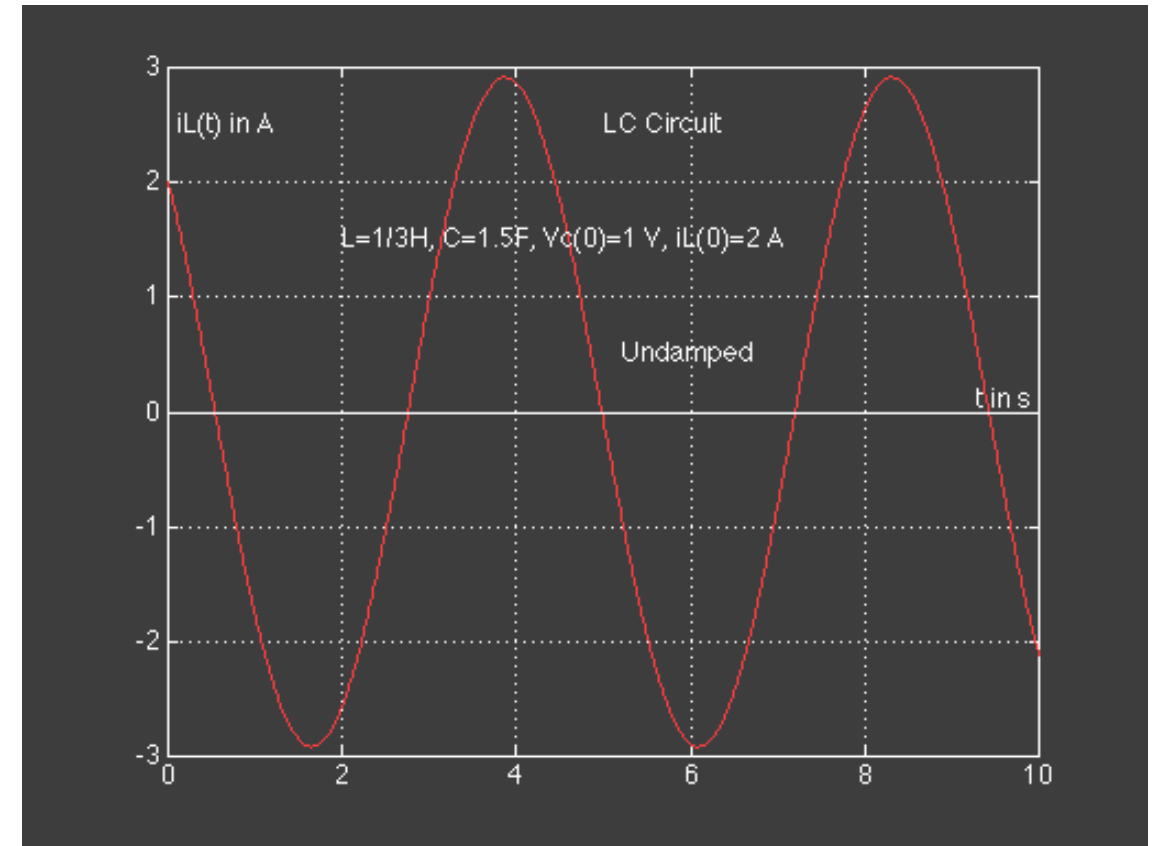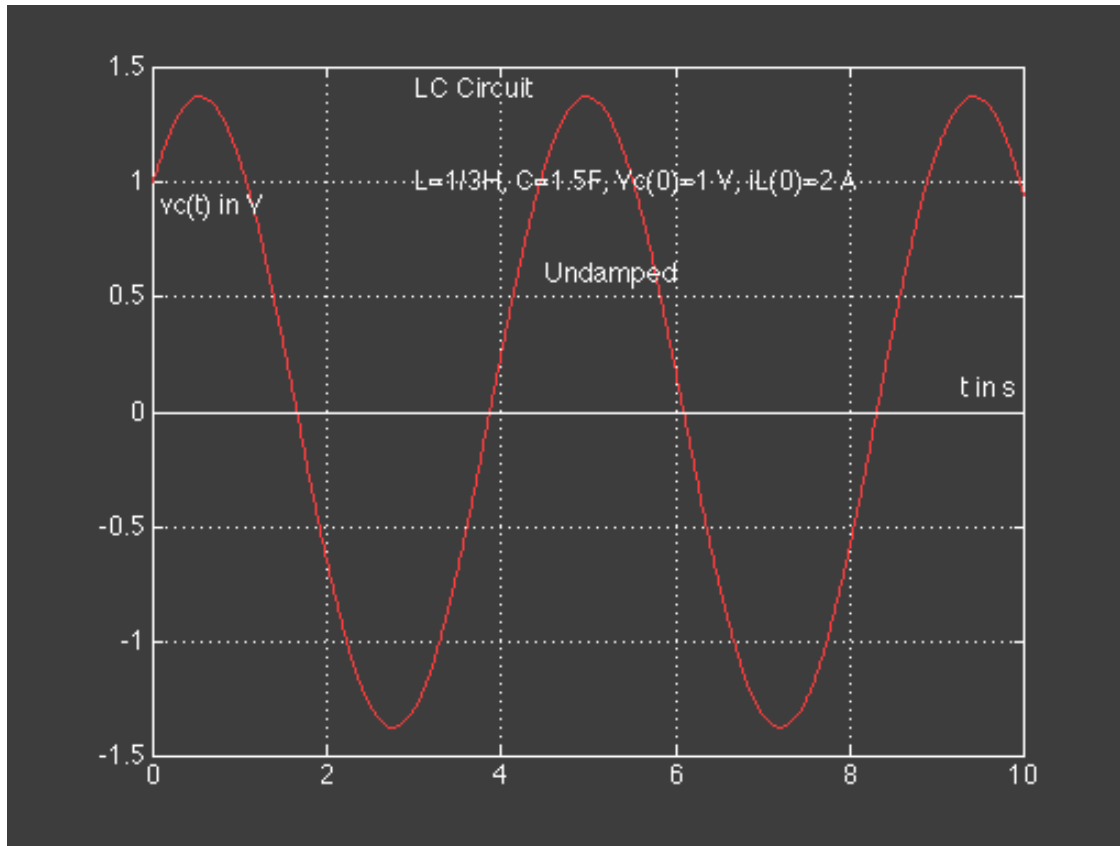
# Case D – Undamped Circuit





$$\delta = 0 \rightarrow s_{1,2} = \pm j\omega_0 \rightarrow v_C(t) = A_1 \cos \omega_0 t + A_2 \sin \omega_0 t = A \cos(\omega_0 t + \varphi)$$



$$v_C(t) = 1.374 \cos(1.414t - 0.756) \text{ V,}$$


$$i_L(t) = 2.915 \cos(1.414t + 0.815) \text{ A}$$

# Summary

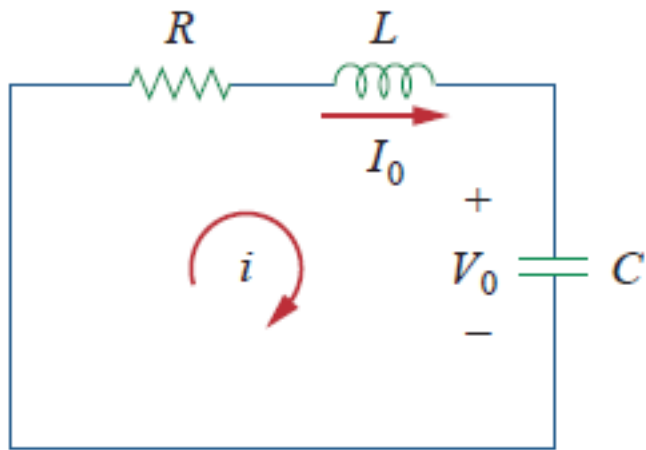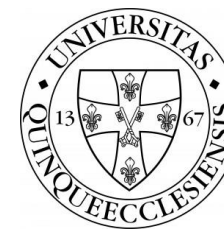

[undamped] vs. [damped]  
natural frequency;  $\omega_0 \geq \omega_d$
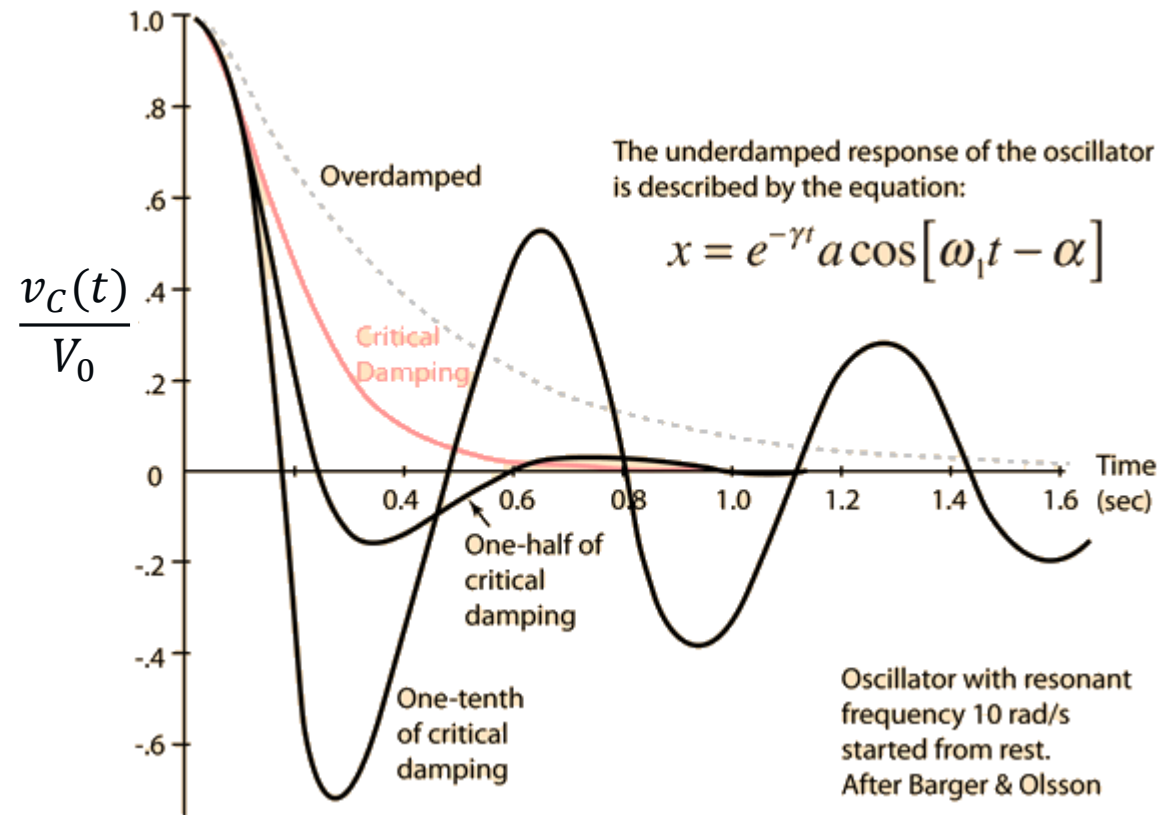
$$\omega_d = \sqrt{\omega_0^2 - \delta^2}$$





- ❑ The Source-Free Series RLC Circuit
- ❑ **Duality in Electric Circuits**
- ❑ The Source-Free Parallel RLC Circuit
- ❑ Step Response of a Series RLC Circuit
- ❑ Step Response of a Parallel RLC Circuit
- ❑ General Second-Order Circuits

# Electrical Duality



**Duality in circuit theory** (A. Russell, 1904).

- ❑ Parallelism bw. pairs of characterizing equations and theorems of circuits
- ❑ Interchanging dual parameters in an expression
- ❑ Dual expression has the same form

## Examples

- ❑ *Duality of electricity and magnetism*

$$\square \quad \sum v_i = 0 \quad \leftrightarrow \quad \sum i_i = 0$$

$$\square \quad \sum R_i = R_{eq} \quad \leftrightarrow \quad \sum G_i = G_{eq}$$

$$\square \quad v_n = v_0 \frac{R_n}{\sum R_i} \quad \leftrightarrow \quad i_n = i_0 \frac{G_n}{\sum G_i}$$

$$\square \quad v_L = L \frac{di_L}{dt} \quad \leftrightarrow \quad i_C = C \frac{dv_C}{dt}$$

Dual Pair 1	Dual Pair 2
Resistance	Conductance
Inductance	Capacitance
Voltage	Current
Voltage source	Current source
Node	Mesh
Series path	Parallel path
Open circuit	Short circuit
KVL	KCL
Thevenin	Norton

# Electrical Duality



**Dual circuits** → same characterizing equations with interchanged dual quantities

*Notice - mutual inductance (for example) has no dual*


## Graphical technique to find the dual circuit

- Place a node at the center of each mesh of the given circuit.
  - Place the reference node (the ground) of the dual circuit outside the given circuit.
- Draw lines between the nodes such that each line crosses an element.
  - Replace that element by its dual.
- To determine the polarity of voltage sources and direction of current sources, follow this rule: A voltage source that produces a positive (clockwise) mesh current has as its dual a current source whose reference direction is from the ground to the nonreference node.

# Electrical Duality



Find the dual circuit.

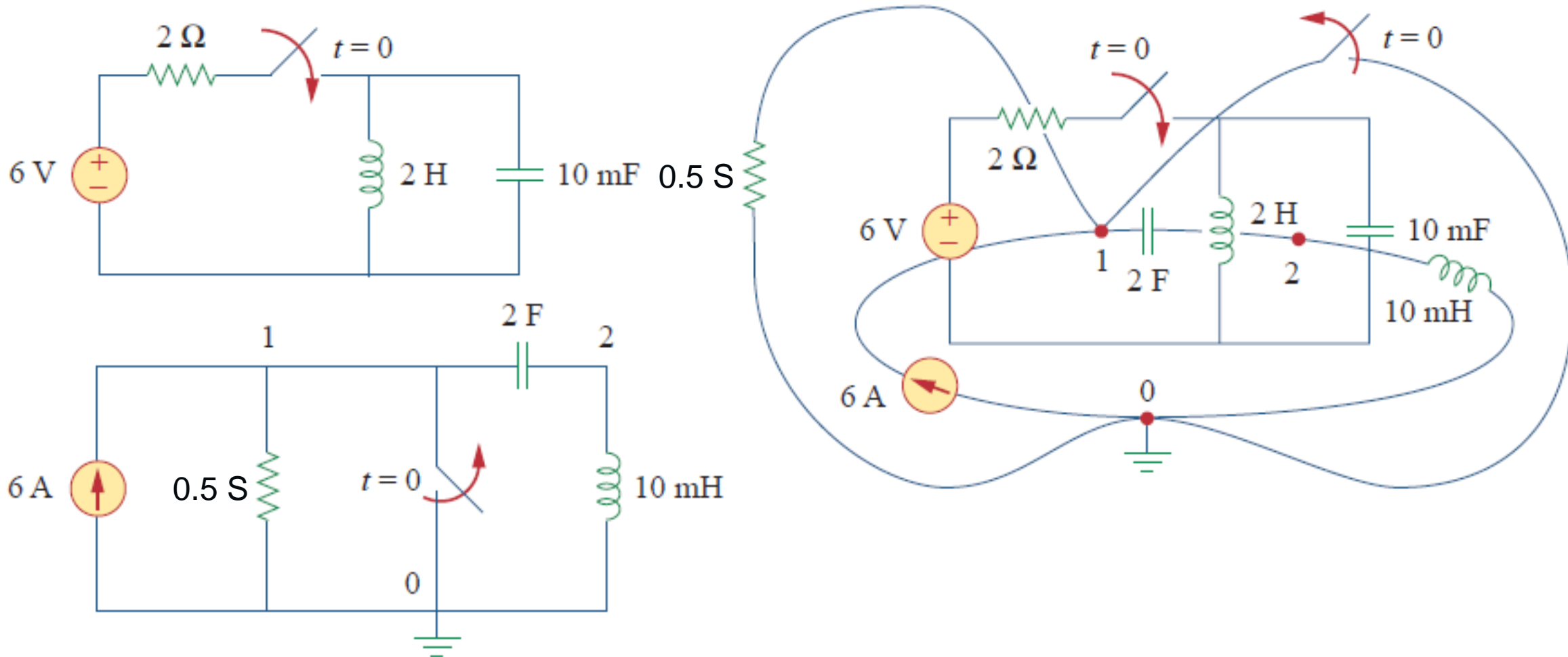






- The Source-Free Series RLC Circuit
- Duality in Electric Circuits
- The Source-Free Parallel RLC Circuit**
- Step Response of a Series RLC Circuit
- Step Response of a Parallel RLC Circuit
- General Second-Order Circuits

# Source-Free Parallel RLC Circuit

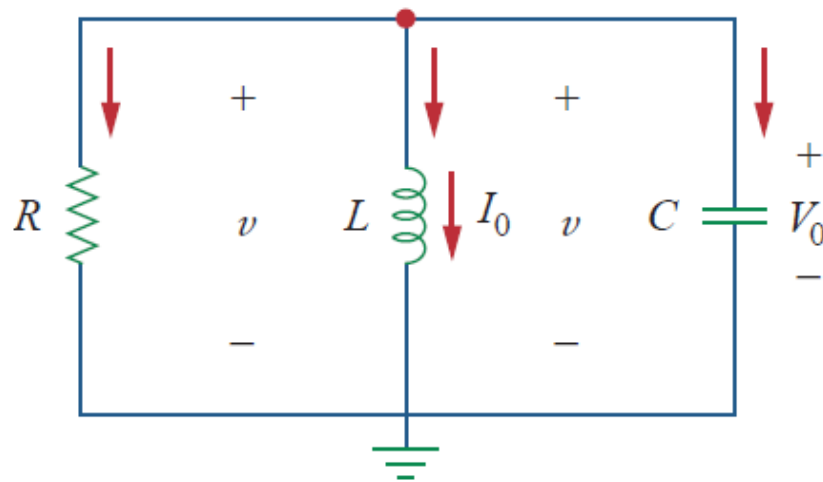

$$v = L \frac{di_L}{dt}, \quad i_C = C \frac{dv}{dt}$$

$$i_L + i_R + i_C = 0 \quad i_L + GL \frac{di_L}{dt} + i_C = 0$$

$$i_C = LC \frac{d^2 i_L}{dt^2} \quad LC \frac{d^2 i_L}{dt^2} + GL \frac{di_L}{dt} + i_L = 0$$

## Initial conditions

To solve second-order equation there must be two initial values.

$$i_L(0) = I_0$$

$$\frac{di_L(0)}{dt} = \frac{1}{L} v(0) = \frac{V_0}{L}$$

## 'Complementary' solution

$$i_L(t) = K e^{st}$$

- $K$  - from initial conditions
- $s$  - from coefficients of diff. equation

# Source-Free Parallel RLC Circuit



$$LC \frac{d^2 i_L}{dt^2} + GL \frac{di_L}{dt} + i_L = 0$$

□ Complementary solution form

$$i_L(t) = K e^{st} \rightarrow K e^{st} (LCs^2 + GLs + 1) = 0$$

□ Characteristic equation

$$LCs^2 + GLs + 1 = 0$$

□ Quadratic characteristic eq.  $\rightarrow$  two roots

$$s_{1,2} = \frac{-GL \pm \sqrt{(GL)^2 - 4LC}}{2LC} = -\frac{G}{2C} \pm \sqrt{\left(\frac{G}{2C}\right)^2 - \frac{1}{LC}}$$


□ Introducing damping factor and natural frequency

$$\delta = \frac{G}{2C}, \quad \omega_0 = \frac{1}{\sqrt{LC}} \rightarrow s_{1,2} = -\delta \pm \sqrt{\delta^2 - \omega_0^2}$$

□ Each root contributes in complementary solution

$$i_L(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

# Source-Free Parallel RLC Circuit

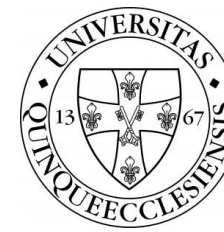

$$s_{1,2} = -\delta \pm \sqrt{\delta^2 - \omega_0^2}$$

CASE A	CASE B	CASE C	CASE D
$\delta^2 - \omega_0^2 > 0$	$\delta^2 - \omega_0^2 = 0$	$\delta^2 - \omega_0^2 < 0$	$\delta = 0$
$s_1 = -\delta + \sqrt{\delta^2 - \omega_0^2}$ $s_2 = -\delta - \sqrt{\delta^2 - \omega_0^2}$	$s_1 = s_2 = -\delta$	$s_1 = -\delta - j\sqrt{\omega_0^2 - \delta^2}$ $s_2 = -\delta + j\sqrt{\omega_0^2 - \delta^2}$	$s_1 = +j\omega_0$ $s_2 = -j\omega_0$
Two real unequal roots Overdamped circuit	Two real equal roots Critically damped circuit	Two cpx. conjugate roots Underdamped circuit	Two imaginary roots Undamped circuit (free-oscillation)

# Source-Free Parallel RLC Circuit



## Case A (overdamped)

$$\delta^2 - \omega_0^2 > 0 \rightarrow s_{1,2} = -\delta \pm \sqrt{\delta^2 - \omega_0^2} \rightarrow i_L(t) = K_1 e^{(-\delta + \sqrt{\delta^2 - \omega_0^2})t} + K_2 e^{(-\delta - \sqrt{\delta^2 - \omega_0^2})t}$$

## Case B (critically damped)


$$\delta^2 - \omega_0^2 = 0 \rightarrow s_1 = s_2 = -\delta \rightarrow i_L(t) = K_1 e^{-\delta t} + K_2 t e^{-\delta t}, \quad t \geq 0$$

## Case C (underdamped)

$$\delta^2 - \omega_0^2 < 0 \rightarrow s_{1,2} = -\delta \pm j\sqrt{\omega_0^2 - \delta^2} = -\delta \pm j\omega_d \rightarrow i_L(t) = e^{-\delta t}(A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

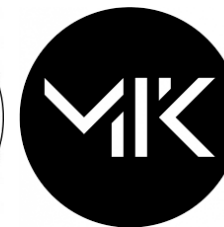
## Case D (undamped)

$$\delta = 0 \rightarrow s_{1,2} = \pm j\omega_0 \rightarrow i_L(t) = A_1 \cos \omega_0 t + A_2 \sin \omega_0 t$$



- The Source-Free Series RLC Circuit
- Duality in Electric Circuits
- The Source-Free Parallel RLC Circuit
- Step Response of a Series RLC Circuit**
- Step Response of a Parallel RLC Circuit
- General Second-Order Circuits

# Step Response of a Series RLC Circuit

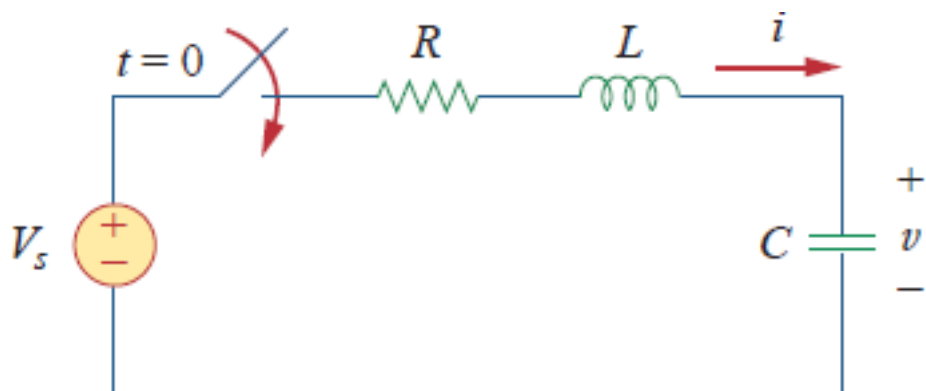

$$L \frac{di}{dt} + Ri + v = V_S, \quad i = C \frac{dv}{dt}$$

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_S}{LC}$$

Complete response = **transient response** ('temporary part, dies out w. time') + **steady-state response** (,permanent part')

$$v(t) = v_{tr}(t) + v_{ss}(t)$$

## Transient part

- Overdamped  $v(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$
- Critically damped  $v(t) = (K_1 + K_2) e^{-\delta t}$
- Underdamped  $v(t) = (K_1 \cos \omega_d t + K_2 \sin \omega_d t) e^{-\delta t}$

**Steady-state part**  $v_{ss}(t) = v(\infty) = V_S$

In general (for any x variable)

$$x(t) = x_{tr}(t) + x_{ss}(t)$$

$$K_1, K_2 \leftarrow x(0), \frac{dx(0)}{dt} \text{ initial conditions}$$


$$s_1, s_2 \dots (\delta, \omega_d) \leftarrow RLC \text{ circuit elements}$$



- The Source-Free Series RLC Circuit
- Duality in Electric Circuits
- The Source-Free Parallel RLC Circuit
- Step Response of a Series RLC Circuit
- Step Response of a Parallel RLC Circuit**
- General Second-Order Circuits



# Step Response of a Series RLC Circuit

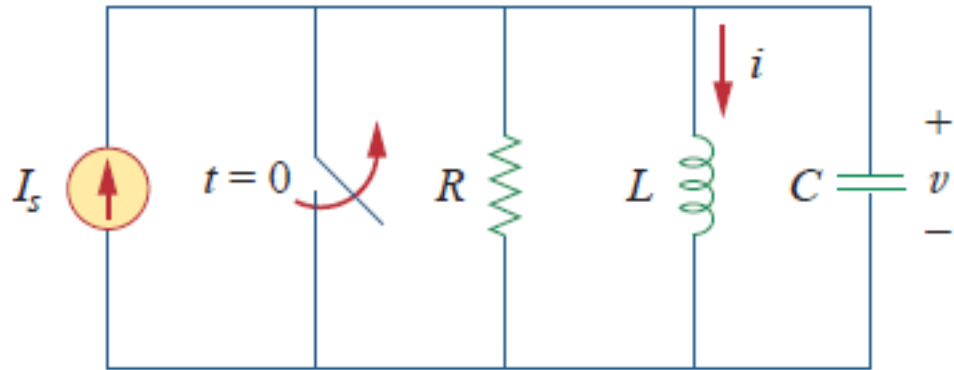

$$C \frac{dv}{dt} + i + \frac{v}{R} = I_s, \quad v = L \frac{di}{dt}$$

$$\frac{d^2i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$

Complete response = **steady-state response** (‘permanent part’) + **transient response** (‘temporary part, dies out w. time’)

$$i(t) = i_{ss}(t) + i_{tr}(t)$$

## Complete response


- Overdamped  $i(t) = I_s + K_1 e^{s_1 t} + K_2 e^{s_2 t}$
- Critically damped  $i(t) = I_s + (K_1 + K_2) e^{-\delta t}$
- Underdamped  $i(t) = I_s + (K_1 \cos \omega_d t + K_2 \sin \omega_d t) e^{-\delta t}$

In general (for any x variable)

$$x(t) = x_{tr}(t) + x_{ss}(t)$$

$$K_1, K_2 \leftarrow x(0), \frac{dx(0)}{dt} \text{ initial conditions}$$
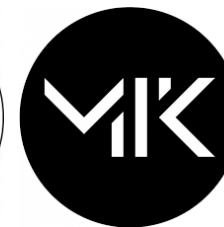
$$s_1, s_2 \dots (\delta, \omega_d) \leftarrow RLC \text{ circuit elements}$$



- The Source-Free Series RLC Circuit
- Duality in Electric Circuits
- The Source-Free Parallel RLC Circuit
- Step Response of a Series RLC Circuit
- Step Response of a Parallel RLC Circuit
- General Second-Order Circuits**

# General Second-Order Circuits




- ❑ Find the initial conditions  $x(0)$ ,  $dx(0)/dt$  and the final value  $x(\infty)$
- ❑ Turn off the independent sources. Find  $x_{tr}(t)$  by KCL/KVL (2nd-order diff. eq.)  
→ characteristic roots (over-, critically, or underdamped) →  $x_{tr}(t)$  w. 2 unknown constants
- ❑ Obtain the steady-state response  $x_{ss}(t) = x(\infty)$
- ❑ Total response  $x(t) = x_{tr}(t) + x_{ss}(t)$
- ❑ Determine the constants in transient response by  $x(0)$ ,  $dx(0)/dt$ .

**Check your skill.**

$v_0(t) = ?$  for  $t > 0$ .  
(Hint: first find  $v_1$  and  $v_2$ .)

Result  $8(e^{-t} - e^{-6t})$  V

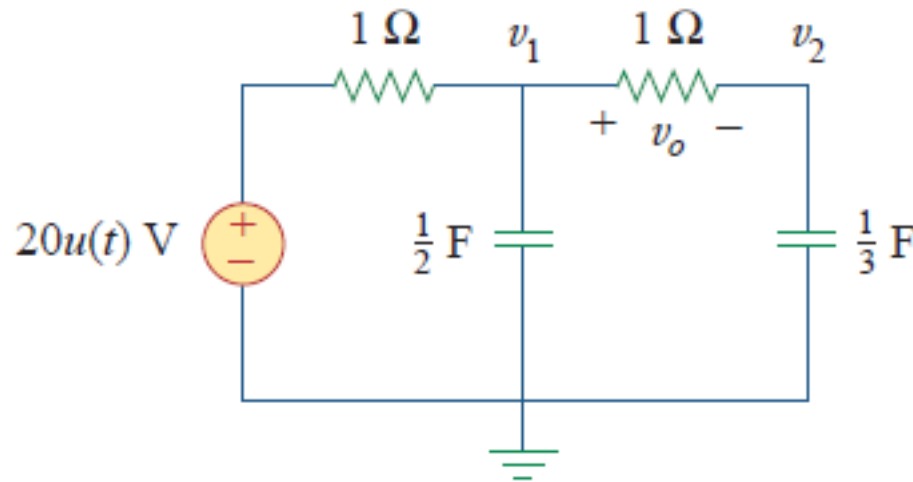

# Questions

