




DR. GYURCSEK ISTVÁN

Exercises with Capacitors and Inductors

Sources and additional materials (recommended)


- ❑ *Dr. Gyurcsek – Dr. Elmer: Theories in Electric Circuits, GlobeEdit, 2016, ISBN:978-3-330-71341-3*
- ❑ *Ch. Alexander, M. Sadiku: Fundamentals of Electric Circuits, 6th Ed., McGraw Hill NY 2016, ISBN: 978-0078028229*
- ❑ *Simonyi K.: Villamosságtan. AK Budapest 1983, ISBN:9630534134*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságtan 1. MK Budapest 2002, TK szám: 49203/I*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságtan 2. TK Budapest 2002, ISBN:9631026043*

Stored Energy in Capacitors

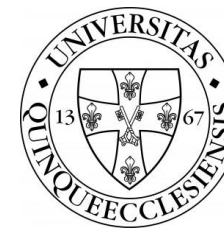


LCE.01 – Calculate energy stored in each capacitor.

Solution

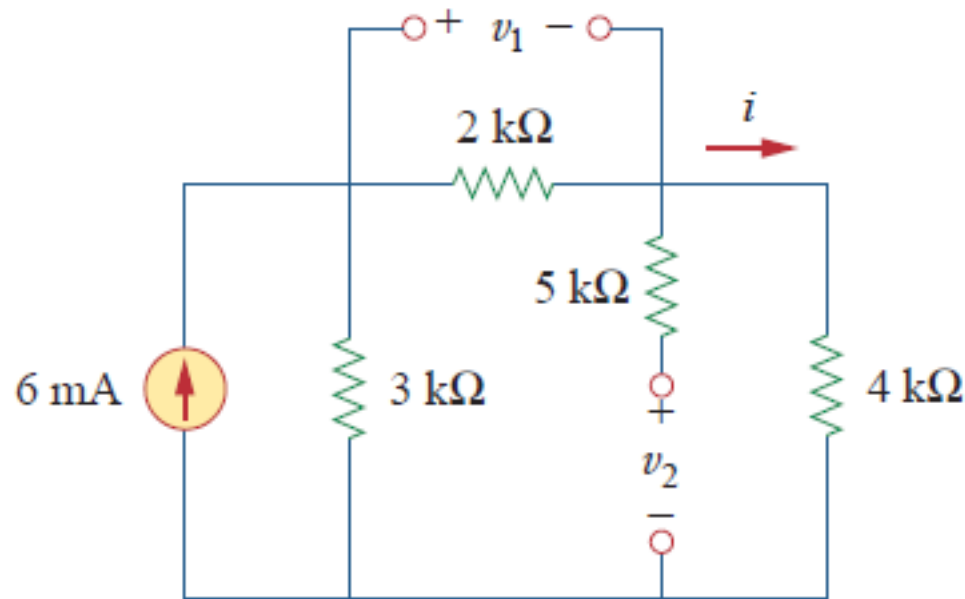
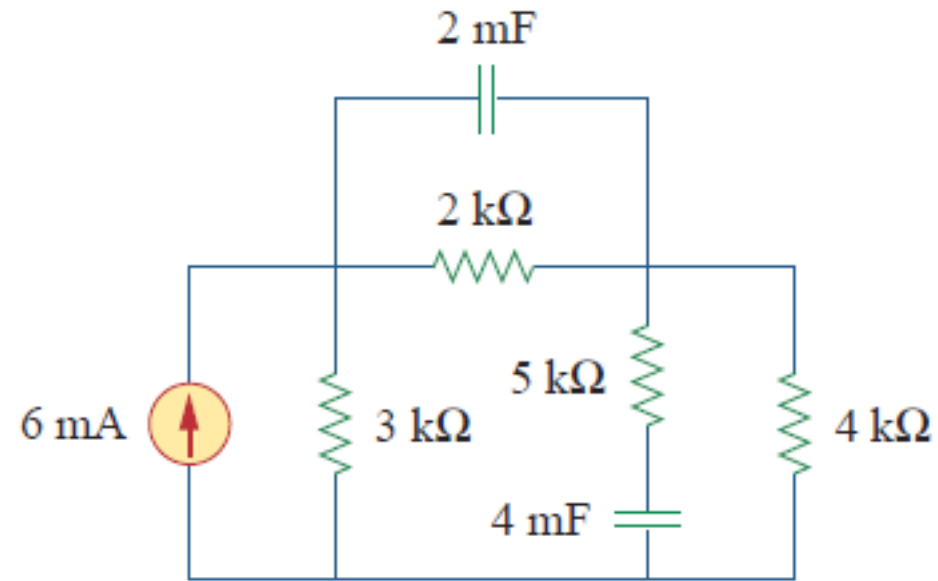
$$i = 6 \frac{3}{3 + 2 + 4} = 2 \text{ mA}$$



$$v_1 = 2000i = 4 \text{ V}, \quad v_2 = 4000i = 8 \text{ V}$$


$$w_1 = \frac{1}{2} C_1 v_1^2 = \frac{1}{2} \cdot 2 \cdot 10^{-3} \cdot 16 = 16 \text{ mJ}$$

$$w_2 = \frac{1}{2} C_2 v_2^2 = \frac{1}{2} \cdot 4 \cdot 10^{-3} \cdot 64 = 128 \text{ mJ}$$

Stored Energy in Capacitors



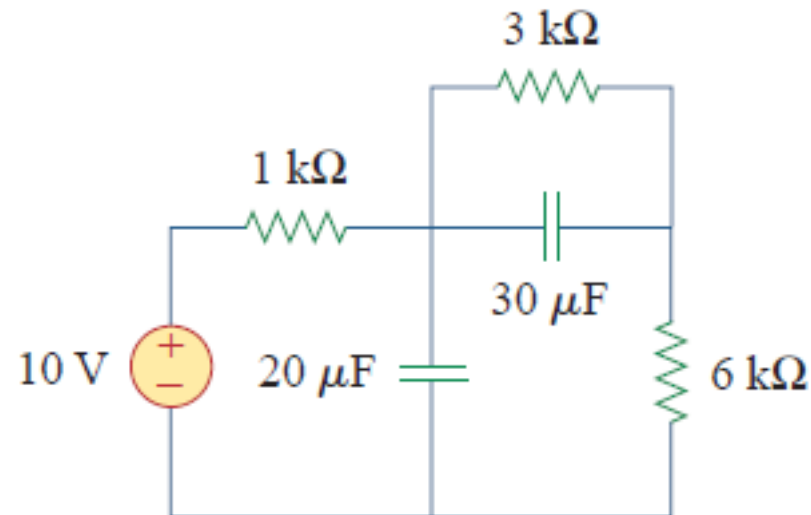LCE.02 – Calculate energy stored in each capacitor.




Solution $w_1 = 810 \mu J$, $w_2 = 135 \mu J$

Equivalent Capacitance



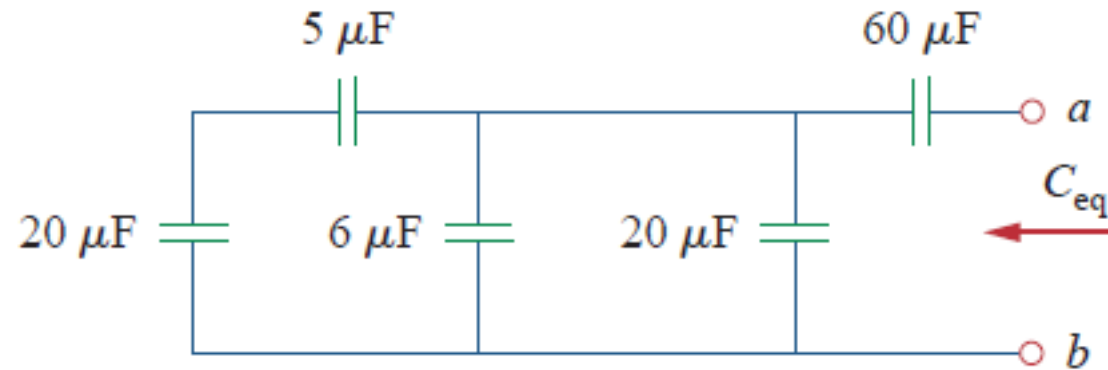
LCE.03 – Find the equivalent capacitance between a - b




Solution

$$\frac{20 \cdot 5}{20 + 5} = 4 \mu F \rightarrow 4 + 6 + 20 = 30 \mu F \rightarrow \frac{30 \cdot 60}{30 + 60} = 20 \mu F$$

Equivalent Capacitance

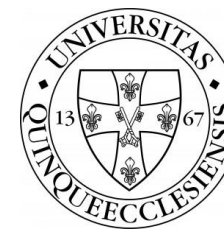

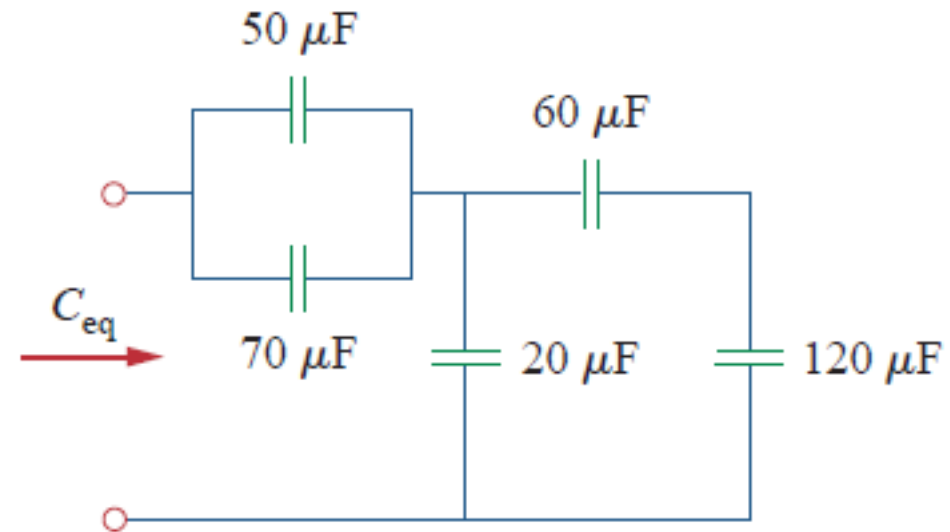LCE.04 – Find the equivalent capacitance.




Solution $40 \mu\text{F}$

Equivalent Capacitance



LCE.05 – Find the voltage across each capacitor.

Solution

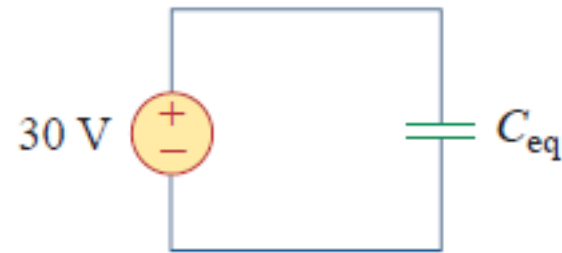


$$C_{eq} = \frac{1}{\frac{1}{60} + \frac{1}{30} + \frac{1}{20}} = 10 \text{ mF}$$

$$q = C_{eq}v = 10\text{m} \cdot 30 = 300 \text{ mC}$$

$$v_1 = \frac{q}{C_1} = \frac{300\text{m}}{20\text{m}} = 15 \text{ V} \quad v_2 = \frac{q}{C_2} = \frac{300\text{m}}{30\text{m}} = 10 \text{ V}$$

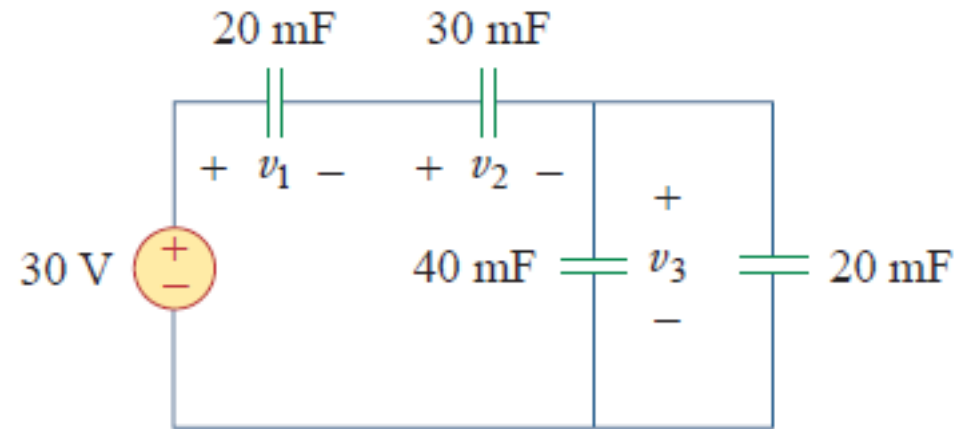
$$v_3 = \frac{q}{C_{34}} = \frac{300\text{m}}{(40 + 20)\text{m}} = 5 \text{ V} \text{ or } \dots v_3 = 30 - v_1 - v_2 = 5 \text{ V}$$



Equivalent Capacitance



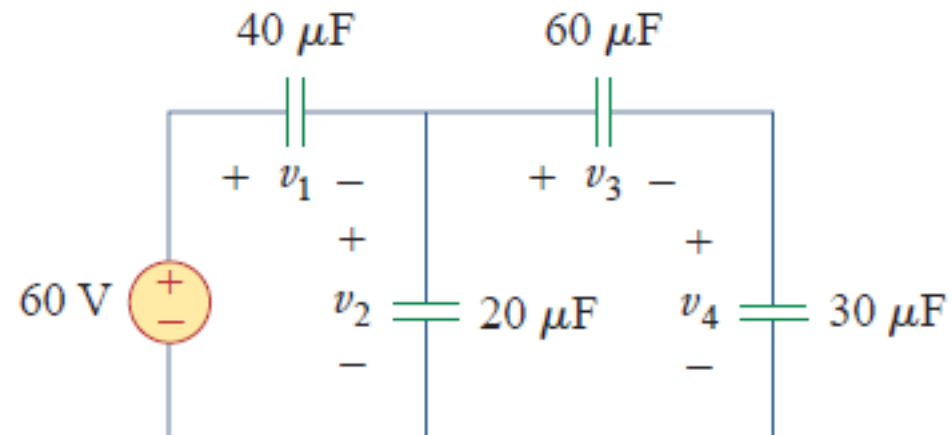LCE.06 – Find the voltage across each capacitor.



Solution $v_1 = 30 \text{ V}$, $v_2 = 30 \text{ V}$, $v_3 = 10 \text{ V}$, $v_4 = 20 \text{ V}$

Inductor Circuits



LCE.07 – $v_C = ?$, $i_L = ?$, $w_C = ?$ $w_L = ?$



Solution

$$i = i_L = \frac{12}{1 + 5} = 2 \text{ A}$$

$$v_C = 5i = 10 \text{ V}$$

$$w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} \cdot 1 \cdot 100 = 50 \text{ J}$$

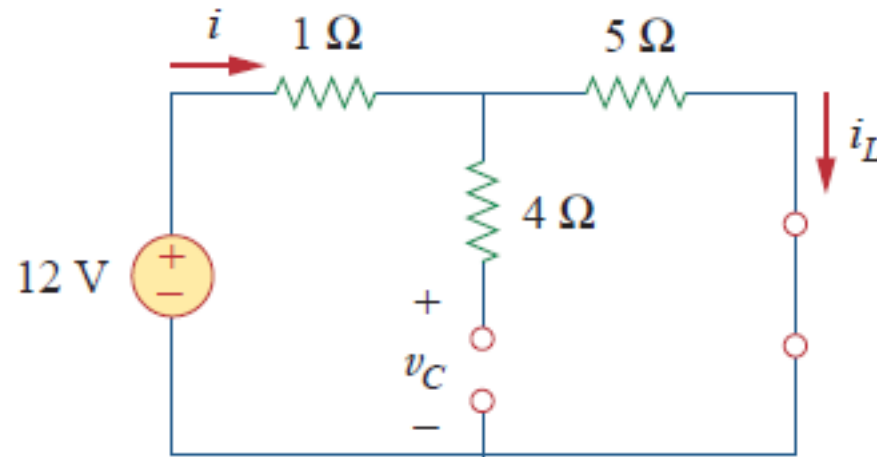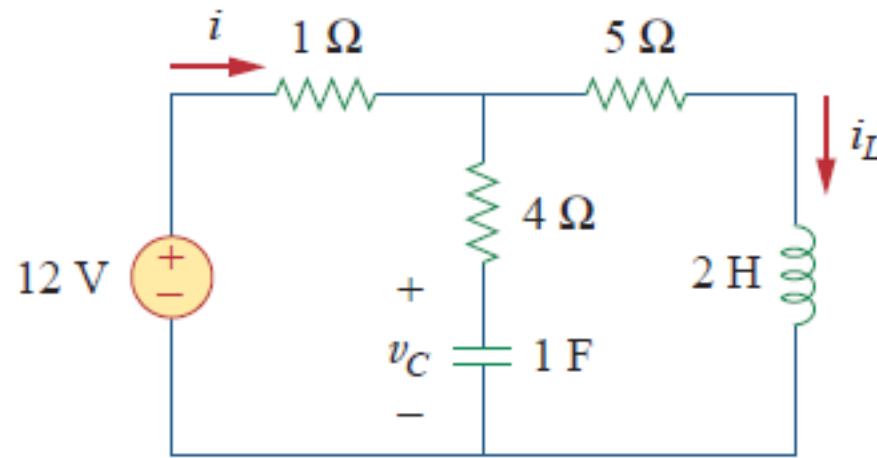
$$w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \cdot 2 \cdot 4 = 4 \text{ J}$$



Inductor Circuits



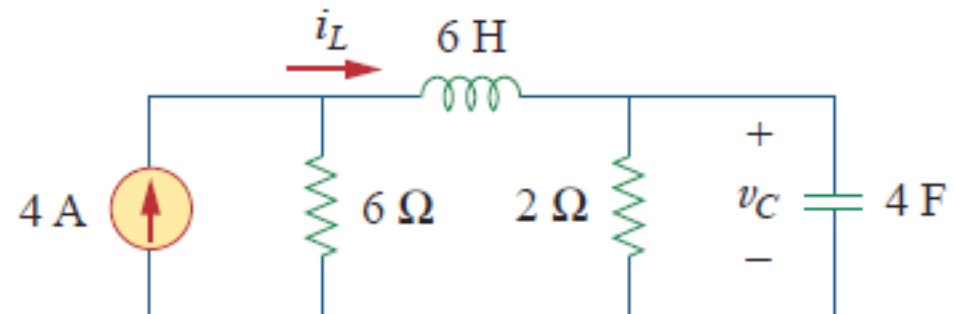LCE.08 – $v_C = ?$, $i_L = ?$, $w_C = ?$ $w_L = ?$




Solution $v_C = 6 V$, $i_L = 3 A$, $w_C = 72 J$, $w_L = 27 J$

Equivalent Inductance




LCE.09 – Find the equivalent inductance.

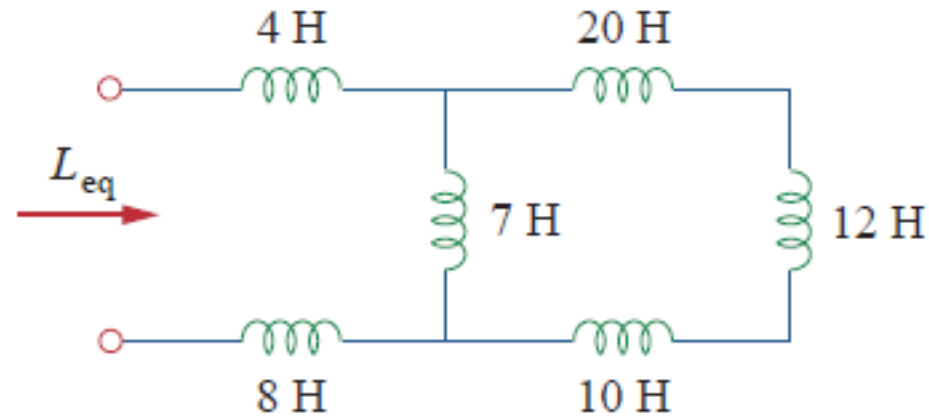


Solution $L_{eq} = 4 + \frac{7 \times 42}{7 + 42} + 8 = 4 + 6 + 8 = 18 H$

Equivalent Inductance

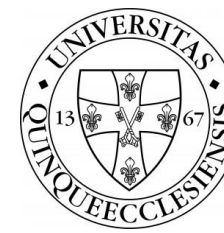

LCE.10 – Find the equivalent inductance.

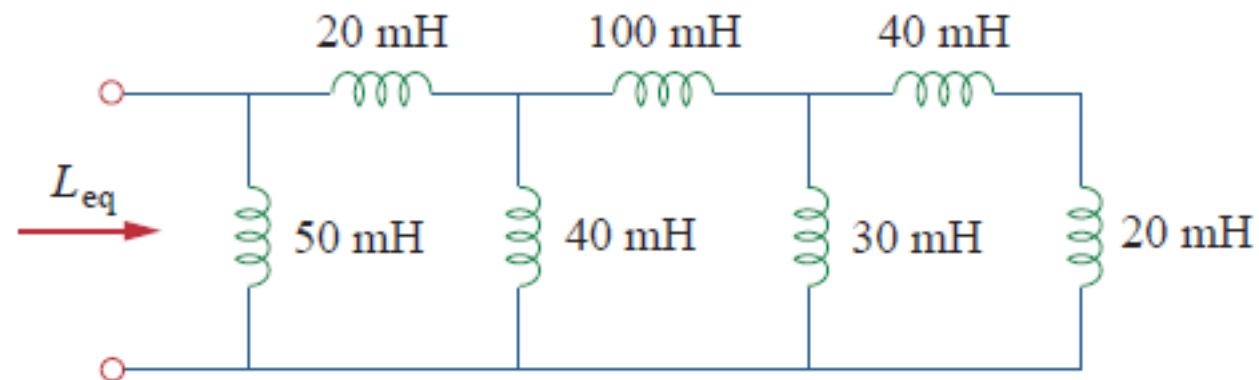

Solution 25 mH

Equivalent Inductance




LCE.11 – $i(t) = 4(2 - e^{-10t}) \text{ mA}$, $i_2(0) = -1 \text{ mA}$

a) $i_1(0) = ?$

b) $v(t) = ?$, $v_1(t) = ?$, $v_2(t) = ?$

c) $i_1(t) = ?$, $i_2(t) = ?$

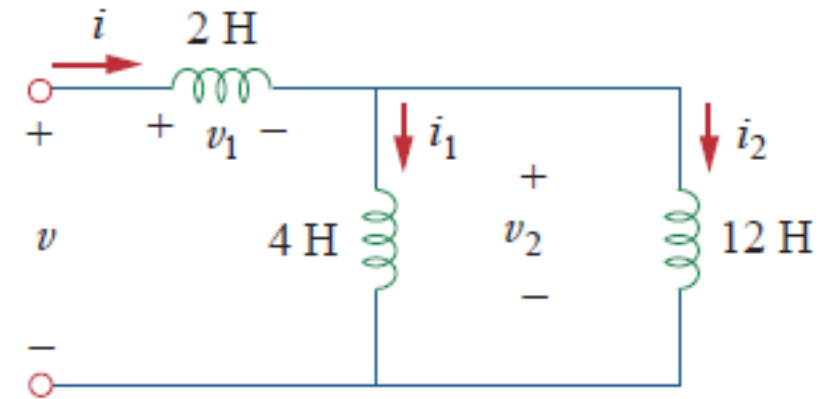

Solution

$$a) i(0) = 4(2 - e^0) = 4 \text{ mA} \rightarrow i_1(0) = i(0) - i_2(0) = 4 - (-1) = 5 \text{ mA}$$

$$b) L_{eq} = 2 + 4 \times 12 = 2 + 3 = 5 \text{ H} \quad v(t) = L_{eq} \frac{di}{dt} = 5 \cdot 4 \cdot (-1)(-10)e^{-10t} = 200 e^{-10t} \text{ mV}$$

$$v_1(t) = 2 \frac{di}{dt} = 2 \cdot (-4)(-10)e^{-10t} = 80 e^{-10t} \text{ mV}$$

$$v(t) = v_1(t) + v_2(t) \rightarrow v_2(t) = v(t) - v_1(t) = 120 e^{-10t} \text{ mV}$$

Equivalent Inductance




$$c) i_1(t) = ?, \quad i_2(t) = ?$$

$$i_1(t) = \frac{1}{4} \int_0^t v_2 dt + i_1(0) = \frac{120}{4} \int_0^t e^{-10t} dt + 5 \text{ mA}$$

$$= -3e^{-10t} \Big|_0^t + 5 \text{ mA} = -3e^{-10t} + 3 + 5 = 8 - 3e^{-10t} \text{ mA}$$

$$i_2(t) = \frac{1}{12} \int_0^t v_2 dt + i_2(0) = \frac{120}{12} \int_0^t e^{-10t} dt - 1 \text{ mA}$$

$$= -e^{-10t} \Big|_0^t - 1 \text{ mA} = -e^{-10t} + 1 - 1 = -e^{-10t} \text{ mA}$$

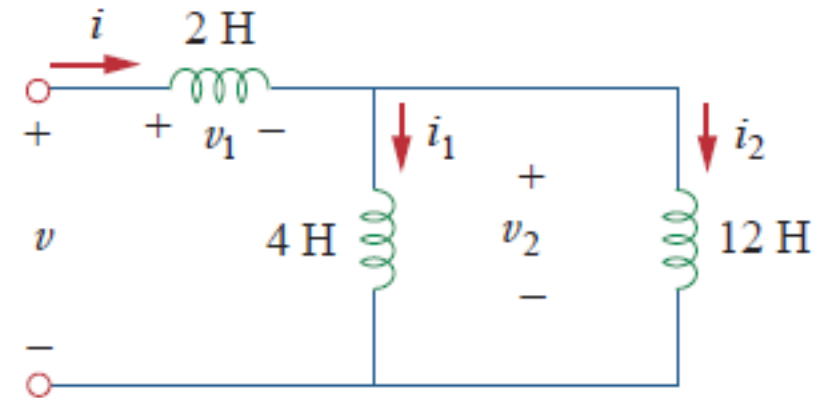


Check $\rightarrow i(t) = i_1(t) + i_2(t)$

Equivalent Inductance



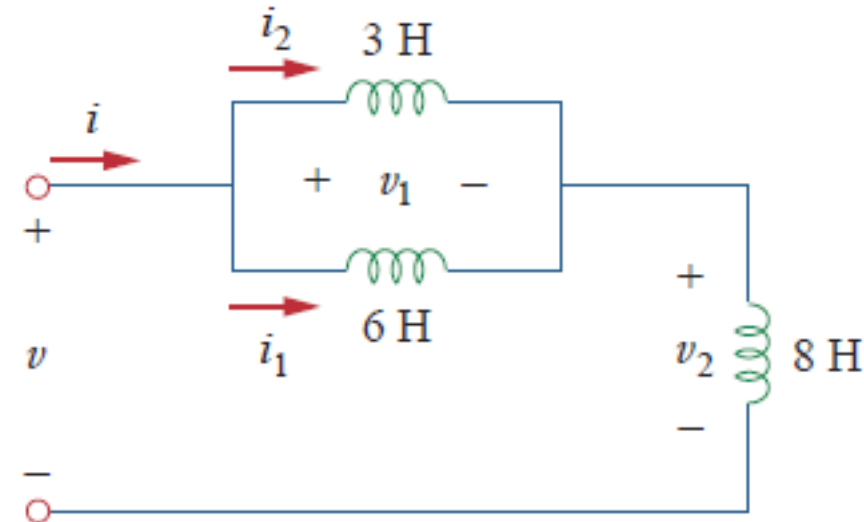LCE.12 – $i_1(t) = 0.6e^{-2t} \text{ A}$, $i(0) = 1.4 \text{ A}$
a) $i_2(0) = ?$
b) $i_2(t) = ?$, $i(t) = ?$
c) $v_1(t) = ?$, $v_2(t) = ?$, $v(t) = ?$



Solution a) $i_2(0) = 0.8 \text{ A}$
b) $i_2(t) = (-0.4 + 1.2e^{-2t}) \text{ A}$, $i(t) = (-0.4 + 1.8e^{-2t}) \text{ A}$
c) $v_1(t) = -36e^{-2t} \text{ V}$, $v_2(t) = -7.2e^{-2t} \text{ V}$, $v(t) = -28.8e^{-2t} \text{ V}$


Integrator Example



LCE.13

$$v_1 = 10 \cos 2t \text{ mV}, v_2 = 0.5t \text{ mV}, v_C(0) = 0 \text{ V}$$

$$v_o = ?$$

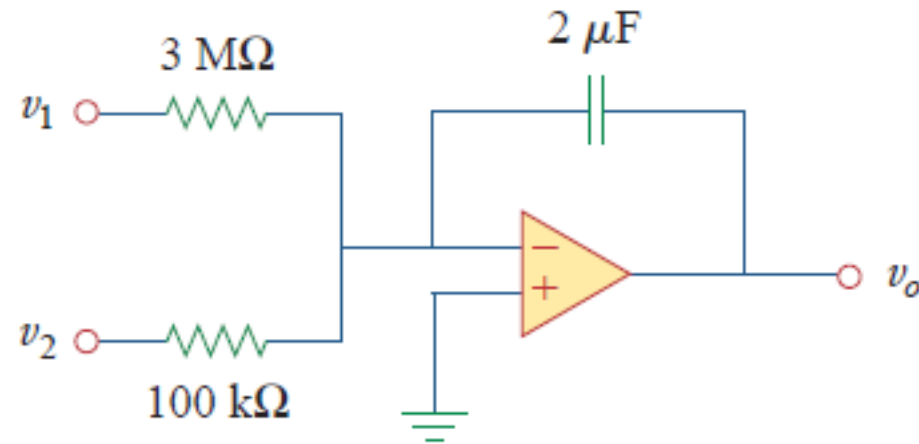

Solution (*summing intergaror*)

$$\begin{aligned} v_o &= -\frac{1}{R_1 C} \int v_1 dt - \frac{1}{R_2 C} \int v_2 dt = -\frac{1}{3 \cdot 10^6 \cdot 2 \cdot 10^{-6}} \int_0^t 10 \cos 2t dt - \frac{1}{100 \cdot 10^3 \cdot 2 \cdot 10^{-6}} \int_0^t 0.5t dt \\ &= -\frac{1}{6} \frac{10}{2} \sin 2t - \frac{1}{0.2} \frac{0.5t^2}{2} = -0.833 \sin 2t - 1.25t^2 \text{ mV} \end{aligned}$$



Differentiator Example



LCE.14

$$v_o(0) = 0 \text{ V}$$

$$v_o(t) = ?$$

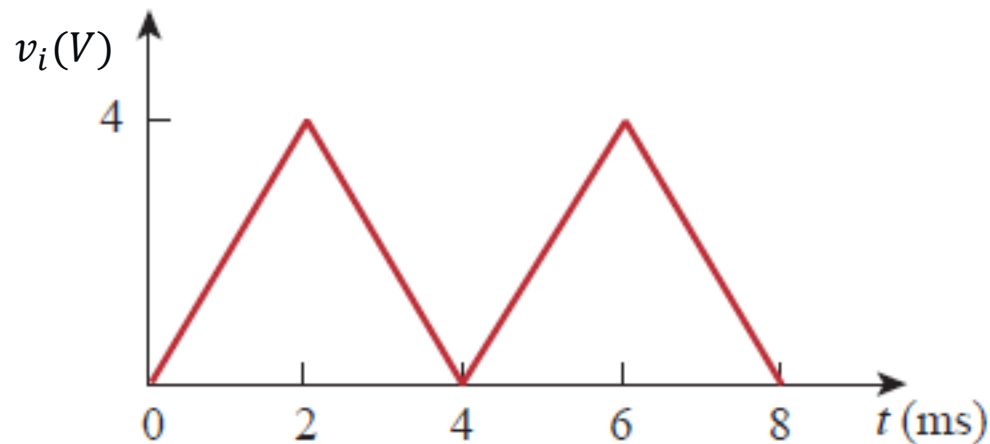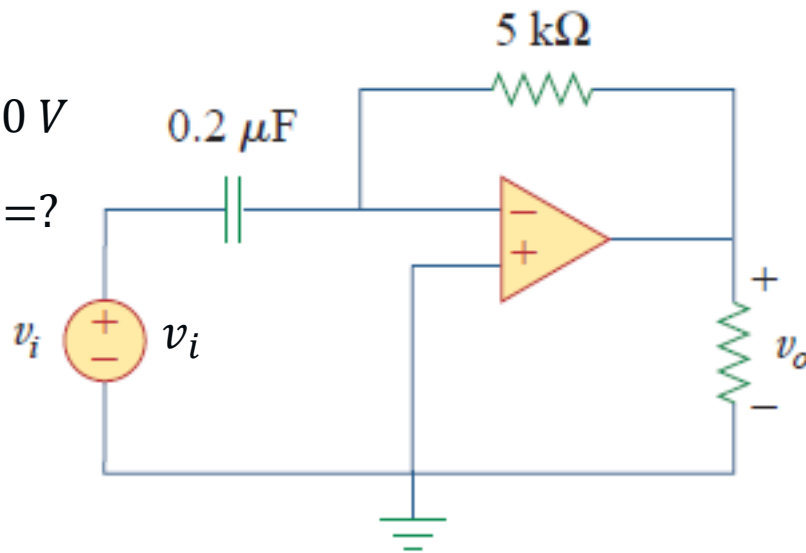


Solution (differentiator circuit)

$$RC = 5 \cdot 10^{-3} \cdot 2 \cdot 10^{-6} = 1 \text{ ms}$$

$$v_i = \begin{cases} 2000t & 0 < t < 2 \text{ ms} \\ 8 - 2000t & 2 < t < 4 \text{ ms} \end{cases}$$
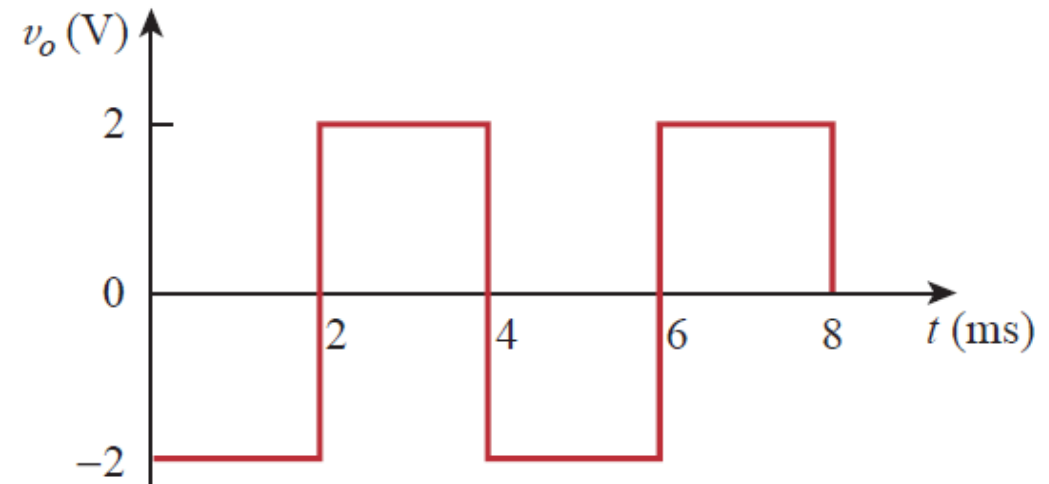
$$v_o = -RC \frac{dv_i}{dt} = \begin{cases} -2 \text{ V} & 0 < t < 2 \text{ ms} \\ +2 \text{ V} & 2 < t < 4 \text{ ms} \end{cases}$$




Differentiator Example



LCE.15

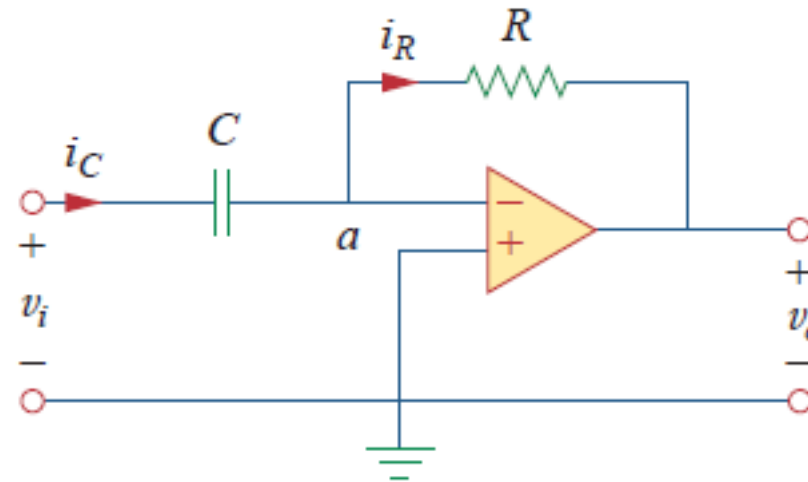$R = 100 \text{ k}\Omega, C = 100 \text{ nF}, v_i(t) = 3t \text{ V}, v_o(t) = ?$



Solution (-30 mV)

Questions

