



DR. GYURCSEK ISTVÁN

# Capacitors and Inductors - Examples


## *Sources and additional materials (recommended)*

- ❑ *Dr. Gyurcsek – Dr. Elmer: Theories in Electric Circuits, GlobeEdit, 2016, ISBN:978-3-330-71341-3*
- ❑ *Ch. Alexander, M. Sadiku: Fundamentals of Electric Circuits, 6th Ed., McGraw Hill NY 2016, ISBN: 978-0078028229*
- ❑ *Simonyi K.: Villamosságtan. AK Budapest 1983, ISBN:9630534134*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságtan 1. MK Budapest 2002, TK szám: 49203/I*
- ❑ *Dr. Selmeczi K. – Schnöller A.: Villamosságtan 2. TK Budapest 2002, ISBN:9631026043*


## Stored Energy in Capacitors

LCE.01 – Calculate energy stored in each capacitor.

Solution

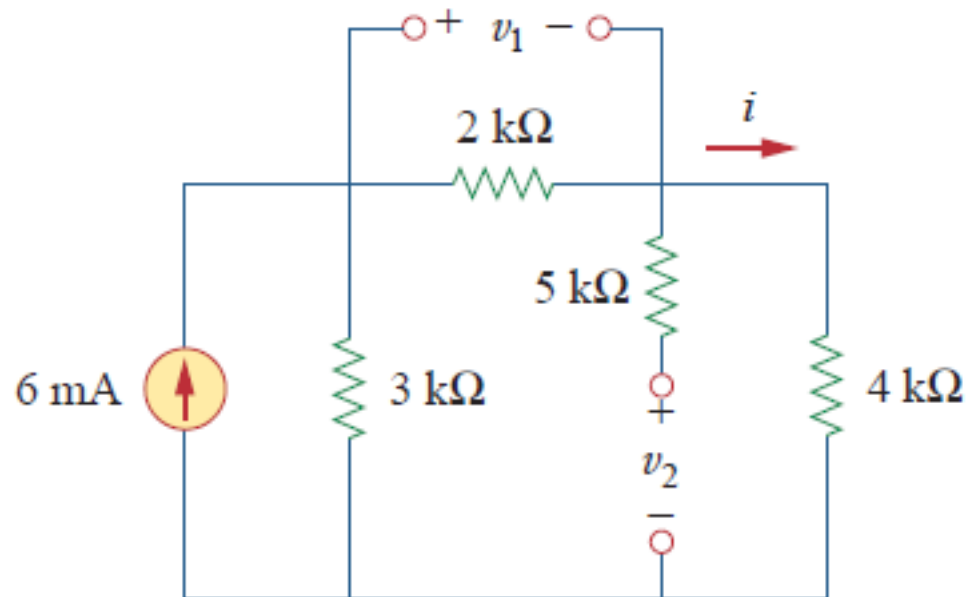
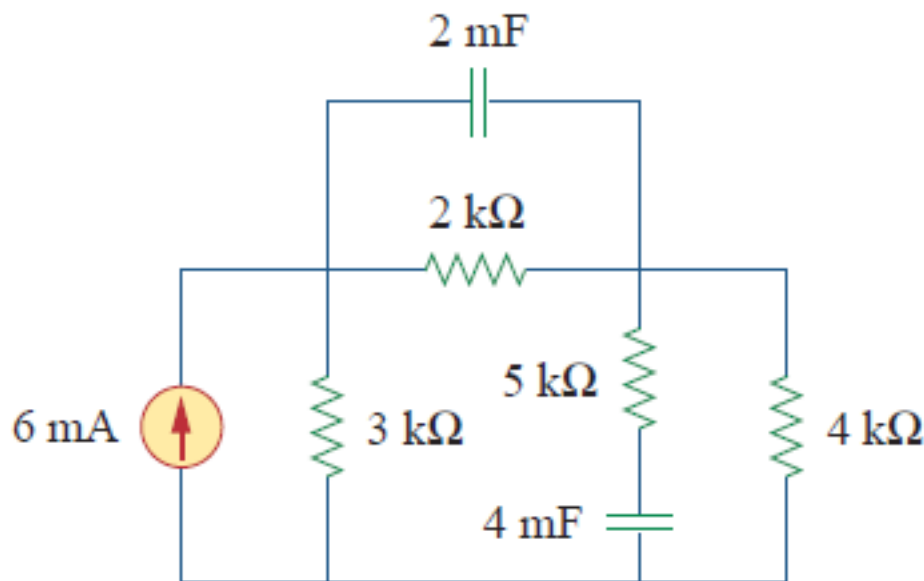
$$i = 6 \frac{3}{3 + 2 + 4} = 2 \text{ mA}$$




$$v_1 = 2000i = 4 \text{ V}, \quad v_2 = 4000i = 8 \text{ V}$$

$$w_1 = \frac{1}{2} C_1 v_1^2 = \frac{1}{2} \cdot 2 \cdot 10^{-3} \cdot 16 = 16 \text{ mJ}$$


$$w_2 = \frac{1}{2} C_2 v_2^2 = \frac{1}{2} \cdot 4 \cdot 10^{-3} \cdot 64 = 128 \text{ mJ}$$

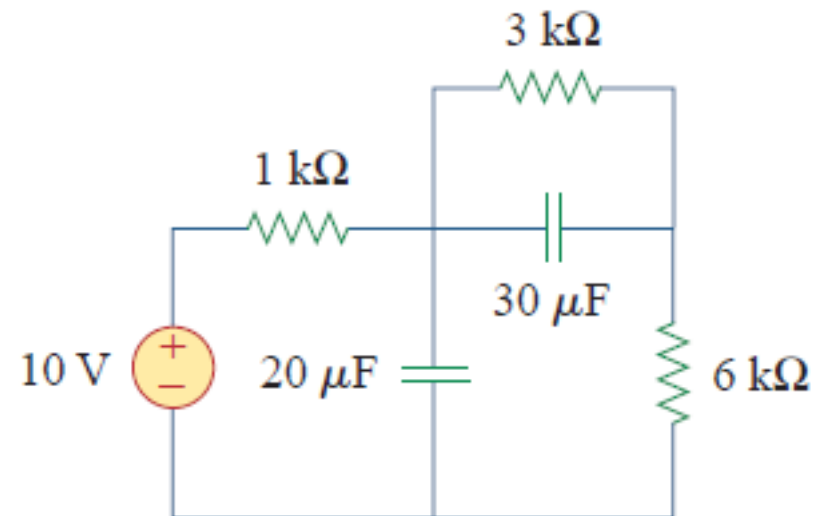LCE.02 – Calculate energy stored in each capacitor.



**Solution**  $w_1 = 810 \mu J$  ,  $w_2 = 135 \mu J$

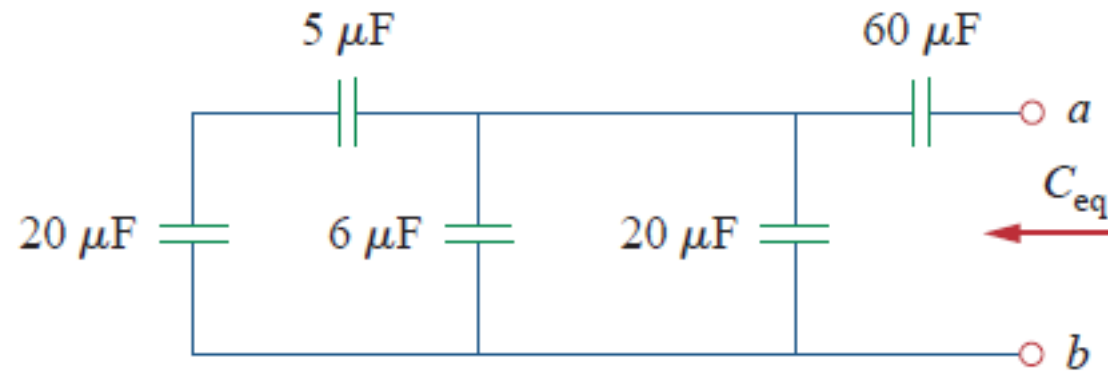**LCE.03** – Find the equivalent capacitance between  $a$ - $b$




**Solution**

$$\frac{20 \cdot 5}{20 + 5} = 4 \mu F \rightarrow 4 + 6 + 20 = 30 \mu F \rightarrow \frac{30 \cdot 60}{30 + 60} = 20 \mu F$$
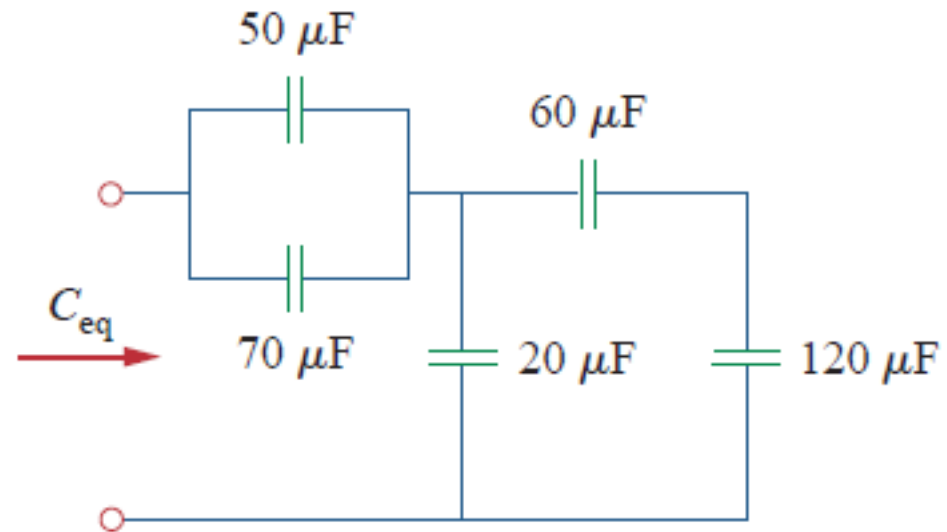
# Equivalent Capacitance



LCE.04 – Find the equivalent capacitance.




**Solution**  $40 \mu\text{F}$

## Equivalent Capacitance

LCE.05 – Find the voltage across each capacitor.

Solution

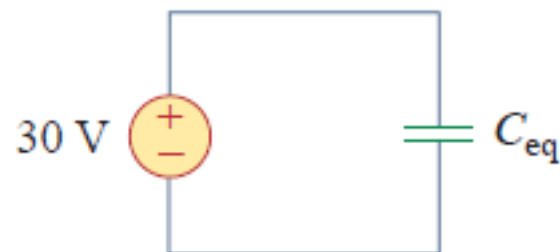


$$C_{eq} = \frac{1}{\frac{1}{60} + \frac{1}{30} + \frac{1}{20}} = 10 \text{ mF}$$

$$q = C_{eq}v = 10\text{m} \cdot 30 = 300 \text{ mC}$$

$$v_1 = \frac{q}{C_1} = \frac{300\text{m}}{20\text{m}} = 15 \text{ V} \quad v_2 = \frac{q}{C_2} = \frac{300\text{m}}{30\text{m}} = 10 \text{ V}$$

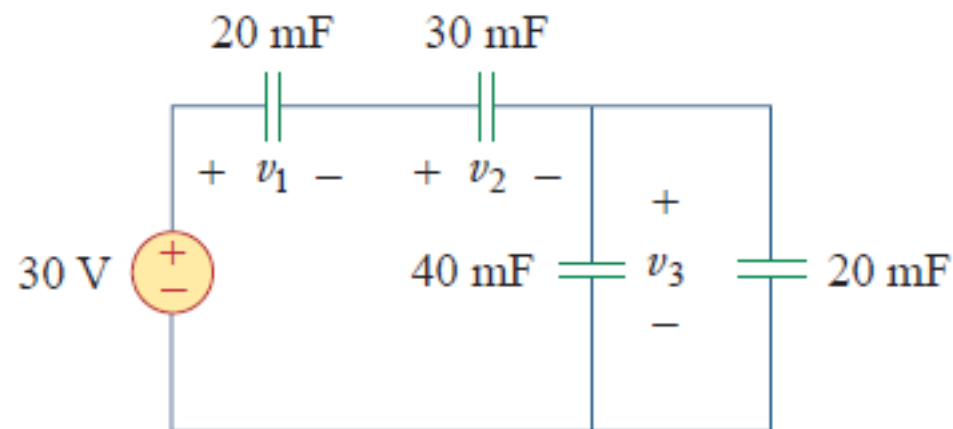
$$v_3 = \frac{q}{C_{34}} = \frac{300\text{m}}{(40 + 20)\text{m}} = 5 \text{ V} \text{ or } \dots v_3 = 30 - v_1 - v_2 = 5 \text{ V}$$


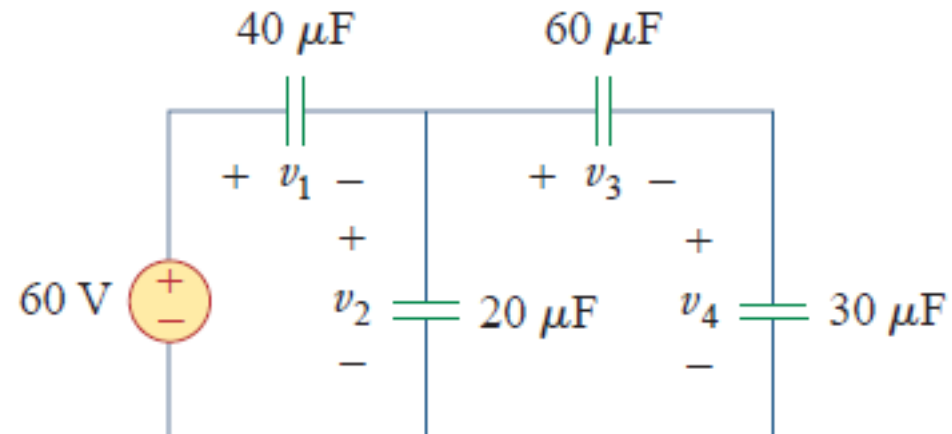
# Equivalent Capacitance



LCE.06 – Find the voltage across each capacitor.



**Solution**  $v_1 = 30 V$ ,  $v_2 = 30 V$ ,  $v_3 = 10 V$ ,  $v_4 = 20 V$

## Inductor Circuit Examples

LCE.07 –  $v_C = ?$ ,  $i_L = ?$ ,  $w_C = ?$   $w_L = ?$



Solution

$$i = i_L = \frac{12}{1 + 5} = 2 \text{ A}$$

$$v_C = 5i = 10 \text{ V}$$

$$w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} \cdot 1 \cdot 100 = 50 \text{ J}$$

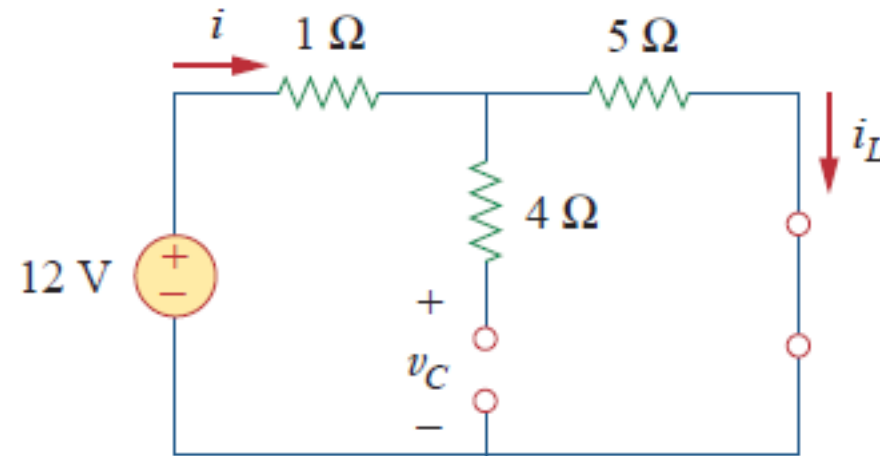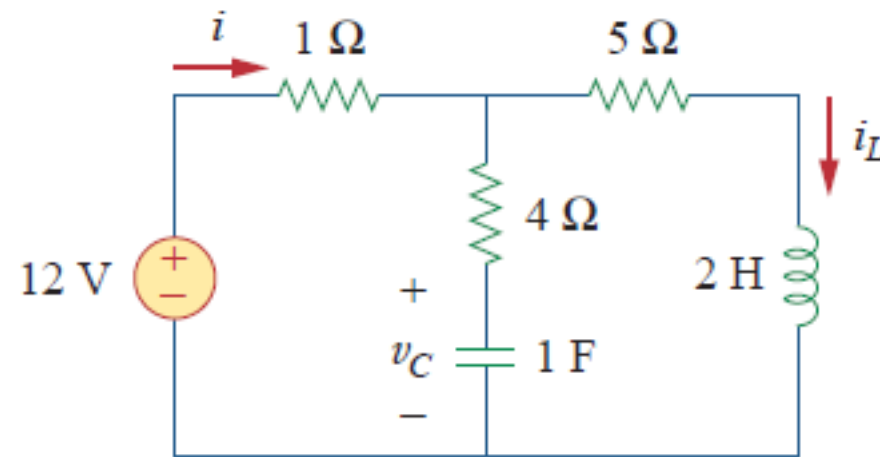
$$w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \cdot 2 \cdot 4 = 4 \text{ J}$$





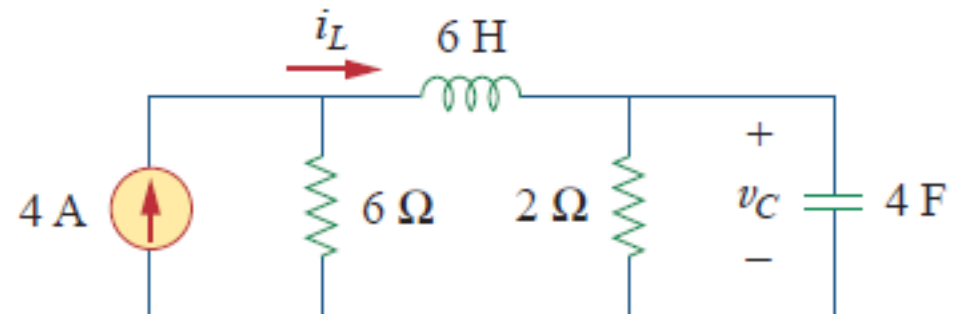
## Inductor Circuit Examples

LCE.08 –  $v_C = ?$ ,  $i_L = ?$ ,  $w_C = ?$   $w_L = ?$



**Solution**  $v_C = 6 V$ ,  $i_L = 3 A$ ,  $w_C = 72 J$ ,  $w_L = 27 J$

LCE.09 – Find the equivalent inductance.

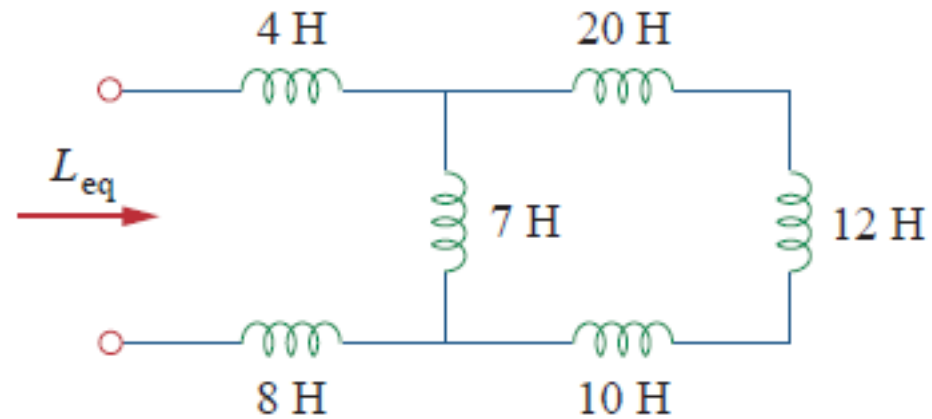


**Solution** 
$$L_{eq} = 4 + \frac{7 \times 42}{7 + 42} + 8 = 4 + 6 + 8 = 18 H$$

# Equivalent Inductance



LCE.10 – Find the equivalent inductance.

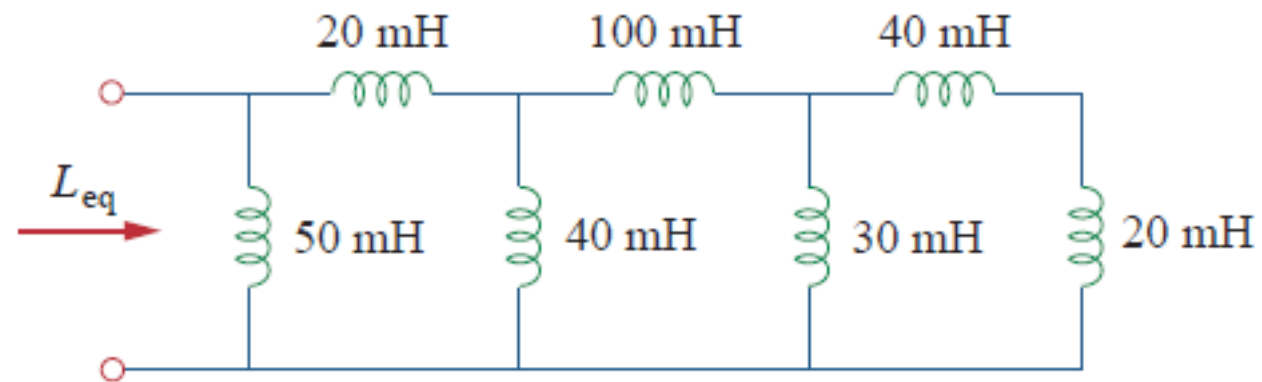

**Solution 25 mH**


## Equivalent Inductance

LCE.11 –  $i(t) = 4(2 - e^{-10t}) \text{ mA}$ ,  $i_2(0) = -1 \text{ mA}$

a)  $i_1(0) = ?$

b)  $v(t) = ?$ ,  $v_1(t) = ?$ ,  $v_2(t) = ?$

c)  $i_1(t) = ?$ ,  $i_2(t) = ?$

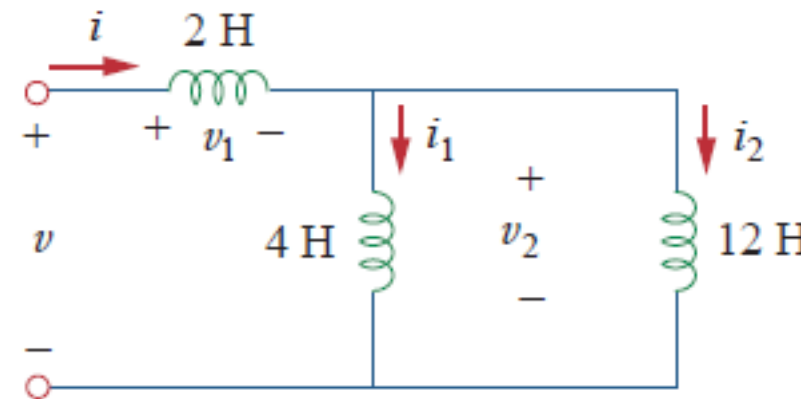

### Solution

$$a) i(0) = 4(2 - e^0) = 4 \text{ mA} \rightarrow i_1(0) = i(0) - i_2(0) = 4 - (-1) = 5 \text{ mA}$$

$$b) L_{eq} = 2 + 4 \times 12 = 2 + 3 = 5 \text{ H} \quad v(t) = L_{eq} \frac{di}{dt} = 5 \cdot 4 \cdot (-1)(-10)e^{-10t} = 200 e^{-10t} \text{ mV}$$

$$v_1(t) = 2 \frac{di}{dt} = 2 \cdot (-4)(-10)e^{-10t} = 80 e^{-10t} \text{ mV}$$

$$v(t) = v_1(t) + v_2(t) \rightarrow v_2(t) = v(t) - v_1(t) = 120 e^{-10t} \text{ mV}$$

## Equivalent Inductance


$$c) i_1(t) = ?, \quad i_2(t) = ?$$

$$i_1(t) = \frac{1}{4} \int_0^t v_2 dt + i_1(0) = \frac{120}{4} \int_0^t e^{-10t} dt + 5 \text{ mA}$$

$$= -3e^{-10t} \Big|_0^t + 5 \text{ mA} = -3e^{-10t} + 3 + 5 = 8 - 3e^{-10t} \text{ mA}$$

$$i_2(t) = \frac{1}{12} \int_0^t v_2 dt + i_2(0) = \frac{120}{12} \int_0^t e^{-10t} dt - 1 \text{ mA}$$


$$= -e^{-10t} \Big|_0^t - 1 \text{ mA} = -e^{-10t} + 1 - 1 = -e^{-10t} \text{ mA}$$

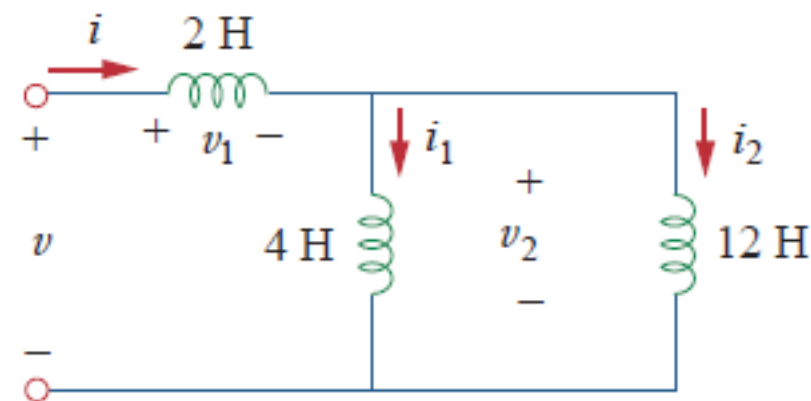

Check  $\rightarrow i(t) = i_1(t) + i_2(t)$
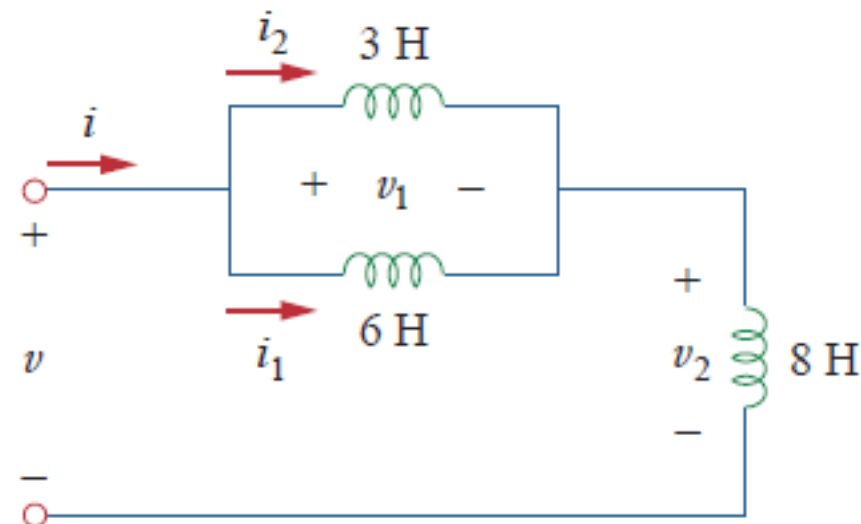
## Equivalent Inductance

**LCE.12** –  $i_1(t) = 0.6e^{-2t} \text{ A}$ ,  $i(0) = 1.4 \text{ A}$   
 a)  $i_2(0) = ?$   
 b)  $i_2(t) = ?$ ,  $i(t) = ?$   
 c)  $v_1(t) = ?$ ,  $v_2(t) = ?$ ,  $v(t) = ?$




**Solution** a)  $i_2(0) = 0.8 \text{ A}$   
 b)  $i_2(t) = (-0.4 + 1.2e^{-2t}) \text{ A}$ ,  $i(t) = (-0.4 + 1.8e^{-2t}) \text{ A}$   
 c)  $v_1(t) = -36e^{-2t} \text{ V}$ ,  $v_2(t) = -7.2e^{-2t} \text{ V}$ ,  $v(t) = -28.8e^{-2t} \text{ V}$

## Integrator Example

### LCE.13

$$v_1 = 10 \cos 2t \text{ mV}, v_2 = 0.5t \text{ mV}, v_C(0) = 0 \text{ V}$$

$$v_o = ?$$

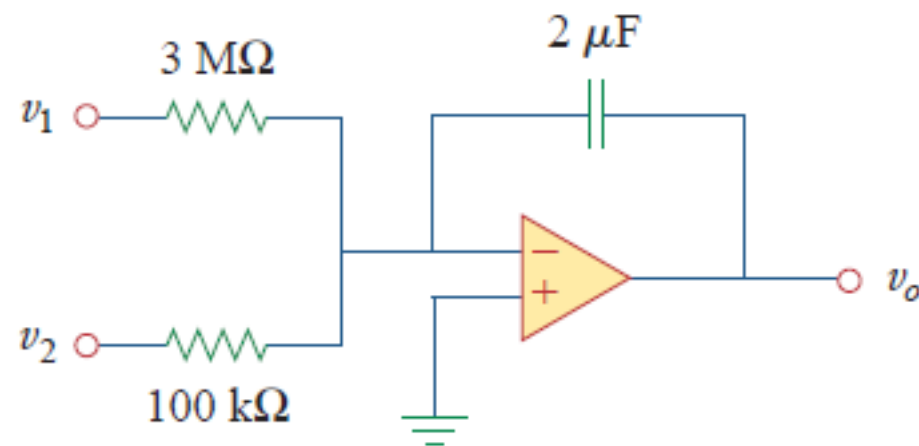

**Solution** (*summing intergaror*)

$$v_o = -\frac{1}{R_1 C} \int v_1 dt - \frac{1}{R_2 C} \int v_2 dt = -\frac{1}{3 \cdot 10^6 \cdot 2 \cdot 10^{-6}} \int_0^t 10 \cos 2t dt - \frac{1}{100 \cdot 10^3 \cdot 2 \cdot 10^{-6}} \int_0^t 0.5t dt$$



$$= -\frac{1}{6} \frac{10}{2} \sin 2t - \frac{1}{0.2} \frac{0.5t^2}{2} = -0.833 \sin 2t - 1.25t^2 \text{ mV}$$

# Differentiator Example

LCE.14

$$v_o(0) = 0 \text{ V}$$

$$v_o(t) = ?$$

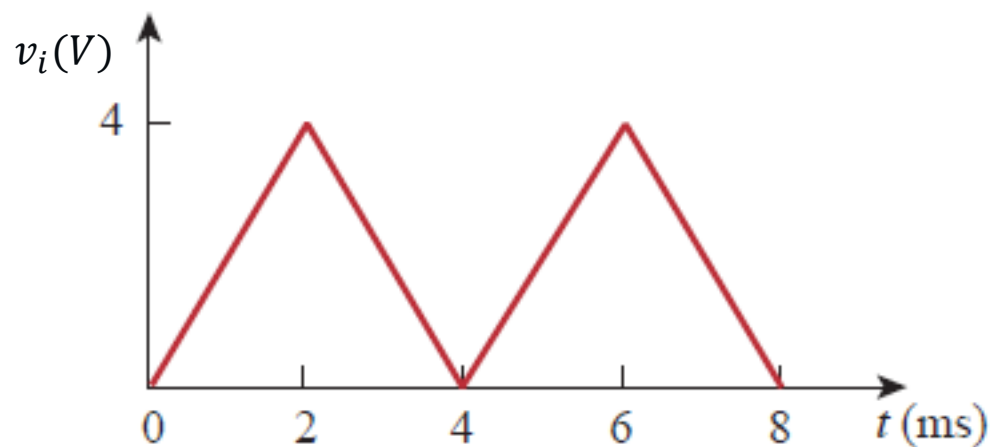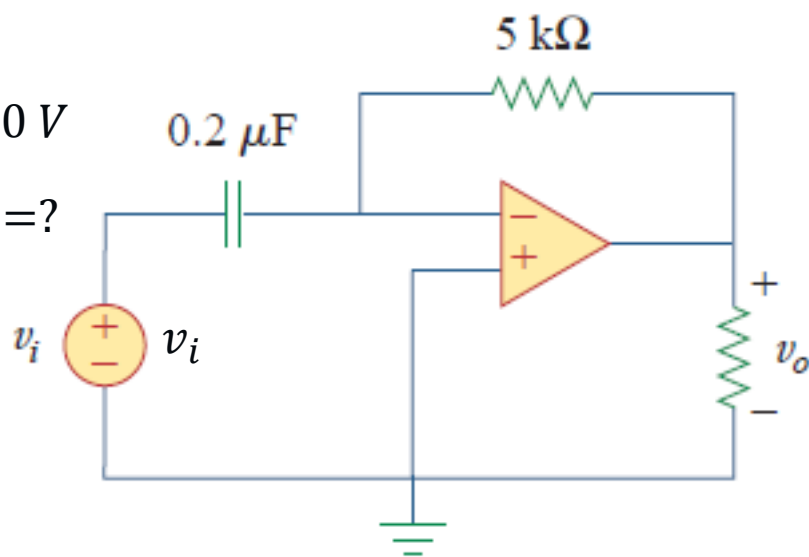


Solution (differentiator circuit)

$$RC = 5 \cdot 10^{-3} \cdot 2 \cdot 10^{-6} = 1 \text{ ms}$$

$$v_i = \begin{cases} 2000t & 0 < t < 2 \text{ ms} \\ 8 - 2000t & 2 < t < 4 \text{ ms} \end{cases}$$
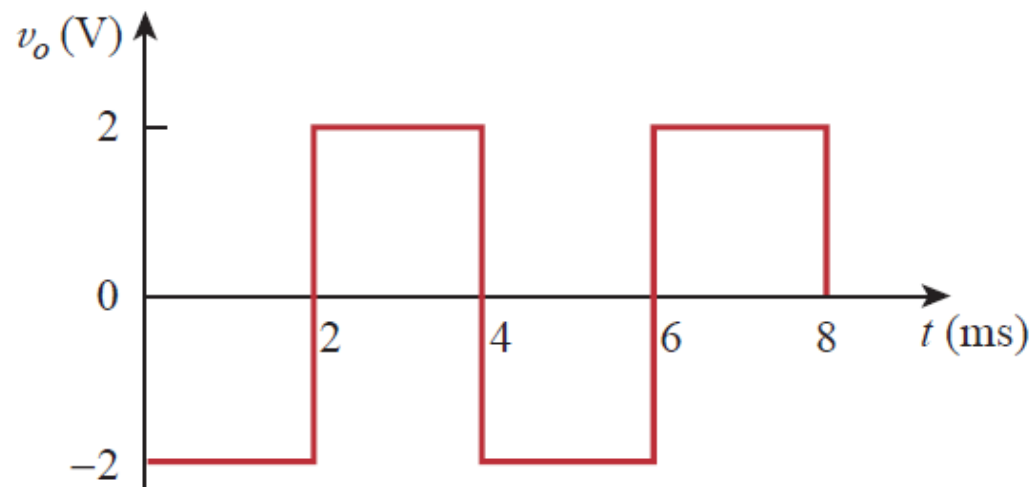
$$v_o = -RC \frac{dv_i}{dt} = \begin{cases} -2 \text{ V} & 0 < t < 2 \text{ ms} \\ +2 \text{ V} & 2 < t < 4 \text{ ms} \end{cases}$$





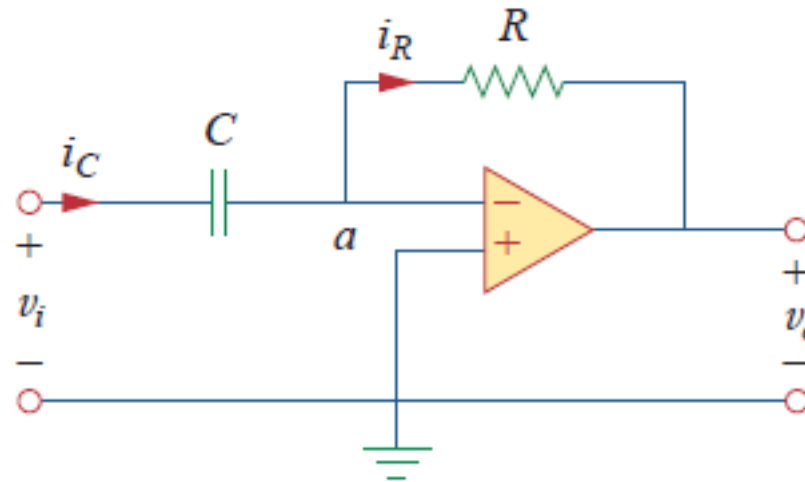
## Differentiator Example



LCE.15

$R = 100 \text{ k}\Omega$ ,  $C = 100 \text{ nF}$ ,  $v_i(t) = 3t \text{ V}$ ,  $v_o(t) = ?$



**Solution** (-30 mV)

# Questions

