




DR. GYURCSEK ISTVÁN

Exercises with Magnetically Coupled Circuits

Sources and additional materials (recommended)

- ❑ *Dr. Gyurcsek – Dr. Elmer: Theories in Electric Circuits, GlobeEdit, 2016, ISBN:978-3-330-71341-3*
- ❑ *Ch. Alexander, M. Sadiku: Fundamentals of Electric Circuits, 6th Ed., McGraw Hill NY 2016, ISBN: 978-0078028229*
- ❑ *W. M. Flanagan, Handbook of Transformer Design and Applications, 2nd ed. (New York: McGraw-Hill, 1993)*
- ❑ *Simonyi K.: Villamosságtan. AK Budapest 1983, ISBN:9630534134*
- ❑ *Zombory L.: Elektromágneses terek. MK Budapest 2006, (www.electro.uni-miskolc.hu)*

Mutual Inductance

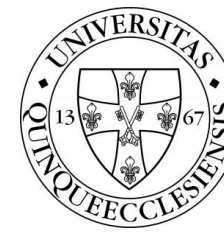

TRF.01

Calculate the phasor currents in the circuit if $V_S = 12$ V.


Solution

$$(1): -12 + (-j4 + j5)I_1 - j3I_2 \rightarrow jI_1 - j3I_2 = 12$$

$$(2): -j3I_1 + (12 + j6)I_2 = 0 \rightarrow I_1 = \frac{(12 + j6)I_2}{j3} = (2 - j4)I_2$$

$$(2 \rightarrow 1): (j2 + 4 - j3)I_2 = (4 - j) = 12 \rightarrow I_2 = \frac{12}{(4 - j)} = 2.91 e^{j14.04^\circ}$$

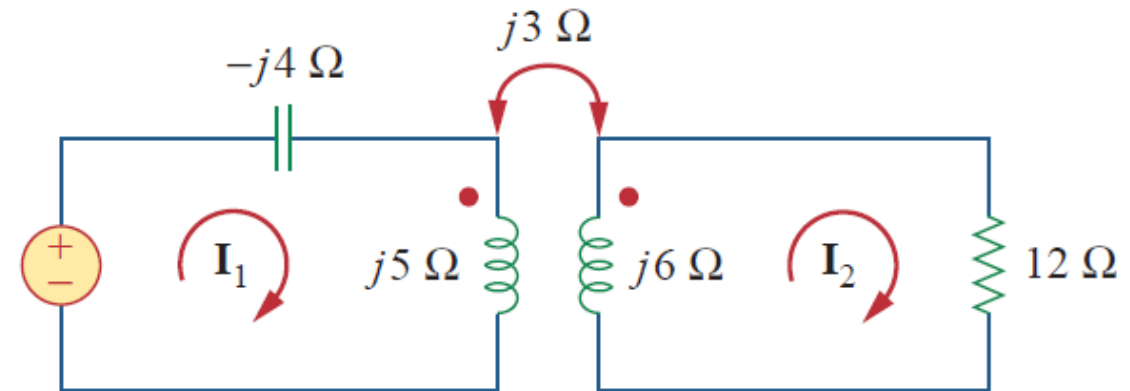
$$I_1 = (2 - j4)I_2 = (2 - j4)2.91 e^{j14.04^\circ} = 4.472 e^{-j63.43^\circ} \cdot 2.91 e^{j14.04^\circ} = 13.01 e^{-j49.39^\circ} \text{ A}$$



Mutual Inductance



TRF.02 – $V_0 = ?$.

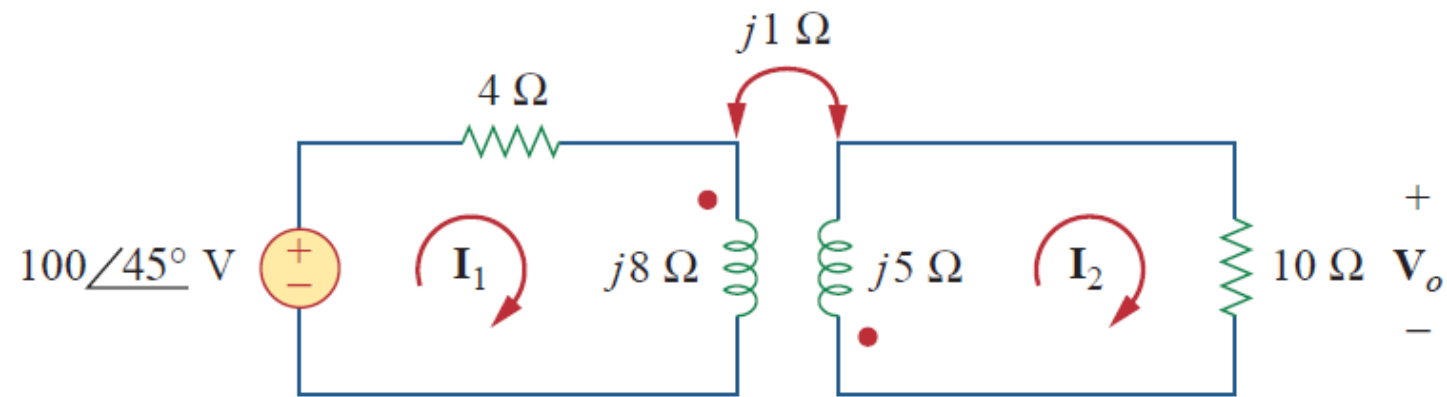


Solution $V_0 = 10 e^{-j135^\circ} \text{ V}$

Mutual Inductance



TRF.03

Calculate the mesh currents.

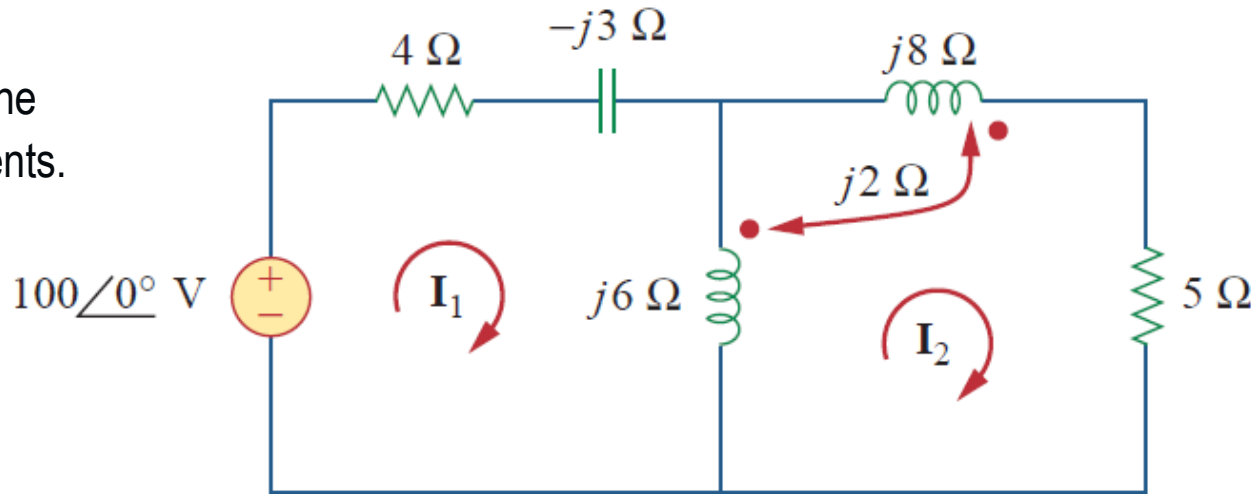

Solution



$$(\text{mesh1}): -100 + I_1(4 - j3 + j6) - j6I_2 - j2I_2 = 0$$

$$\rightarrow 100 = I_1(4 + j3) - j8I_2$$

$$(\text{mesh2}): 0 = -j2I_1 - j6I_1 + (j6 + j8 + j2 \cdot 2 + 5)I_2 = 0$$

$$\rightarrow 0 = -j8I_1 + (5 + j18)I_2$$
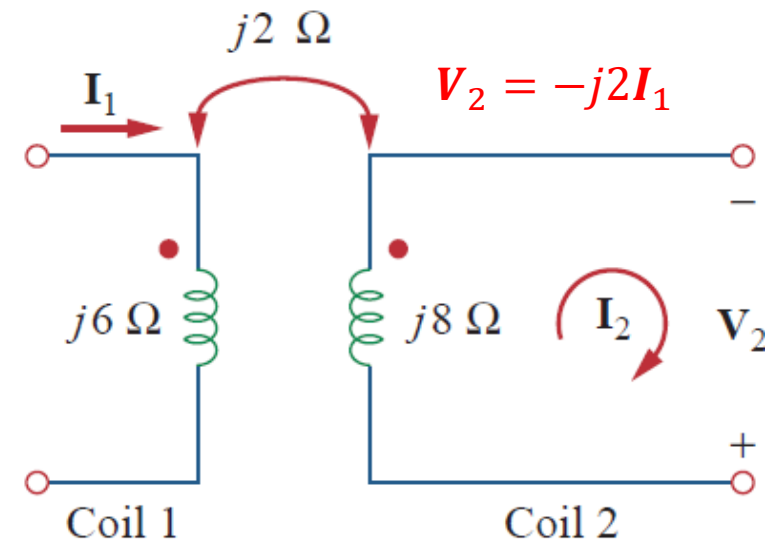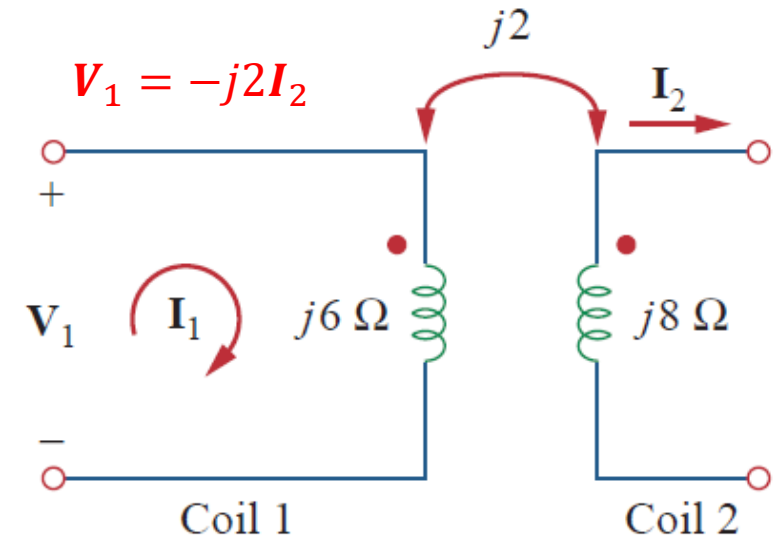
$$\begin{bmatrix} 100 \\ 0 \end{bmatrix} = \begin{bmatrix} 4 + j3 & -j8 \\ -j8 & 5 + j18 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



Mutual Inductance



$$\begin{bmatrix} 100 \\ 0 \end{bmatrix} = \begin{bmatrix} 4 + j3 & -j8 \\ -j8 & 5 + j18 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 4 + j3 & -j8 \\ -j8 & 5 + j18 \end{vmatrix} = 30 + j87$$

$$\Delta_1 = \begin{vmatrix} 100 & -j8 \\ 0 & 5 + j18 \end{vmatrix} = 100(5 + j18)$$

$$\Delta_2 = \begin{vmatrix} 4 + j3 & 100 \\ -j8 & 0 \end{vmatrix} = j800$$


$$I_1 = \frac{\Delta_1}{\Delta} = \frac{100(5 + j18)}{30 + j87} = \frac{1,868.2 e^{j74.5^\circ}}{92.03 e^{j71^\circ}} = 20.3 e^{j3.5^\circ} \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{j800}{30 + j87} = \frac{800 e^{j90^\circ}}{92.03 e^{j71^\circ}} = 8.693 e^{j19^\circ} \text{ A}$$

Mutual Inductance



TRF.04 – Calculate the mesh currents.

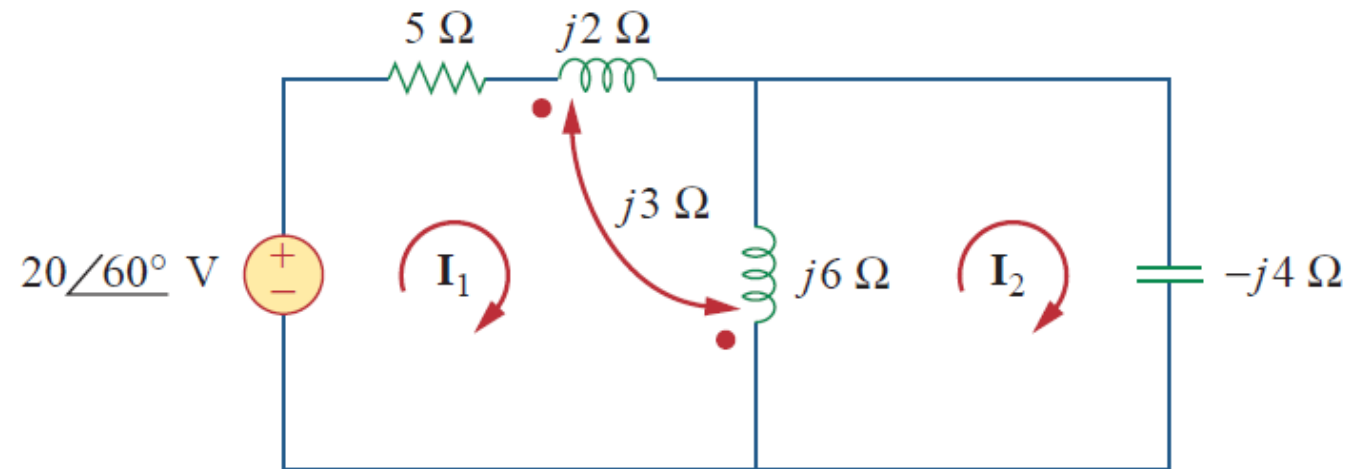

Solution $I_1 = 3.583 e^{j86.56^\circ} A$, $I_2 = 5.383 e^{j86.56^\circ} A$

Energy in Coupled Circuit



TRF.05 – Determine the coupling coefficient and calculate the energy stored in the coupled inductors at $t = 1$ s if

$$v = 60 \cos(4t + 30^\circ) \text{ V}$$

Solution $k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{20}} = 0.56$


(1): $(10 + j20)I_1 + j10I_2 = 60 e^{j30^\circ}$

(2): $j10I_1 + (j16 - j4)I_2 = 0 \rightarrow I_1 = -1.2I_2$

(2 \rightarrow 1): $(-12 - j14)I_2 = 60 e^{j30^\circ}$

$\rightarrow I_2 = 3.254 e^{j160.6^\circ} \text{ A}$

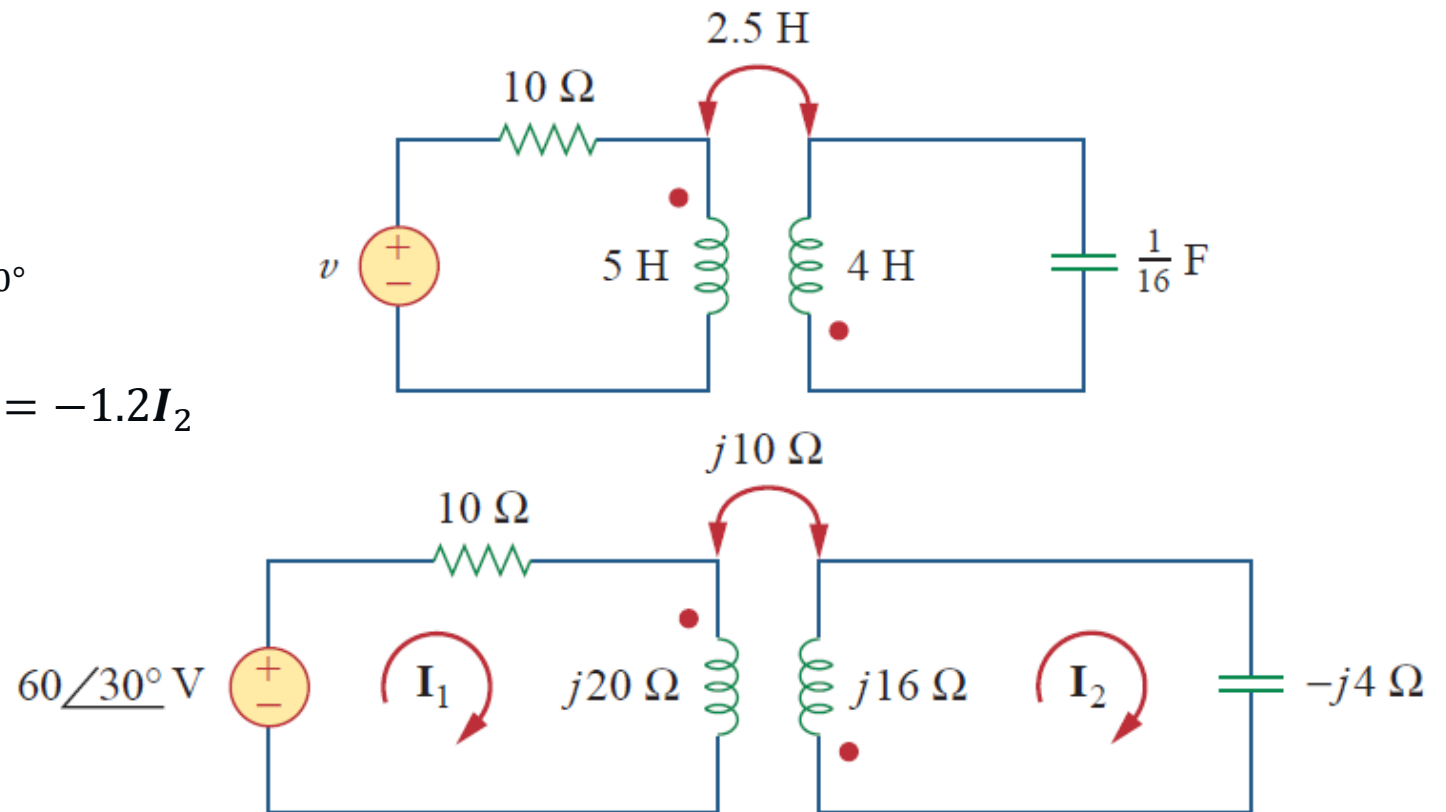$I_1 = -1.2I_2 = 3.905 e^{-j19.4^\circ} \text{ A}$



Energy in Coupled Circuit



$$I_1 = 3.905 e^{-j19.4^\circ} \rightarrow i_1(t) = 3.905 \cos(4t - 19.4^\circ)$$

$$I_2 = 3.254 e^{j160.6^\circ} \rightarrow i_2(t) = 3.254 \cos(4t + 160.6^\circ)$$

$$t = 1 \text{ s} \rightarrow 4t = 4 \text{ rad} = 229.2^\circ$$

$$I_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389 \text{ A}$$

$$I_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824 \text{ A}$$


$$w = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 \pm M I_1 I_2 = \frac{1}{2} \cdot 5 \cdot (-3.389)^2 + \frac{1}{2} \cdot 4 \cdot (2.824)^2 + 2.5 \cdot (-3.389) \cdot 2.824 = 20.73 \text{ J}$$

Energy in Coupled Circuit



TRF.06

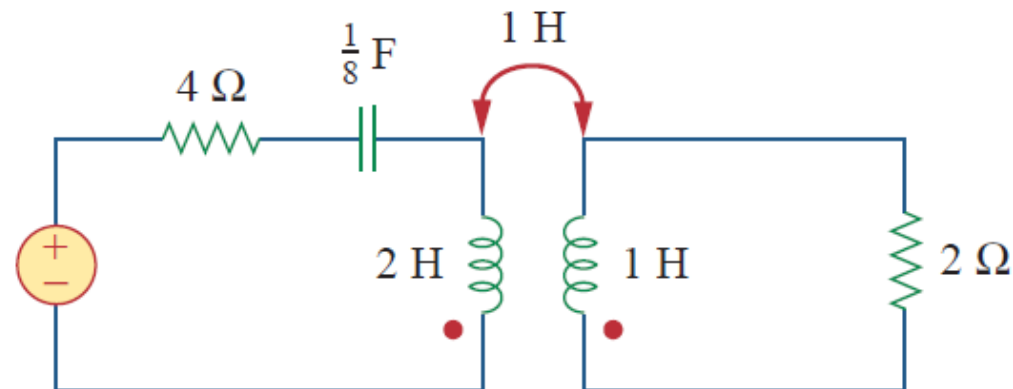Determine the coupling coefficient and calculate the energy stored in the coupled inductors at $t = 1.5$ s if $v_S = 40 \cos 4t$




Solution $k = 0.7071$, $w = 39.4 \text{ J}$

Linear Transformers



TRF.07 – Find the input impedance and current I_1 .
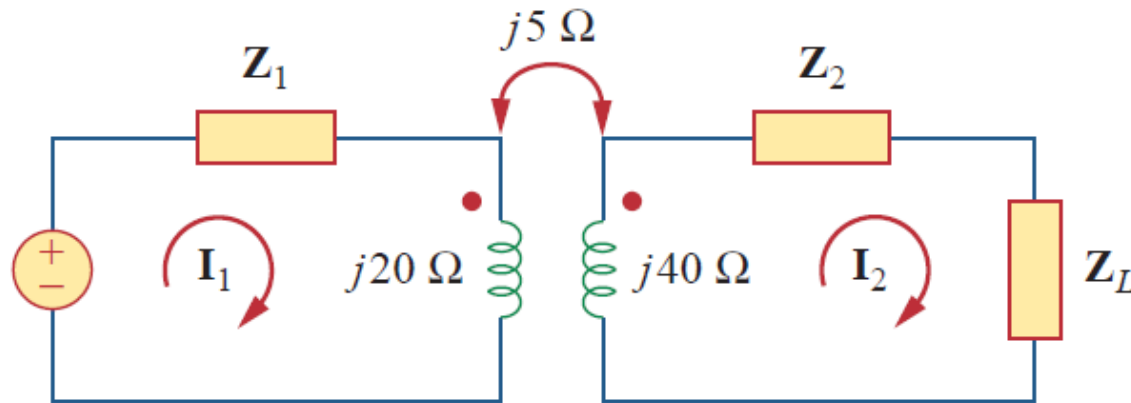
$$V_S = 50 e^{j60^\circ} \text{ V}, \mathbf{Z}_1 = 60 - j100 \ \Omega, \mathbf{Z}_2 = 30 + j40 \ \Omega, \mathbf{Z}_L = 80 + j60 \ \Omega$$




Solution


$$\mathbf{Z}_{in} = \mathbf{Z}_1 + j20 + \frac{5^2}{j40 + \mathbf{Z}_2 + \mathbf{Z}_L} = 60 - j100 + j20 + \frac{25}{110 + j140} = 60 - j80 + 1.14 e^{-j51.84^\circ}$$

$$= 60.09 - j80.11 = 100.14 e^{-j53.1^\circ} \ \Omega \quad \mathbf{I}_1 = \frac{\mathbf{V}}{\mathbf{Z}_{in}} = \frac{50 e^{j60^\circ}}{100.14 e^{-j53.1^\circ}} = 0.5 e^{j113.1^\circ} \ \text{A}$$

Linear Transformers

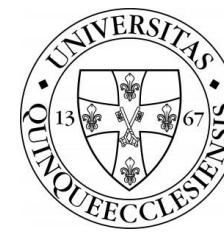

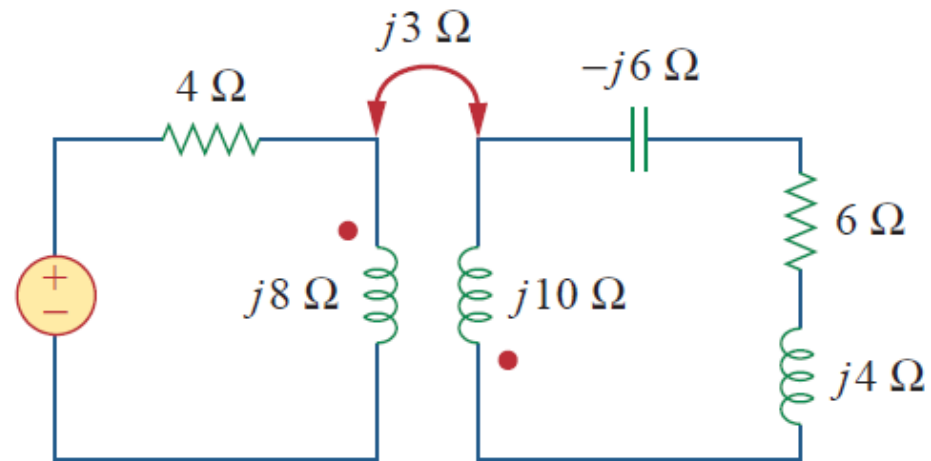TRF.08 – Find the input impedance and current from V_S if $V_S = 20 V$




Solution $Z_{in} = 8.58 e^{j58.05^\circ} \Omega$, $I_S = 2.331 e^{-j58.05^\circ} A$

Linear Transformers



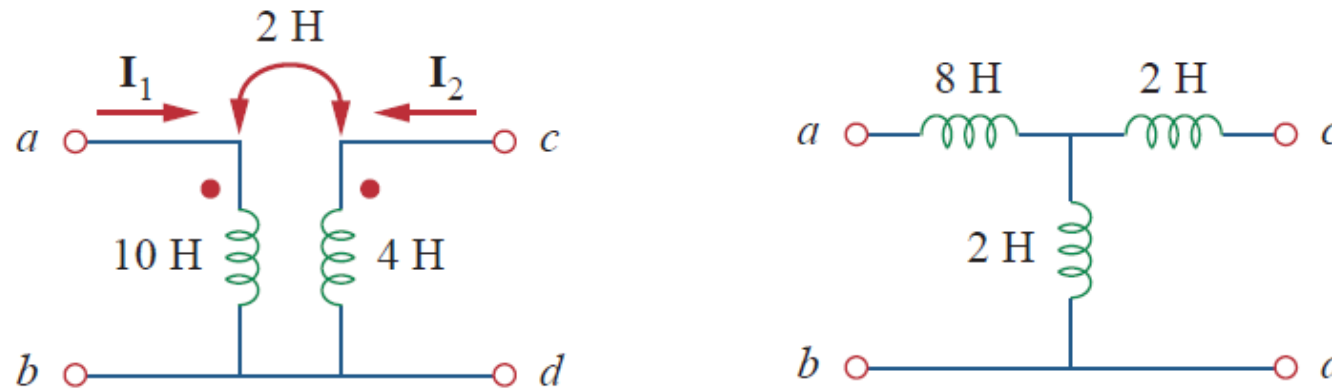TRF.09 – Determine the T-equivalent circuit of the linear transformer



Solution $L_1 = 10 H$, $L_2 = 4 H$, $M = 2 H$,

$$L_a = L_1 - M = 8 H, \quad L_b = L_2 - M = 2 H, \quad L_c = M = 2 H$$

Ideal Transformers



TRF.10 – $I_1 = ?$, $V_O = ?$, $S_S = ?$

Solution

$$Z_R = \frac{20}{n^2} = \frac{20}{4} = 5 \Omega$$


$$Z_{in} = 4 - j6 + Z_R = 9 - j6 = 10.82 e^{-j33.69^\circ} \Omega$$

$$I_1 = \frac{120}{Z_{in}} = 11.09 e^{j33.69^\circ} A$$


$$I_2 = -\frac{1}{n} I_1 = -5.545 e^{j33.69^\circ} = 5.545 e^{j213.69^\circ} A$$

$$V_O = 20 I_2 = 110.9 e^{j213.69^\circ} V$$

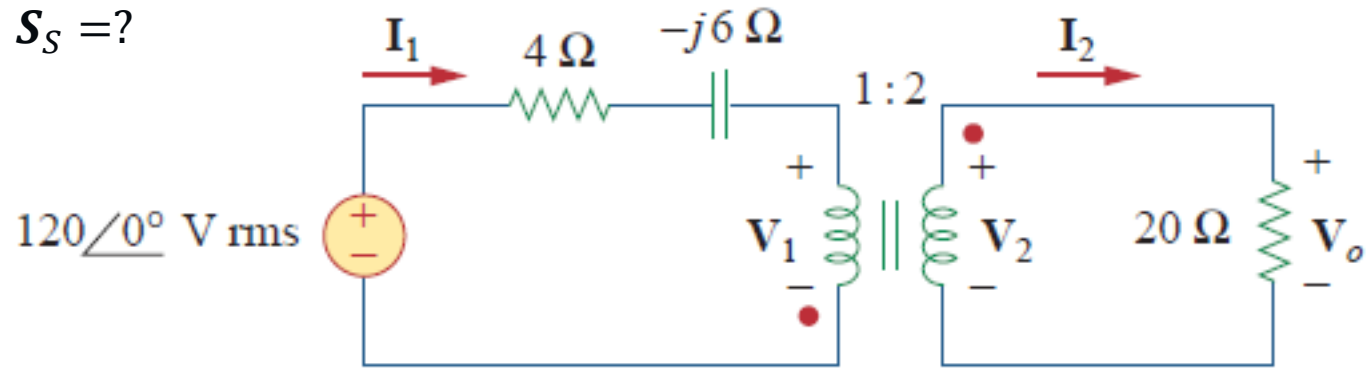
$$S_S = V_S I_1^* = 120 \cdot 11.09 e^{-j33.69^\circ} = 1,330.8 e^{-j33.69^\circ} VA$$



Ideal Transformers

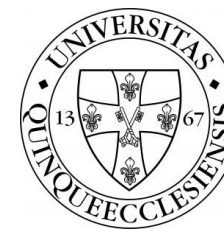

TRF.11 – $V_o = ?$, $S_S = ?$

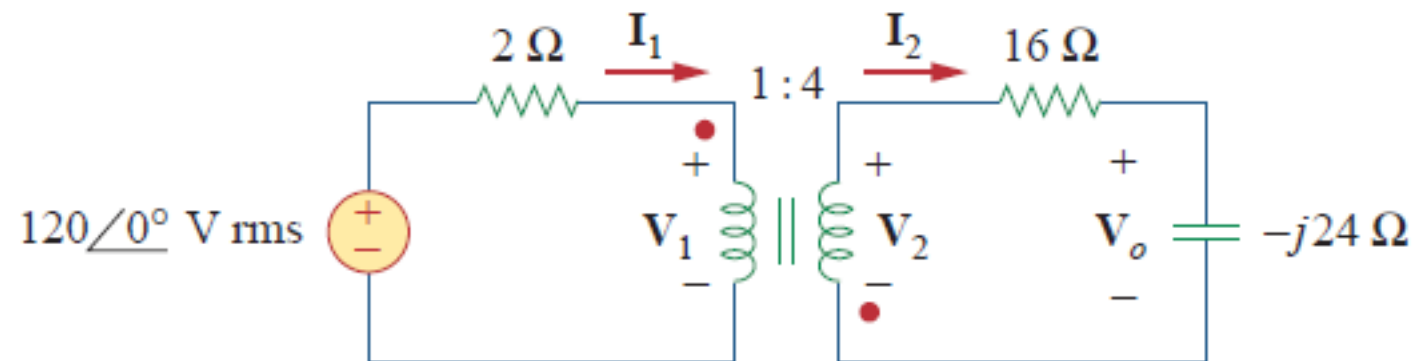

Solution $V_o = 214.7 e^{j116.56^\circ} \text{ V}$ $S_S = 4.293 e^{-j26.56^\circ} \text{ kVA}$

Ideal Transformers



TRF.12 – Calculate the power supplied to the load resistor.

Solution

$$\text{(mesh1): } -120 + (20 + 30)I_1 - 30I_2 + V_1 = 0$$

$$\rightarrow 50I_1 - 30I_2 + V_1 = 120$$

$$\text{(mesh2): } V_2 + (10 + 30)I_2 - 30I_1 = 0$$

$$\rightarrow -30I_1 + 40I_2 - V_2 = 0$$


$$V_2 = -\frac{1}{2}V_1, \quad I_2 = -2I_1$$

$$\text{(mesh1} \leftarrow V_1, I_1\text{): } -55I_2 - 2V_2 = 120$$

$$\text{(mesh2} \leftarrow V_1, I_1\text{): } 15I_2 + 40I_2 - V_2 = 0 \rightarrow V_2 = 55I_2$$

$$-165I_2 = 120 \rightarrow I_2 = -0.7272 \text{ A}$$

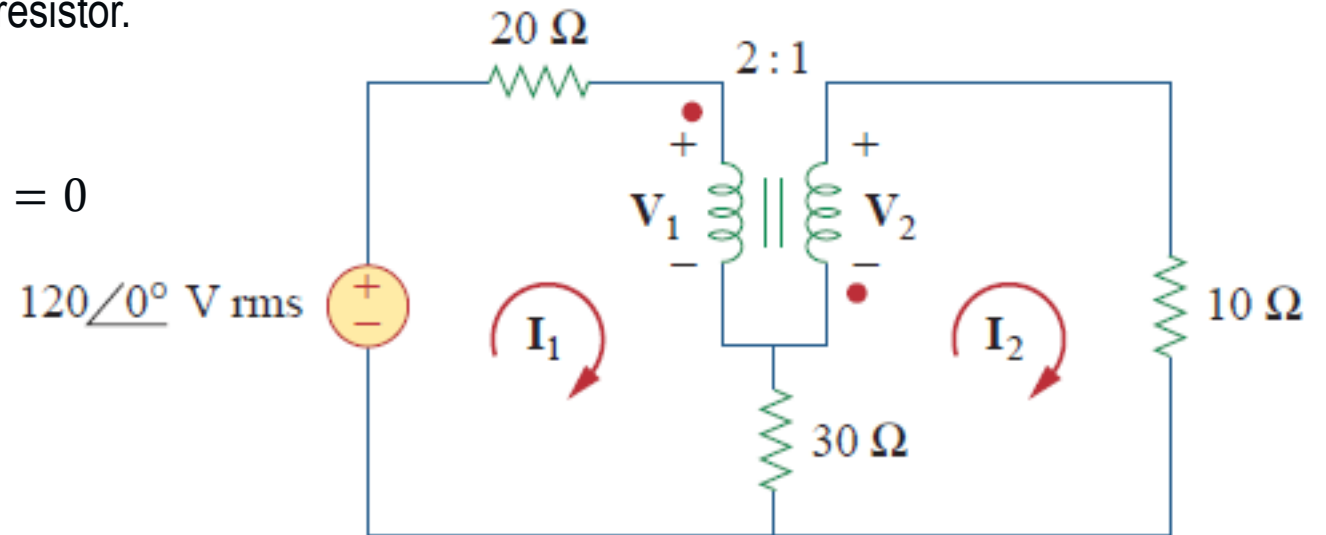
$$P = (-0.7272)^2 \cdot 10 = 5.3 \text{ W}$$



Ideal Transformers



TRF.13 - $V_o = ?$

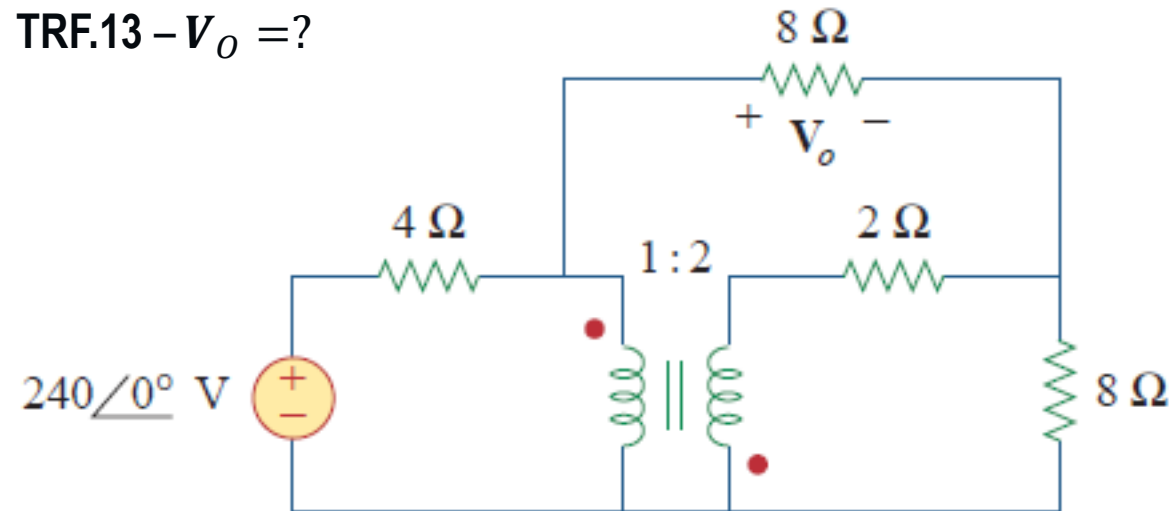


Solution ... 96 V

Ideal Autotransformers



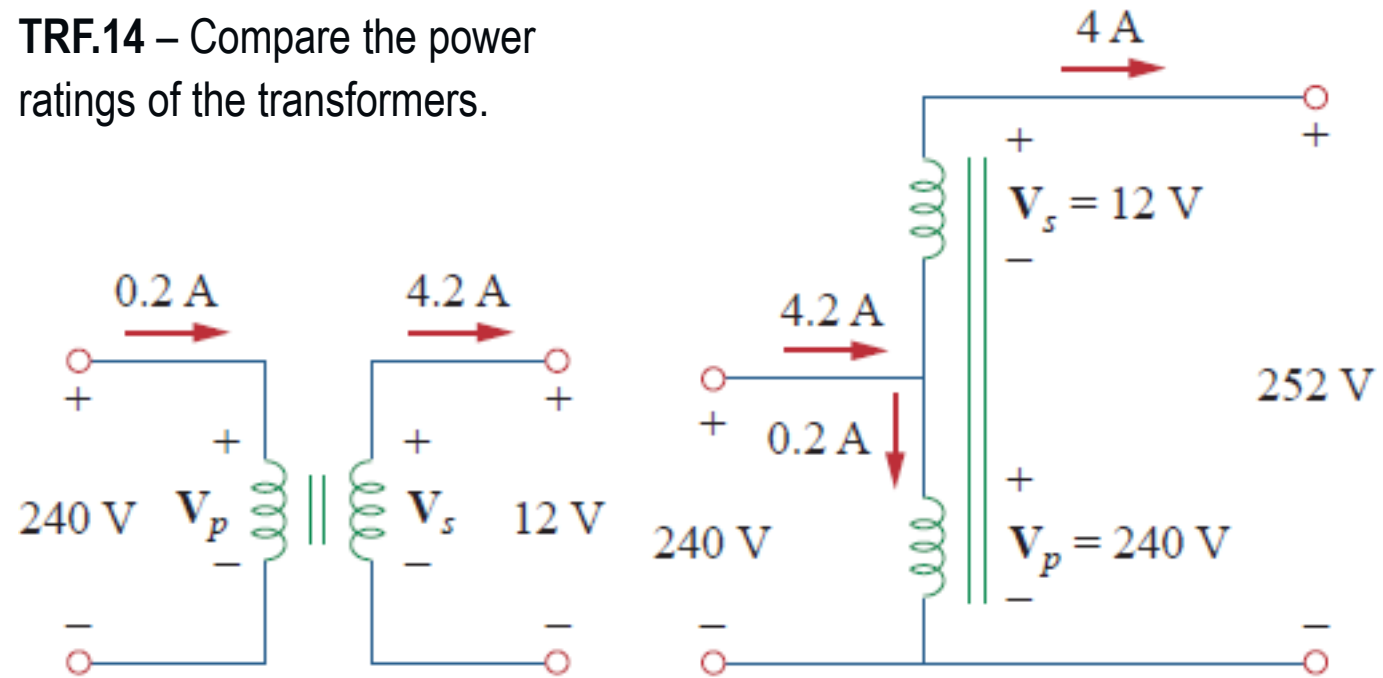TRF.14 – Compare the power ratings of the transformers.



Solution

(AUTOTR. 21 TIMES HIGHER!!!)

$$AUTOTR. \rightarrow S_1 = 4.2 \cdot 240 = 1,008 \text{ VA}, \quad S_2 = 4 \cdot 252 = 1,008 \text{ VA}$$

$$2 \text{ WINDING TR.} \rightarrow S_1 = 0.2 \cdot 240 = 48 \text{ VA}, \quad S_2 = 4 \cdot 12 = 48 \text{ VA}$$

Ideal Autotransformers



TRF.15 – $Z_L = (8 + j6) \Omega$, $I_1 = ?$, $I_2 = ?$, $I_0 = ?$, $S_L = ?$

Solution


$$\frac{V_1}{V_2} = \frac{N_1}{N_1 + N_2} = \frac{80}{200}$$

$$V_2 = \frac{200}{80} V_1 = \frac{200}{80} 120 e^{j30^\circ} = 300 e^{j30^\circ} \text{ V}$$

$$I_2 = \frac{V_2}{Z_L} = \frac{300 e^{j30^\circ}}{8 + j6} = \frac{300 e^{j30^\circ}}{10 e^{j36.87^\circ}} = 30 e^{-j6.87^\circ} \text{ A}$$

$$\frac{I_1}{I_2} = \frac{N_1 + N_2}{N_1} = \frac{200}{80}$$

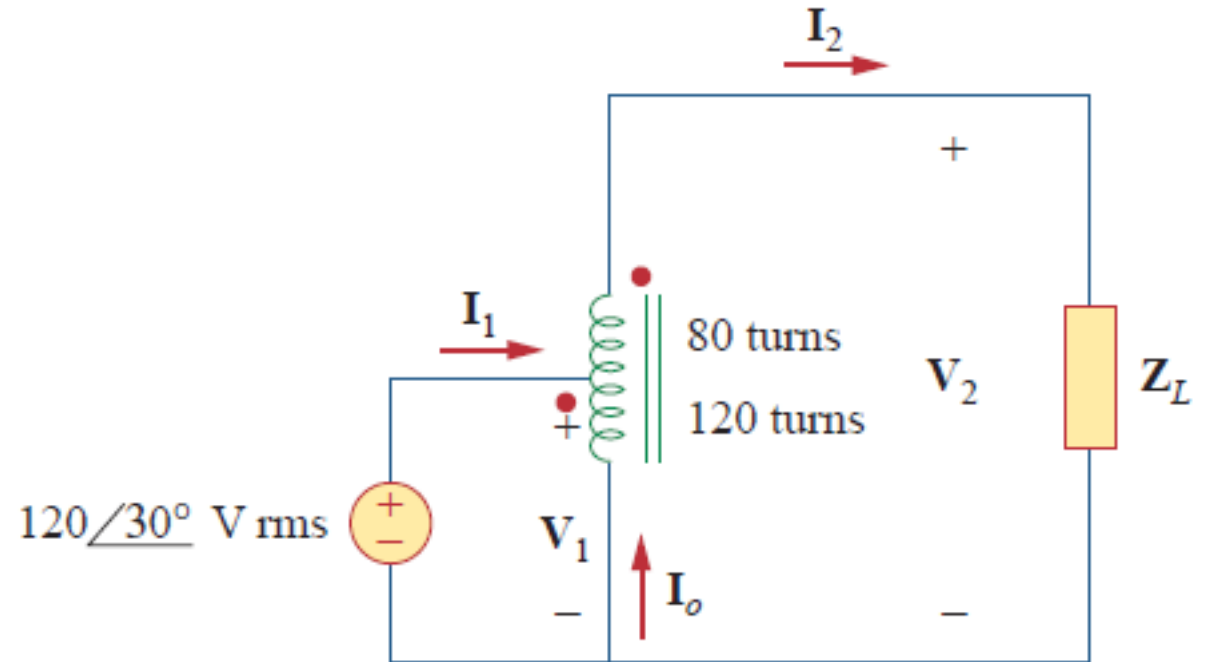
$$I_1 = \frac{200}{80} I_2 = \frac{200}{80} 30 e^{-j6.87^\circ} = 75 e^{-j6.87^\circ}$$




$$I_1 + I_0 = I_2 \rightarrow I_0 = I_2 - I_1 = 30 e^{-j6.87^\circ} - 75 e^{-j6.87^\circ} = 45 e^{j173.13^\circ}$$

$$S_2 = V_2 I_2^* = I_2^2 Z_L = 30^2 \cdot 10 e^{j36.87^\circ} = 9 e^{j36.87^\circ} \text{ kVA}$$

Ideal Autotransformers

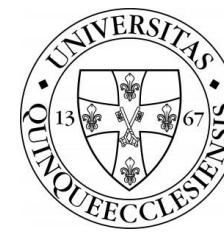

TRF.16 – $V_1 = 1,250 \text{ V}$, $V_2 = 500 \text{ V}$, $I_1 = ?$, $I_2 = ?$, $I_o = ?$

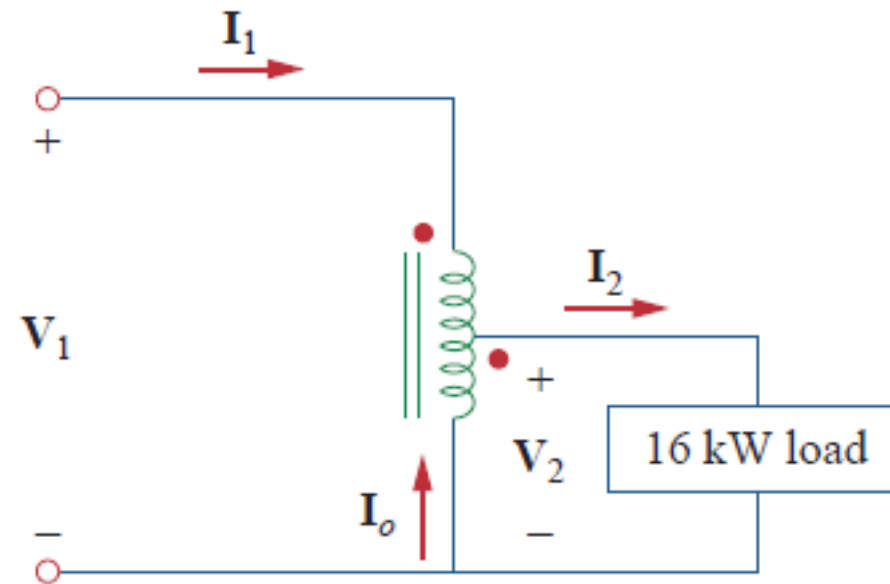

Solution 12.8 A, 32 A, 19.2 A

Three-Phase Transformers




TRF.17 – Determine the type of transformer connections. Find the line voltage and current on the primary side.
Determine the kVA rating of each transformer used in the transformer bank. (The transformers are ideal.)

Solution ... (YD)

$$I_{Ls} = \frac{S_{tot}}{\sqrt{3}V_{Ls}} = \frac{42,000}{\sqrt{3} \cdot 240} = 101 \text{ A}$$

$$I_{Lp} = \frac{n}{\sqrt{3}} I_{Ls} = \frac{5 \cdot 101}{\sqrt{3}} = 292 \text{ A}$$
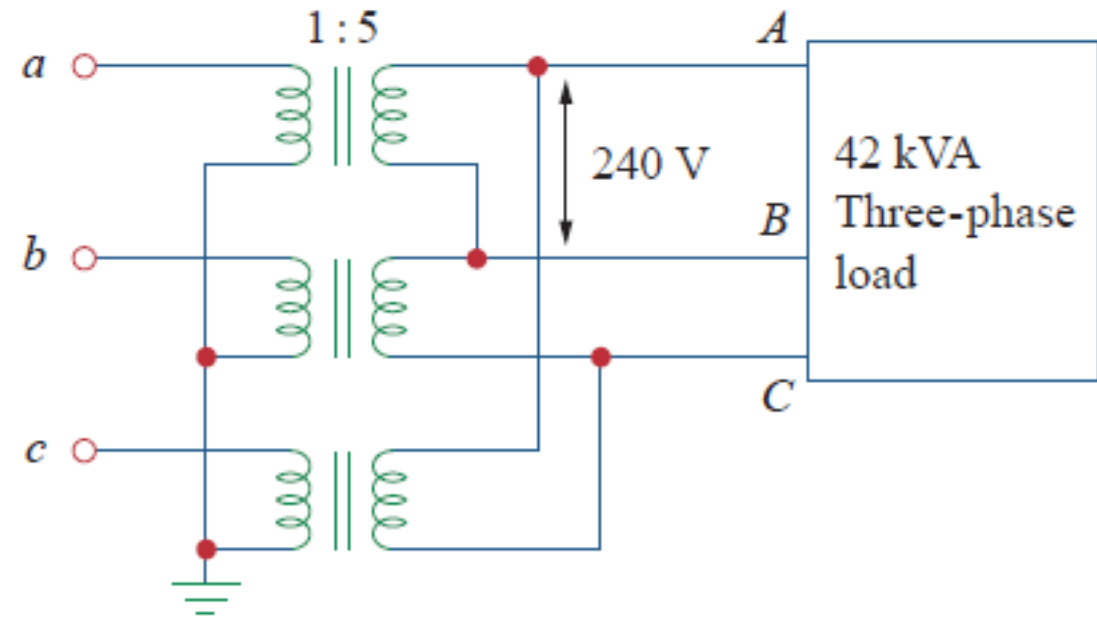
$$V_{Lp} = \frac{\sqrt{3}}{n} V_{Ls} = \frac{\sqrt{3} \cdot 240}{5} = 83.14 \text{ V}$$



$$S = \frac{S_{tot}}{3} = 14 \text{ kVA} \quad \dots \text{or} \quad S_s = V_{Ps} I_{Ps} = V_{Ls} \frac{I_{Ls}}{\sqrt{3}} = 240 \cdot \frac{101}{\sqrt{3}} = 14 \text{ kVA} \quad \dots \text{or} \quad S_p = V_{Pp} I_{Pp} = \frac{V_{Lp}}{\sqrt{3}} I_{Lp} = \frac{83.14}{\sqrt{3}} \cdot 292 = 14 \text{ kVA}$$

Three-Phase Transformers



TRF.18 – A three-phase DD transformer is used to step down a line voltage of 625 kV, to supply a plant operating at a line voltage of 12.5 kV. The plant draws 40 MW with a lagging power factor of 85 percent.

Find:

- a) the current drawn by the plant
- b) the turns ratio
- c) the current on the primary side of the transformer
- d) the load carried by each transformer

Solution (a) 2.1736 kA, (b) 0.02, (c) 43.47 A, (d) 15.69 MVA.

Questions

